

17415

21718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic communication devices are not permissible in Examination Hall.

Marks

1. Attempt any TEN of the following:

20

- a) State Fleming's right hand rule.
- b) Classify different types of generators.
- c) Draw:
 - (i) Torque Vs. Armature current.
 - (ii) Speed Vs. armature current.Characteristics for DC shunt motor.
- d) State Fleming's left hand rule.
- e) Which DC motor can be selected for following types of loads
 - (i) Electric Traction
 - (ii) Lathe Machine
 - (iii) Crane
 - (iv) Printing Machine

P.T.O.

- f) Give classification of DC motors.
- g) Classify types of transformers.
- h) Draw circuit diagram for short circuit test of single phase transformer.
- i) Why transformer rating is in KVA?
- j) Write difference between efficiency and all day efficiency of transformer.
- k) Draw connection diagram of transformer for Scott connection.
- l) State types of cooling arrangements used in transformer (Any four).

2. Attempt any FOUR of the following: 16

- a) State principle of operation of DC generator.
- b) Derive an e.m.f. equation of generator.
- c) "D.C. Series motor cannot operate on no load." – Justify the statement.
- d) Write power stages of DC motor with flow diagram.
- e) State the necessity of starter for D.C. motor. State various types of D.C. motor starter.
- f) A 220 V DC shunt motor runs at a speed of 850 rpm and takes a current 20 A from mains. Calculate the speed if the torque is doubled. Armature resistance is 0.2Ω .

3. Attempt any FOUR of the following: 16

- a) Draw practical transformer on load phasor diagram at lagging P.F.
- b) Estimate the percentage efficiency and regulation of a 100 KVA, 6600 V/250 V, 50hz 1ϕ transformer at full load and 0.8 lagging p.f. from following readings
O.C. test : 6600 V, 1.5 A, 900 W,
S.C. test : 290 V, 12 A, 860 W.

- c) Compare distribution transformer with power transformer on any four points.
- d) Draw the equivalent circuit of transformer referred to primary side.
- e) State any two advantages of parallel operation of transformer. State the two conditions for connecting single phase transformers in parallel.
- f) Identify the circuit diagram given in Fig. No. 1 Select proper range of all meters if the transformer is having rating of 440 V/ 220 V, 2 KVA.

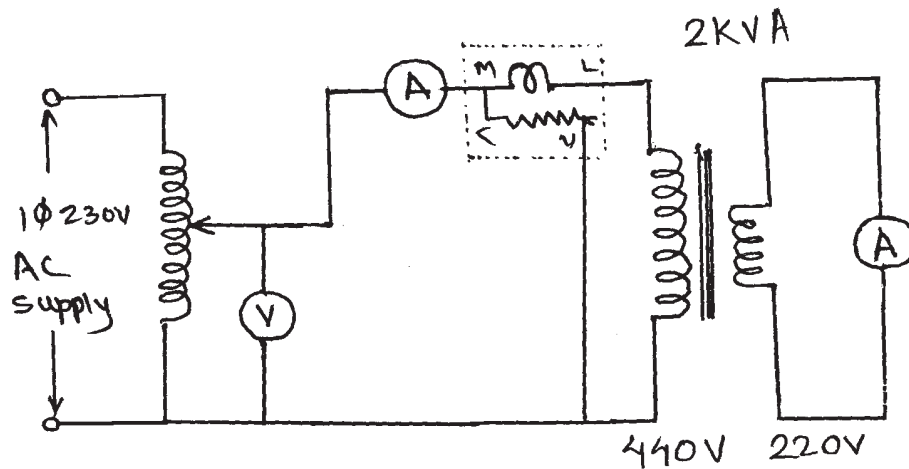


Fig. No. 1

4. Attempt any FOUR of the following:

16

- a) A 40 KVA, single phase transformer with a ratio of 2000 / 250 V has a primary resistance of 1.15Ω and a secondary resistance of 0.01555Ω . If the transformer is designed for 75% of full load, find its efficiency when delivering full load at 0.8 power factor.
- b) Fig. No. 2 shows the equivalent circuit of a 220/2200 V, single phase transformer as referred to the primary side. Calculate:
- Primary current
 - Power factor
 - Secondary terminal voltage.
 - Output of transformer.

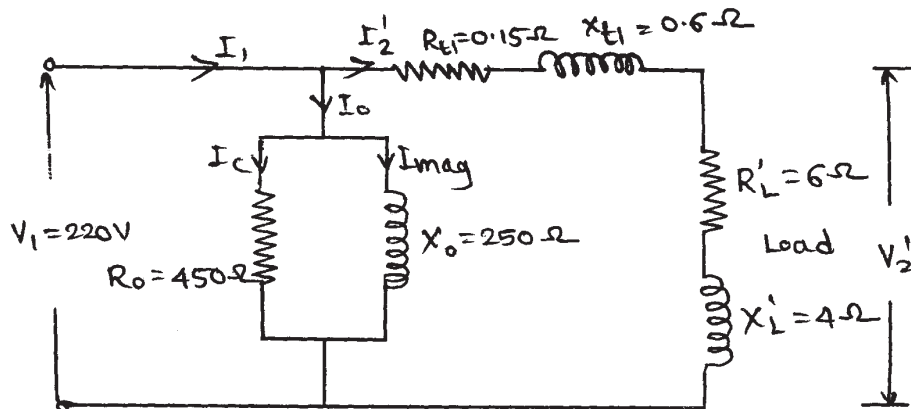


Fig. No. 2

- c) Two transformers A of 40 KVA with $Z_A = (3 + j4) \Omega$ and B of 25 KVA. Share equally a load of 50 KVA. While working in parallel, Find how they will share a load of 40 KVA. Comment your answer.
- d) The efficiency of 100 KVA, 1100/440 V, 1ϕ transformer is 87% on half load at 0.8 (lag) and 89% on full load at unity power factor. Determine iron and copper losses.
- e) List various losses in a transformer and the places at which they occur.
- f) Derive the condition for obtaining maximum efficiency of transformer.

5. Attempt any FOUR of the following:

16

- a) Draw polarity test of 1 ϕ transformer.
- b) A 500 KVA, distribution transformer having copper and iron losses of 5 KW and 3 KW respectively. On full load. The transformer is loaded as shown below.

Loading (KW)	Power Factor (lag)	No. of hrs.
400	0.8	08
300	0.75	10
200	0.8	03
No load	—	03

- c) State the advantages of a morphous core type distribution transformer.
- d) State with neat sketch the construction of three phase auto transformer.
- e) What is the aim of conducting phasing out test on three phase transformer? Draw diagrams for phasing out test.
- f) Write selection criteria of distribution transformer with any four point.

6. Attempt any FOUR of the following:

16

- a) Identify the parts shown in the diagram of a transformer in Fig. No. 3

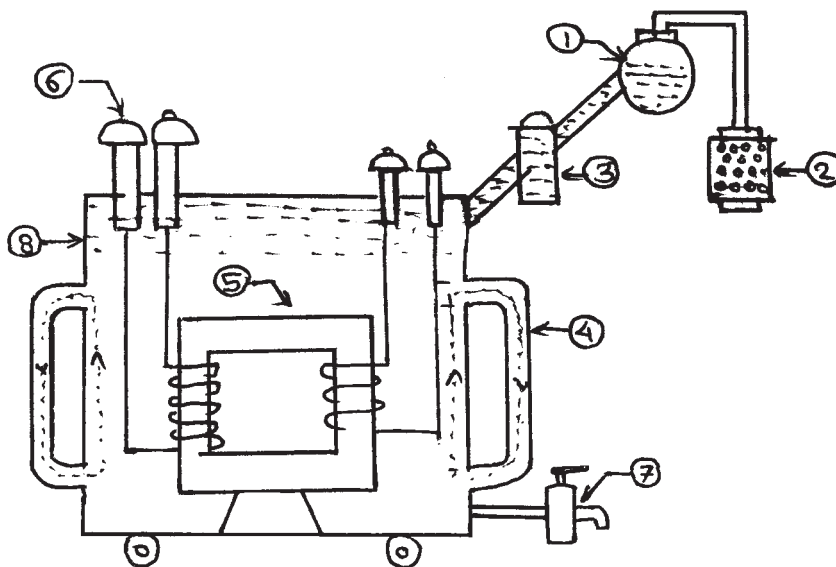


Fig. No. 3

P.T.O.

17415

[6]

Marks

- b) Compare auto transformer with two winding transformer.
(Any four point.)
 - c) Explain construction and operation of current transformer.
Draw a connection diagram for C.T. connection with 1ϕ load.
 - d) Explain construction and working of isolation transformer.
 - e) Compare single phase welding transformer with two winding transformer on the basis of construction, winding size.
 - f) List special features (any four) of isolation transformer with any four applications.
-