



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION

(Autonomous)
(ISO/IEC - 27001 - 2005 Certified)

SUMMER- 2019 EXAMINATION

Subject Name: Analog Circuits



Model Answer

Subject Code:

22433

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by the candidate may vary, but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills)
- 4) While assessing figures, the examiner may give credit for principal components indicated in the figure. The figures drawn by the candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and the model answer.
- 6) In case of any questions credit may be given by judgement on the part of examiner of relevant answer based on candidate's understanding.
- 7) In programming language papers, credit may be given to any other program based on equivalent concept.

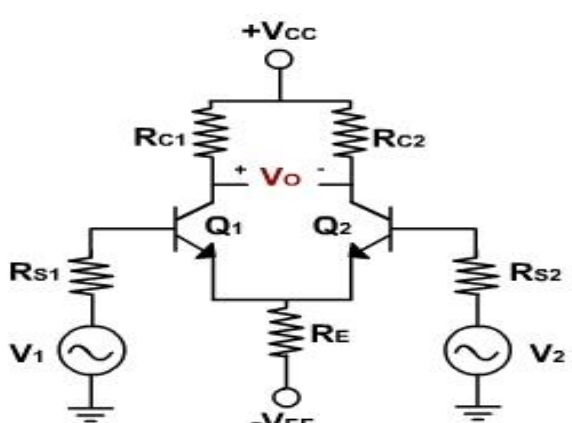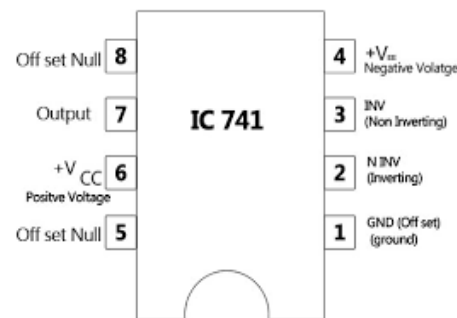Q. No.	Sub Q. N.	Answer	Marking Scheme
1.		Attempt any FIVE of the following:	10 M
	a)	<p>Draw circuit diagram of dual input Balanced output differential amplifier. Ans:</p>  <p style="text-align: center;">Fig: Dual input Balanced output differential amplifier</p>	02M
	b)	<p>Draw pin diagram of IC 741. Ans:</p>  <p style="text-align: center;">Fig: Pin diagram of IC 741</p>	02M

c) Suggest and draw op-amp based circuit using Butterworth filter to fulfill following frequency response (Refer Fig. No.1).

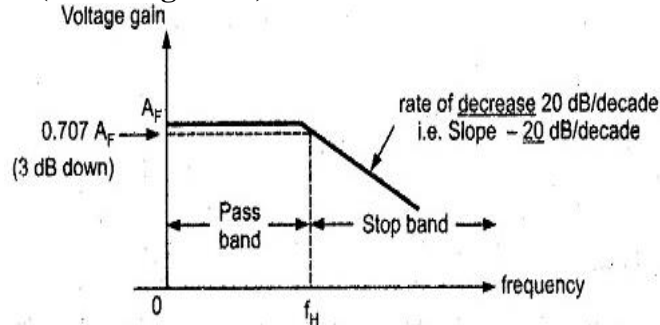


Fig. No. 1

Ans:

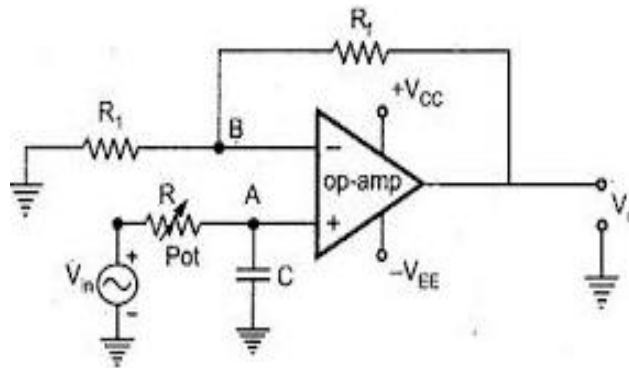


Fig: Butterworth low pass filter

02M

d) Draw astable multivibrator using IC 555.

Ans:

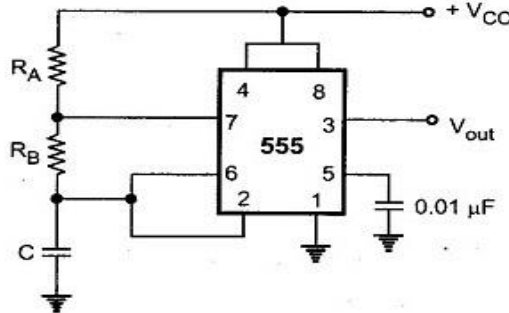


Fig: Astable multivibrator

02M

e) Draw circuit diagram of Butterworth band pass filter using OP-AMP

Ans:

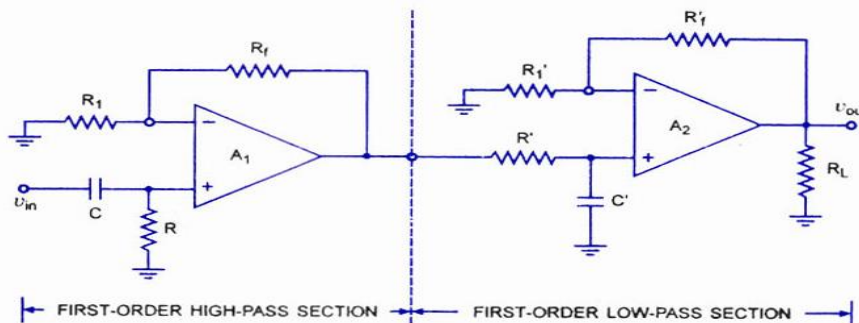
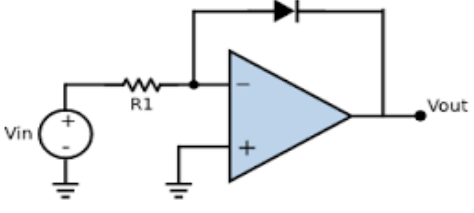
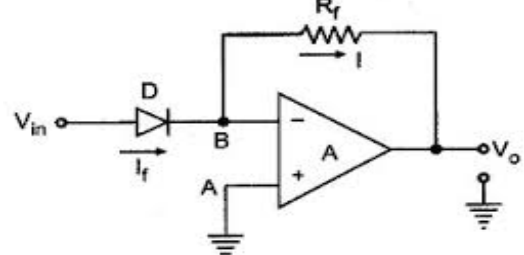
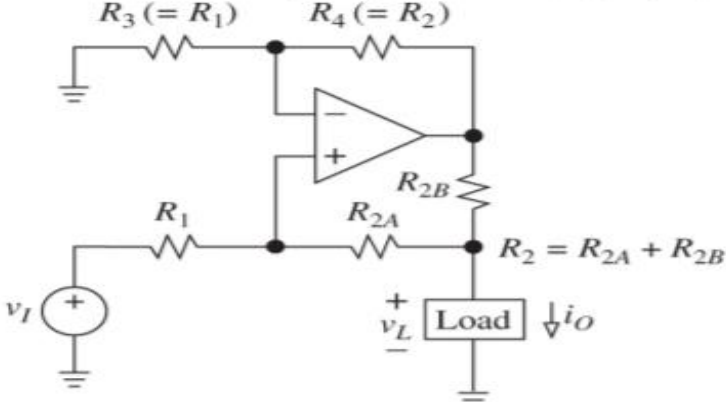
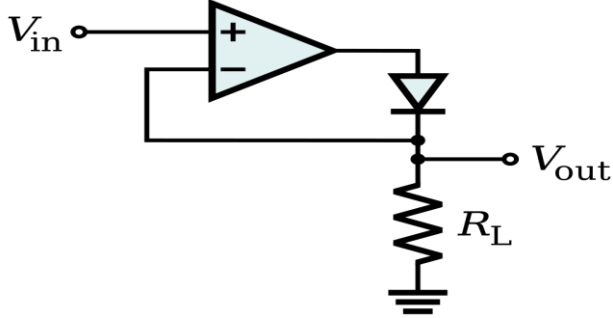
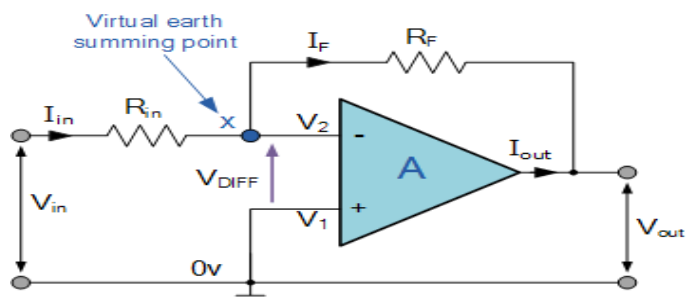


Fig: Butterworth band pass filter using OP-AMP

02M

<p>f)</p>	<p>Draw circuit diagram of log and antilog amplifiers using OP-AMP. Ans:</p> <div style="display: flex; justify-content: space-around;"> <div style="text-align: center;">  <p>Fig: Log amplifier</p> </div> <div style="text-align: center;">  <p>Fig: Antilog amplifier</p> </div> </div> <p style="text-align: center;">Table: Circuit diagram of log and antilog amplifier using OP-AMP</p>	<p>02M</p>
<p>g)</p>	<p>Draw circuit diagram of V to I converter using OP-AMP with grounded load. Ans:</p>  <p style="text-align: center;">Fig: V to I converter using OP-AMP with grounded load.</p>	<p>02M</p>
<p>2.</p>	<p>Attempt any THREE of the following:</p>	<p>12 M</p>
<p>a)</p>	<p>Draw circuit diagram of precision rectifier using op-amp and describe its working. Ans:</p>  <p style="text-align: center;">Fig: Circuit diagram of precision rectifier using op-amp</p> <p>The precision rectifier, also known as a super diode, is a configuration obtained with an operational amplifier in order to have a circuit behave like an ideal diode and rectifier.^[1] It is useful for high-precision signal processing. The op-amp-based precision rectifier should not be confused with the power MOSFET-based active rectification ideal diode. The basic circuit implementing such a feature is shown on the right, where can be any load. When the input voltage is negative, there is a negative voltage on the diode, so it works like an open circuit, no current flows through the load, and the output voltage is zero. When the input is positive, it is amplified by the operational amplifier, which switches the diode on. Current flows through the load and,</p>	<p>02M</p> <p>02M</p>

	<p>because of the feedback, the output voltage is equal to the input voltage. The actual threshold of the super diode is very close to zero, but is not zero. It equals the actual threshold of the diode, divided by the gain of the operational amplifier. This basic configuration has a problem, so it is not commonly used. When the input becomes (even slightly) negative, the operational amplifier runs open-loop, as there is no feedback signal through the diode. For a typical operational amplifier with high open-loop gain, the output saturates. If the input then becomes positive again, the op-amp has to get out of the saturated state before positive amplification can take place again. This change generates some ringing and takes some time, greatly reducing the frequency response of the circuit.</p>	
<p>b)</p>	<p>With neat sketch derive the expression for output voltage of inverting amplifier. Ans:</p>  <p>Fig: Inverting amplifier Expression for output voltage of inverting amplifier:</p> $i = \frac{V_{in} - V_{out}}{R_{in} + R_f}$ <p>therefore, $i = \frac{V_{in} - V_2}{R_{in}} = \frac{V_2 - V_{out}}{R_f}$</p> $i = \frac{V_{in}}{R_{in}} - \frac{V_2}{R_{in}} = \frac{V_2}{R_f} - \frac{V_{out}}{R_f}$ <p>so, $\frac{V_{in}}{R_{in}} = V_2 \left[\frac{1}{R_{in}} + \frac{1}{R_f} \right] - \frac{V_{out}}{R_f}$</p> <p>and as, $i = \frac{V_{in} - 0}{R_{in}} = \frac{0 - V_{out}}{R_f}$ $\frac{R_f}{R_{in}} = \frac{0 - V_{out}}{V_{in} - 0}$</p> <p>the Closed Loop Gain (A_v) is given as, $\frac{V_{out}}{V_{in}} = - \frac{R_f}{R_{in}}$</p>	<p>02M</p> <p>02M</p>
<p>c)</p>	<p>Design second order butterworth high pass filter. If pass band gain is 2, R = 20 kΩ, C = 0.05 μF and draw the designed circuit diagram. Ans: Design steps of second order butterworth high pass filter as follows: Let us consider the capacitor values as $C_1 = C_2 = C = 0.05 \mu F$ Let us consider the capacitor values as $R_1 = R_2 = R = 20 k\Omega$ The equation of the cut-off frequency is $F = 1 / 2\pi RC$ By re-arranging this equation we have $F = 1 / 2\pi RC$</p>	<p>02M</p>

By substituting the values of capacitor as $0.05\mu\text{F}$ AND $R = 20\text{ K}\Omega = 2\text{ K}\Omega$. and calculate cut-off frequency. Therefore cut-off frequency is **0.19 KHz**

Fc=0.159 KHz

Let the gain of the filter is $1 + R_1/R_2 = 2$

$$R_1 / R_2 = 1$$

$$R_1 = R_2$$

Therefore we can take $R_1 = R_2 = 20\text{ K}\Omega$

The gain of the filter is $1 + R_1/R_2$ and the equation of the cut-off frequency is $f_c = 1 / 2\pi\sqrt{R_3R_4C_1C_2}$.

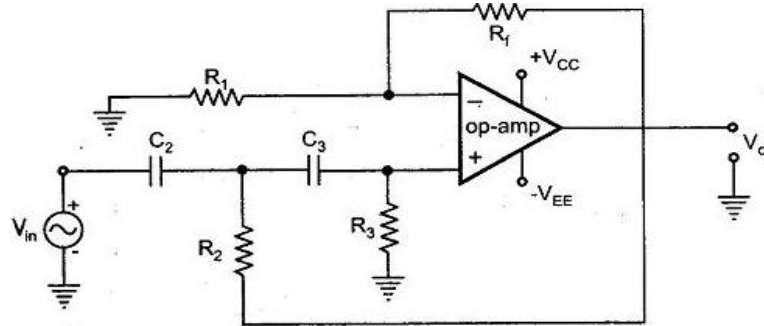


Fig: Second order butterworth high pass filter

02M

d) **Draw I to V converter using OP-AMP. Also derive its output expression.**

Ans:

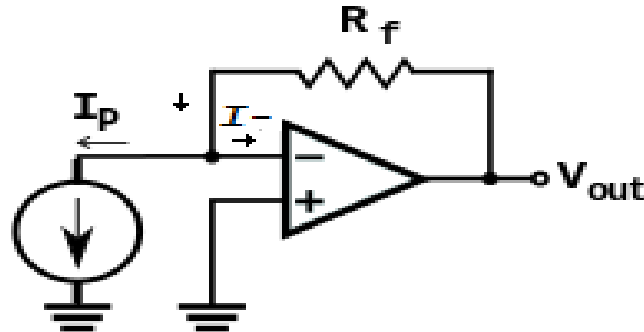


Fig: I to V converter using OP-AMP



A current to voltage converter will produce a voltage proportional to the given current. This circuit is required if your measuring instrument is capable only of measuring voltages and you need to measure the current output. If your instrument or data acquisition module (DAQ) has an input impedance that is several orders larger than the converting resistor, a simple resistor circuit can be used to do the conversion. However, if the input impedance of your instrument is low compared to the converting resistor then the following opamp circuit should be used.

To analyse the current to voltage converter by inspection,

- if we apply KCL to the node at V- (the inverting input) and let the input current to the inverting input be I-, then
 $V_{out} - V - R_f = I_p + I^- \quad (1) \quad V_{out} - V - R_f = I_p + I^-$
- since the output is connected to V- through R_f, the opamp is in a negative feedback configuration. Thus
 $V^- = V^+ = 0 \quad (2) \quad V^- = V^+ = 0$
- and assuming that I- is 0 and simplifying,
 $V_{out} = I_p R_f \quad (3)$


02M

02M

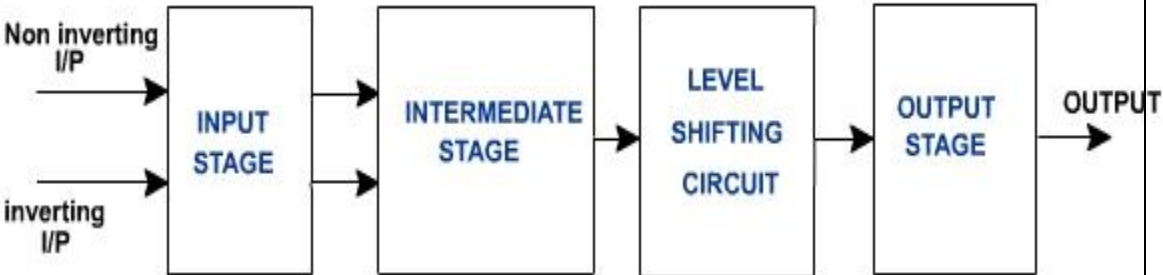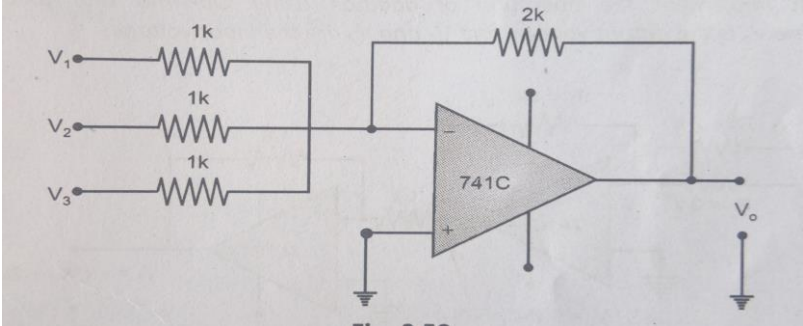3.	<p>Attempt any THREE of the following:</p>	12 M
a)	<p>Draw block diagram of OP-AMP. State function of level shifter and output stage. Ans:</p>  <p>Fig: The block diagram of OP-AMP</p> <p>Level shifting stage is used to bring the dc level to zero volts w.r.t. ground. Op-amp is a direct coupled amplifier, So when input is zero or at ground potential ,the output of op-amp will be at some positive DC level which is an error voltage called as offset voltage . So in order to pull this o/p DC offset voltage to zero, the DC level shifter is used. The output stage increases the output voltage swing and raises the current supplying capability of the OPAMP. It also provides low output resistance.</p>	<p>02M</p> <p>02M</p>
b)	<p>For the given circuit, obtain output equation V₀. (Refer Fig. No. 2)</p>  <p>Fig. No. 2</p> <p>Ans:</p> <p>In the circuit, the input signals V_a, V_b, V_c are applied to the inverting input of the opamp through input resistors R_a, R_b, R_c. Any number of input signals can be applied to the inverting input in the above manner. R_f is the feedback resistor. R_a=1kΩ, R_b=1kΩ, R_c=1k Ω and R_f=1kΩ R_a = R_b = R_c = R</p> <div style="background-color: #e0e0e0; padding: 10px;"> <p>Solution: For inverting adder: $V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$</p> <p>$R_1 = R_2 = R_3 = R$</p> <p>$V_o = \frac{R_f}{R} (V_1 + V_2 + V_3) = \frac{2k}{1k} (V_1 + V_2 + V_3) = -2(V_1 + V_2 + V_3)$</p> </div>	<p>02M</p> <p>02M</p>
c)	<p>Draw and explain the working principle of wein bridge oscillator using IC 741. Ans:</p> <p>When bridge oscillator is an audio frequency sine wave oscillator of high stability and simplicity. Before that let us see what is oscillator? An oscillator is a circuit that produces periodic electric signals such as sine wave or square wave. The</p>	

application of oscillator includes sine wave generator, local oscillator for synchronous receivers etc. Here we are discussing wein bridge oscillator using 741 op amp IC. It is a low frequency oscillator. The op-amp used in this oscillator circuit is working as non-inverting amplifier mode. Here the feedback network need not provide any phase shift. The circuit can be viewed as a wien bridge with a series RC network in one arm and parallel RC network in the adjoining arm. Resistors R_i and R_f are connected in the remaining two arm.


02M

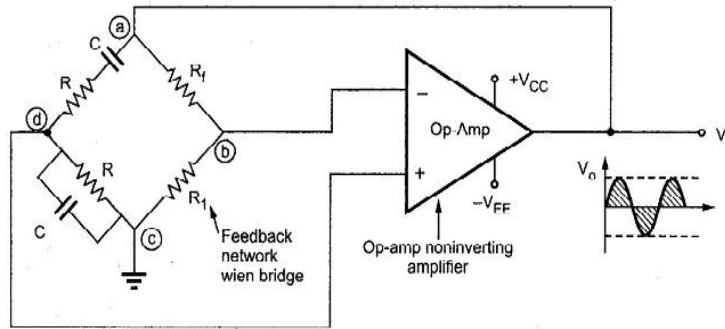

02M


Fig: Wein bridge oscillator using IC 741

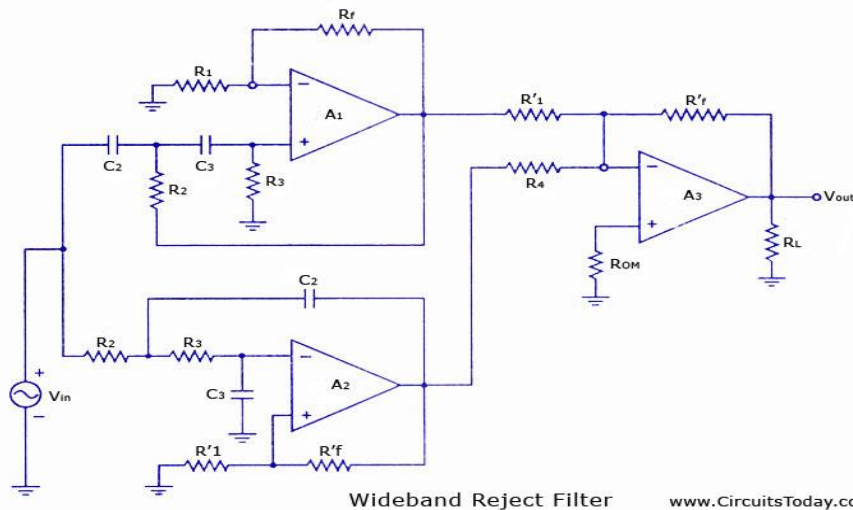d) Draw the labeled circuit diagram of Band reject filter. Also sketch its frequency response for ± 20 dB/decade roll off rate.
Ans:





02M

Fig: Circuit diagram of band reject filter

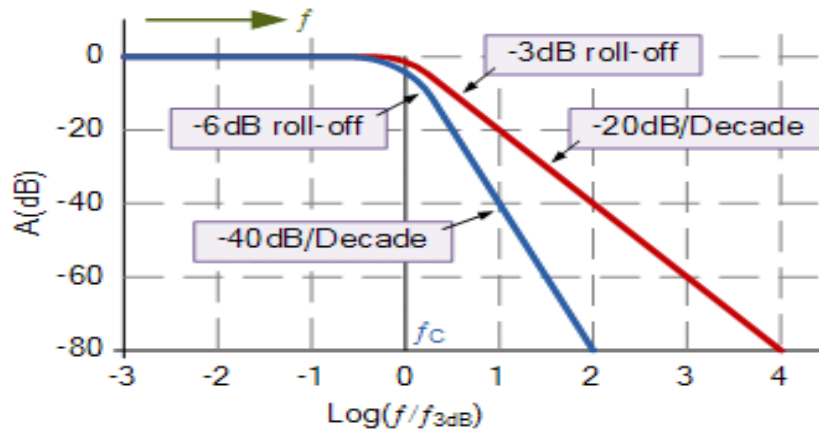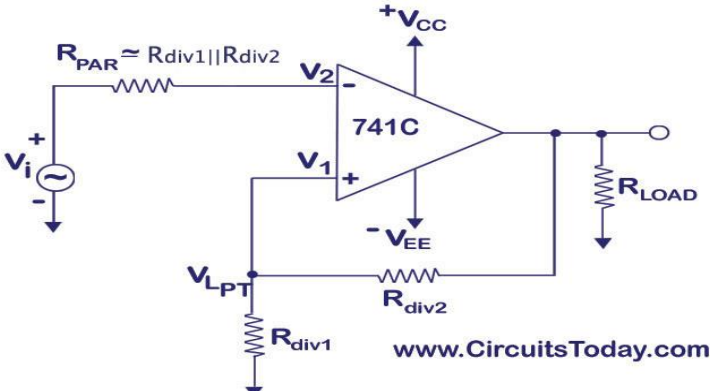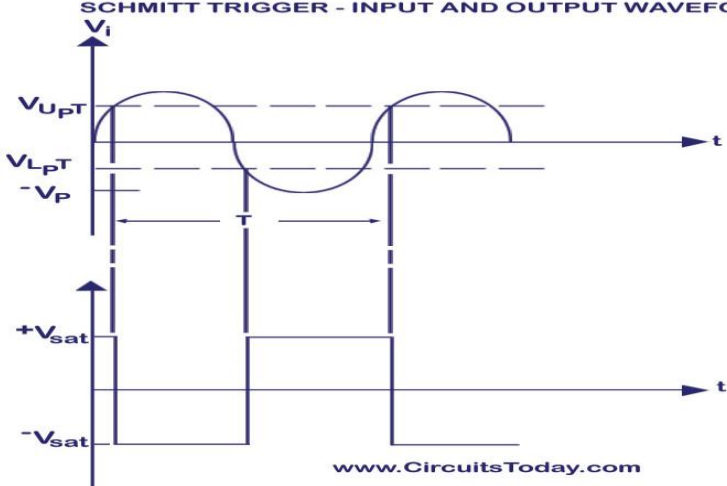

02M

Fig: Frequency response for ± 20 db/decade roll off rate.

4.	Attempt any THREE of the following:	12 M
	<p>a) Draw the circuit diagram of Schmitt trigger using OP-AMP. Describe its working with input and output waveforms. Ans:</p> <p style="text-align: center;">SCHMITT TRIGGER USING OP - AMP 741C</p>  <p style="text-align: center;">Fig: Circuit diagram of Schmitt trigger using OP-AMP</p> <p>As shown in the circuit diagram, a voltage divider with resistors Rdiv1 and Rdiv2 is set in the positive feedback of the 741 IC op-amp. The same values of Rdiv1 and Rdiv2 are used to get the resistance value $R_{par} = R_{div1} R_{div2}$ which is connected in series with the input voltage. Rpar is used to minimize the offset problems. The voltage across R1 is feedback to the non-inverting input. The input voltage Vi triggers or changes the state of output Vout every time it exceeds its voltage levels above a certain threshold value called Upper Threshold Voltage (Vupt) and Lower Threshold Voltage (Vlpt).</p> <p style="text-align: center;">SCHMITT TRIGGER - INPUT AND OUTPUT WAVEFORM</p>  <p style="text-align: center;">Fig: Input and output waveform.</p>	<p style="text-align: right;">02M</p> <p style="text-align: right;">01M</p> <p style="text-align: right;">01M</p>
	<p>b) Draw the OP-AMP based circuit diagram to provide output V0 = 5V, if Vin = -1V applied. Ans:</p> <p>The OP-AMP based circuit diagram to provide output V0 = 5V, if Vin = -1V applied is known as Inverting circuit.</p>	02M

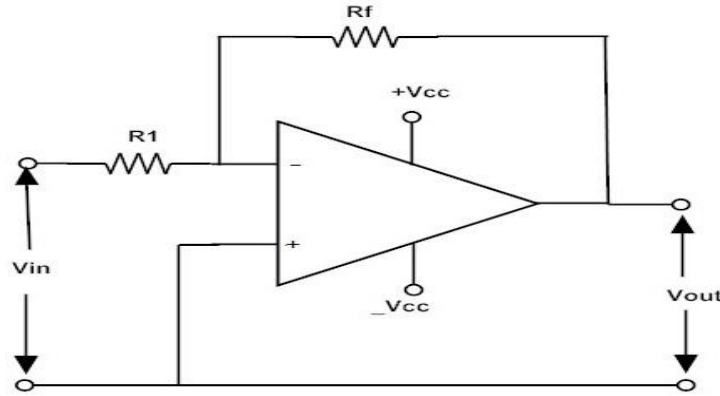


Fig: OP-AMP based circuit diagram

02M

c) Suggest the OP-AMP based circuit to perform below operation (Refer Fig. No. 3)

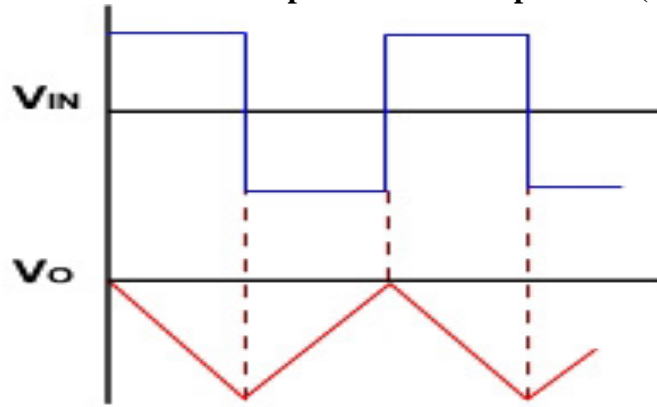


Fig. No. 3

Ans:

Integrator circuit:

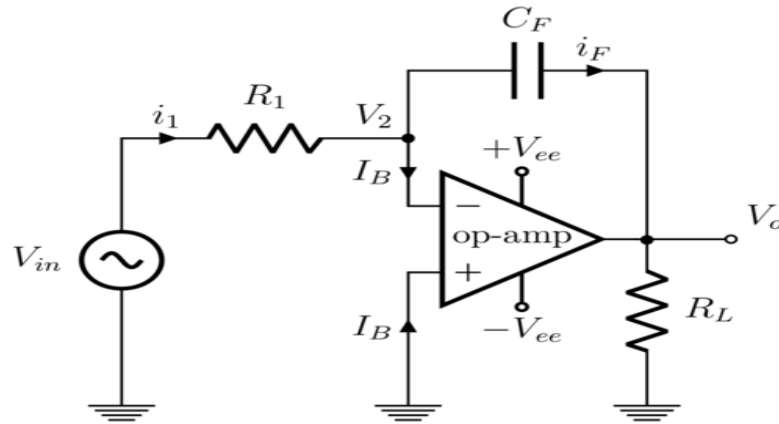



Fig: Integrator circuit

The integrator circuit outputs the integral of the input signal over a frequency range based on the circuit time constant and the bandwidth of the amplifier. The input signal is applied to the inverting input so the output is inverted relative to the polarity of the input signal. The ideal integrator circuit will saturate to the supply rails depending on the polarity of the input offset voltage and requires the addition of a feedback resistor, R2, to provide a stable DC operating point. The feedback resistor limits the lower frequency range over which the integration function is performed. This circuit is most commonly used as part of a larger feedback/servo loop which provides the DC feedback path, thus removing the requirement for a feedback resistor

The formula for determining voltage output for the integrator is as follows:

01M

02M

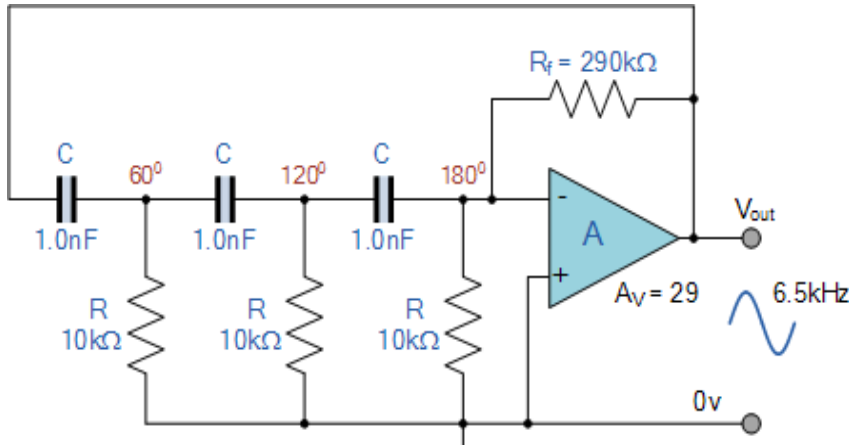	$\frac{dv_{out}}{dt} = - \frac{V_{in}}{RC}$ <p style="text-align: center;">or</p> $V_{out} = \int_0^t \frac{V_{in}}{RC} dt + c$ <p style="text-align: center;">Where, c = Output voltage at start time (t=0)</p>	01M
	<p>d) Define i) Roll off rate of filter ii) Cut off frequency of filter iii) Q factor of filter iv) Bandwidth of filter.</p> <p>Ans:</p> <p>i) Roll-off rate of filter: The gain falls off rapidly in the stop band. The rate at which it falls off is called as the roll-off rate. The roll-off rate is decided by order of filter.</p> <p>ii) Order of filter: The high pass & low pass filters the term pole and order will have the same meaning. That means the no. Of poles will equal to the filter order.</p> <p>iii) Q factor of filter : It is a dimensionless parameter that describes how underdamped an oscillator or resonator is,^[1] and characterizes a resonator's bandwidth relative to its centre frequency</p> <p>iv) Bandwidth of filter : Bandwidth is the difference between the upper and lower frequencies in a continuous band of baseband bandwidth applies to a low-pass filter or baseband signal.</p>	01M Each
	<p>e) Draw and describe the circuit diagram of RC phase shift oscillator using IC 741.</p> <p>Ans:</p>  <p style="text-align: center;">Fig: Circuit diagram of RC phase shift oscillator using IC 741</p> <p>In the amplifier tutorials we saw that a single stage transistor amplifier can produce 180° of phase shift between its output and input signals when connected in a class-A type configuration. For an oscillator to sustain oscillations indefinitely, sufficient feedback of the correct phase, that is “Positive Feedback” must be provided along with the transistor amplifier being used acting as an inverting stage to achieve this. In an RC Oscillator circuit the input is shifted 180° through the amplifier stage and 180° again through a second inverting stage giving us “180° + 180° = 360°” of phase shift which is effectively the same as 0° thereby giving us the required positive feedback. In other words, the phase shift of the feedback loop should be “0”. In a Resistance-Capacitance Oscillator or simply an RC Oscillator, we make use of the fact that a phase shift occurs between the input to a RC network and the output from the same network by using RC elements in the feedback branch.</p>	02M 02M

<p>5.</p>	<p>Attempt any <u>TWO</u> of the following:</p>	<p>12 M</p>
	<p>a) State the need of differential amplifier in OP-AMP. Draw dual input unbalanced output differential amplifier. Ans: It is basically used as a building block of an operational amplifier which is called as operational amplifier (op-amp). The main function of the differential amplifier is, it amplifies the changes between two i/p voltages. But, conquers any voltage common to the two i/ps. This article gives an overview of differential amplifier along with its mathematical expressions.</p> <div data-bbox="565 537 1127 905" data-label="Diagram"> </div> <p align="center">Fig: Differential amplifier in OP-AMP</p>	<p>03M</p> <p>03M</p>
	<p>b) Draw and explain block diagram of IC 555. Draw pin configuration of IC 555. Ans:</p> <div data-bbox="427 1014 1252 1486" data-label="Diagram"> <p align="center">555 IC Timer Block Diagram</p> </div> <p align="center">Fig: Block diagram of IC 555</p> <p>The block diagram of a 555 timer is shown in the above figure. A 555 timer has two comparators, which are basically 2 op-amps), an R-S flip-flop, two transistors and a resistive network. Resistive network consists of three equal resistors and acts as a voltage divider. Comparator 1 compares threshold voltage with a reference voltage + 2/3 V_{CC} volts. Comparator 2 compares the trigger voltage with a reference voltage + 1/3 V_{CC} volts. Output of both the comparators is supplied to the flip-flop. Flip-flop assumes its state according to the output of the two comparators. One of the two transistors is a discharge transistor of which collector is connected to pin 7. This transistor saturates or cuts-off according to the output state of the flip-flop. The saturated transistor provides a discharge path to a capacitor connected externally. Base of another transistor is connected to a reset terminal. A pulse applied to this terminal resets the whole timer irrespective of any input.</p>	<p>02M</p> <p>02M</p>

	<p style="text-align: center;">555 TIMER IC</p> <div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>Top View Of Metal Can Package</p> </div> <div style="text-align: center;"> <p>8-Pin DIP <small>www.CircuitsToday.com</small></p> </div> </div>	02M
--	--	------------

Fig: Pin configuration of IC 555

<p>c)</p>	<p>Draw and explain differentiator using IC 741. State its output expression.</p> <p>Ans:</p> <div style="text-align: center;"> </div> <p style="text-align: center;">Fig: Differential amplifier using IC 741</p> <p>All operational amplifiers (op-amps) are differential amplifiers because of their input configuration. When the first voltage signal is connected to the input terminal and another voltage signal is connected onto the opposite input terminal then the resultant output voltage are proportional to the difference between the two input voltage signals of V_1 and V_2. The output voltage can be solved by connecting each i/p intern to 0v ground using super position theorem.</p>	03M
-----------	---	------------

Fig: Differential amplifier using IC 741

6.	<p>Attempt any <u>TWO</u> of the following:</p>	12 M
-----------	--	-------------

<p>a)</p>	<p>Draw circuit diagram of instrumentation amplifier using 3 op-amps and state its output voltage expression.</p> <p>Ans:</p> <div style="text-align: center;"> </div> <p style="text-align: center;"><small>Figure 1 : Circuit diagram of Instrumentation Amplifier</small></p> <p style="text-align: center;">Fig: Instrumentation amplifier using 3 OP-AMP</p> <p>A circuit providing an output based on the difference between two inputs (times a scale factor) is given in the above figure. In the circuit diagram, opamps labelled A_1 and A_2 are the input buffers. Anyway the gain of these buffer stages are not unity because of the presence of R_1 and R_g. Op amp labelled A_3 is wired as a standard differential amplifier. R_3 connected from the output of A_3 to its non inverting input is the feedback resistor. R_2 is the input resistor. The voltage gain of the instrumentation amplifier can be expressed by using the equation below.</p>	03M
-----------	--	------------



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION

(Autonomous)

(ISO/IEC - 27001 - 2005 Certified)

	<p>Voltage gain (A_v) = $V_o/(V_2-V_1) = (1 + 2R_1/R_g) \times R_3/R_2$ If need a setup for varying the gain, replace R_g with a suitable potentiometer. Instrumentation amplifiers are generally used in situations where high sensitivity, accuracy and stability are required. Instrumentation amplifiers can be also made using two opamps, but they are rarely used and the common practice is to make it using three opamps like what is shown here. The only advantages of making an instrumentation amplifier using 2 opamps are low cost and improved CMRR. A high gain accuracy can be achieved by using precision metal film resistors for all the resistances. Because of large negative feedback employed, the amplifier has good linearity, typically about 0.01% for a gain less than 10. The output impedance is also low, being in the range of milli-ohms. The input bias current of the instrumentation amplifier is determined by the op-amps A1 and A2. A simplified instrumentation amplifier design is shown below. Here the resistances labelled R_1 are shorted and R_g is removed. This results in a full series negative feedback path and the gain of A1 and A2 will be unity. The removal of R_1 and R_g simplifies the equation to $A_v = R_3/R_2$.</p>	03M																											
b)	<p>Compare open loop and closed loop configuration of OP-AMP (6 points) Ans:</p> <table border="1" data-bbox="284 835 1377 1297"> <thead> <tr> <th>parametres</th> <th>Open loop</th> <th>Closed loop</th> </tr> </thead> <tbody> <tr> <td>1. feedback</td> <td>No feedback is used.</td> <td>Positive or negative feedback is used.</td> </tr> <tr> <td>2. Input resistance</td> <td>Very high</td> <td>Depends on the circuit</td> </tr> <tr> <td>3. Output resistance</td> <td>Low</td> <td>Very low</td> </tr> <tr> <td>4. Bandwidth</td> <td>Bandwidth is low</td> <td>Bandwidth is high</td> </tr> <tr> <td>5. Gain</td> <td>Voltage gain is very high</td> <td>Voltage gain is low as compared to open</td> </tr> <tr> <td>6. Stability</td> <td>Not Stable</td> <td>More stable</td> </tr> <tr> <td>7. Effect of noise</td> <td>More</td> <td>Less</td> </tr> <tr> <td>8. Application</td> <td>Comparator ,zero crossing detector</td> <td>It is used in linear amplifier, oscillator</td> </tr> </tbody> </table> <p style="text-align: center;">Table: Compare open loop and closed loop configuration of OP-AMP</p>	parametres	Open loop	Closed loop	1. feedback	No feedback is used.	Positive or negative feedback is used.	2. Input resistance	Very high	Depends on the circuit	3. Output resistance	Low	Very low	4. Bandwidth	Bandwidth is low	Bandwidth is high	5. Gain	Voltage gain is very high	Voltage gain is low as compared to open	6. Stability	Not Stable	More stable	7. Effect of noise	More	Less	8. Application	Comparator ,zero crossing detector	It is used in linear amplifier, oscillator	01M Each point
parametres	Open loop	Closed loop																											
1. feedback	No feedback is used.	Positive or negative feedback is used.																											
2. Input resistance	Very high	Depends on the circuit																											
3. Output resistance	Low	Very low																											
4. Bandwidth	Bandwidth is low	Bandwidth is high																											
5. Gain	Voltage gain is very high	Voltage gain is low as compared to open																											
6. Stability	Not Stable	More stable																											
7. Effect of noise	More	Less																											
8. Application	Comparator ,zero crossing detector	It is used in linear amplifier, oscillator																											
c)	<p>Advantages of active filter over passive filter (any six). Ans: Active filters have three main advantages over passive filters:</p> <ul style="list-style-type: none"> • Inductors can be avoided. Passive filters without inductors cannot obtain a high Q (low damping), but with them are often large and expensive (at low frequencies), may have significant internal resistance, and may pick up surrounding electromagnetic signals. • The shape of the response, the Q (Quality factor), and the tuned frequency can often be set easily by varying resistors, in some filters one parameter can be adjusted without affecting the others. Variable inductances for low frequency filters are not practical. • The amplifier powering the filter can be used to buffer the filter from the electronic components it drives or is fed from, variations in which could otherwise significantly affect the shape of the frequency response. 	02M Each point																											