

17424

21819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each Section on separate answer sheet.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

SECTION - I

- 1. Attempt any NINE of the following:** **18**
- a) State Ohm's law.
 - b) How many 60 W lamps may be safely connected to 240 V circuits fitted with 5 A fuse?
 - c) Define energy and power.
 - d) State necessity of fuse.
 - e) What is earthing?
 - f) Mention types of earthing.
 - g) Why is earthing necessary in a wiring installation?

P.T.O.

- h) Define transformer.
- i) Describe the winding of transformer with function and their material used for a transformer.
- j) Which type of transformer has no electrical isolations?
- k) Define voltage ratio and transformation ratio.
- l) Write two safety precautions to be taken while handling an electrical equipments.

2. Attempt any FOUR of the following: 16

- a) Differentiate between two winding transformer and auto transformer on any four points.
- b) Define fuse. Also explain the working of HRC fuse in brief.
- c) Compare single phase with three phase ac supply.
- d) State the function of “no volt coil” and “overload coil” in case of oc shunt motor starter.
- e) Draw a neat diagram of resistance split phase induction motor. State any two applications.
- f) Compare squirrel cage and slip ring type three phase inductions motor.

3. Attempt any FOUR of the following: 16

- a) What is the importance of improvement in power factors? State any two methods for power factor improvements.
- b) List the different parts of DC machine. State function of any two parts.
- c) State the necessity of starter for dc motor. Also give two applications of dc series motor and dc shunt motor.
- d) With connection diagram, explain working principle of capacitor start capacitor run single phase induction motor.
- e) Compare core-type and shell-type transformer by four points.
- f) Draw the wiring diagram of stair case wiring and explain its working.

SECTION - II

- 4. Attempt any NINE of the following:** **18**
- a) Define resistor and inductor with their symbols.
 - b) Define intrinsic and extrinsic semiconductor.
 - c) List the applications of TRIAC.
 - d) Draw the VI characteristics of PN junction diode and zener diode.
 - e) Draw the symbol of NPN and PNP transistor.
 - f) List the application of transistor.
 - g) Draw the block diagram of rectifier.
 - h) What is the need of filter?
 - i) Draw the symbol of AND and OR gate with their truth table.
 - j) Why NAND and NOR called as universal gates?
 - k) List the types of LED and LCD display.
 - l) What is the concept of power amplifier?
- 5. Attempt any FOUR of the following:** **16**
- a) Draw construction and explain working of PN junction diode in forward bias.
 - b) Draw construction and explain working of light emitting diode.
 - c) Describe De-Morgan's theorems.
 - d) Draw circuit diagram of full wave bridge rectifier. Explain working with their input and output wave forms.
 - e) Explain the working of single stage CE amplifier with the help of neat circuit diagram.
 - f) Describe the working of TRIAC with the help of a neat sketch. Also state its two applications.

6. Attempt any FOUR of the following:**16**

- a) Describe the working principle of zener diode as a shunt regulator with the help of neat circuit diagram.
 - b) Draw the V-I characteristics of SCR. Explain different modes of operation of SCR.
 - c) Describe the working of NPN transistor, with the help of neat sketch.
 - d) Describe the working of series inductor filter with the help of neat sketch.
 - e) Draw and explain zener as a voltage regulator.
 - f) Draw all basic gates using NOR gate.
-