

17510

21819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--


- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

	Marks
1. (A) Attempt any THREE :	12
(a) Draw neat labelled diagram showing basic structure of power system.	
(b) State the expression for real and reactive power for sending end.	
(c) Compare ac resistance with dc resistance.	
(d) 3 φ transmission line has impedance $(10 + j30)\Omega/\text{ph}$ and admittance of $j2.827 \times 10^{-4} \text{ S}/\text{ph}$. Calculate GCC using π method.	
(B) Attempt any ONE :	6
(a) Balanced 3 φ load of 30 MW is supplied at 132 kV, 50 Hz, 0.8 lag p.f. $Z = (20 + j52)\Omega/\text{ph}$ and $Y = 315 \times 10^{-6} \text{ S}/\text{ph}$. Use nominal J method and calculate ABCD constants, sending end voltage and % regulation.	
(b) Explain self GMD and mutual GMD with the help of example.	

2. Attempt any TWO :

16

- (a) (i) Define generalised circuit constants.
(ii) Derive the condition for maximum power at receiving end.
- (b) Determine inductance of 1ϕ transmission line for arrangement shown in fig. 1.
Diameter of conductor is 1 cm.

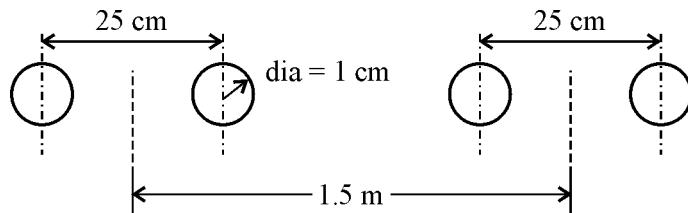
**Fig. 1**

- (c) A 3ϕ line has parameters $A = D = 0.9 \angle 0.4$, $B = 99 \angle 76.86$ V_S and V_R are maintained at 220 kV. Calculate maximum power supplied at sending end.

3. Attempt any FOUR :

16

- (a) Draw equivalent circuit for alternator and medium transmission line T model.
(b) State the advantages of circle diagram.
(c) Calculate self GMD for fig. 2.

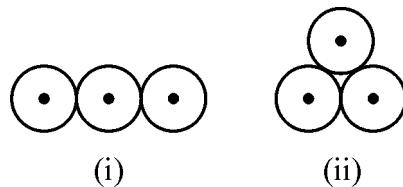
**Fig. 2**

- (d) Explain step-by-step procedure for drawing receiving end circle diagram.
(e) Determine capacitance of 3ϕ line with conductors mounted at corners of triangle with 3 m side. Diameter of conductor is 0.8 cm

4. (A) Attempt any THREE :

12

- (a) Define transposition. State its necessity. List out advantages of transposition.
- (b) A 3 pH, 132 KV, transmission line delivers 40 mVA at 0.8 pf lag. Draw circle diagram and determine sending end voltage if $A = 0.98\angle 3^\circ$, $B = 110\angle 72^\circ$.
- (c) Draw reactance diagram for given power system as shown fig. 3 considering generator as base.

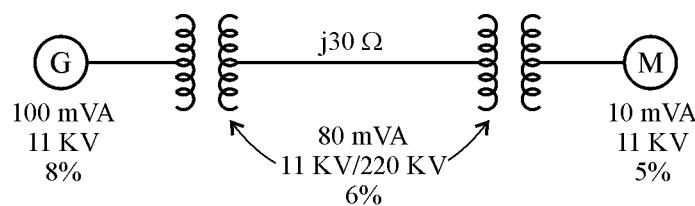**Fig. 3**

- (d) Give the expression for complex power at receiving end. State the equation of real power and reactive power.

(B) Attempt any ONE :

6

- (a) Prove that $AD - BC = 1$.
- (b) Derive the equation for inductance of 3φ line with conductors mounted at corners of triangle with unsymmetrical spacing.

5. Attempt any TWO :

16

- (a) A 275 KV transmission line has following GCC, $A = 0.85\angle 75^\circ$, $B = 300\angle 75^\circ$, determine power at unity pf that can be received if voltage at each end is maintained at 275 KV.

P.T.O.

- (b) Explain the necessity of reactive power compensation. List out the equipments used for reactive power compensation and state its field of application.
- (c) A 1 ϕ line with solid conductor of 10 mm dia. and spacing between conductor is 4 m. Calculate inductance and capacitance.

6. Attempt any FOUR :**16**

- (a) Explain step-by-step procedure for sending end circle diagram.
- (b) List out the role of power system engineer.
- (c) State the significance of inductance and capacitance.
- (d) 3 ϕ transmission line has constants A & B as $0.9\angle i$ & $100\angle 85\Omega/\text{ph}$ respectively. Calculate receiving end complex power if voltage is maintained at 200 KV at both end with load angle 8° .
- (e) 3 ϕ , 400 KV, 500 km transmission line has parameters as

$$R = 0.025 \Omega/\text{km/ph}$$

$$\text{Inductance} = 1 \text{ mH/km/ph}$$

$$\text{Capacitance} = 0.020 \mu\text{F/km/ph}$$

Calculate AB CD parameters for nominal T method.
