

# 17638

**21819**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. a) **Attempt any THREE of the following:** **12**
- (i) State the meaning of holding current and latching current. Label them on the VI characteristics of SCR.
- (ii) Draw circuit diagram of single phase full bridge inverter. Draw waveform of load voltage and load current for RL load.
- (iii) State the necessity of converter and give the classifications of controlled converter.
- (iv) Draw a schematic of step up chopper and explain it.
- b) **Attempt any ONE of the following:** **6**
- (i) Discuss the method of overcoming the intermittent power flow in a basic series inverter. Illustrate your answer with relevant circuit and waveform.

P.T.O.

- (ii) For a single phase full controlled half wave converter system and sketch waveforms for load voltage and load current for:
- 1) RL load
  - 2) RL load with free wheeling diode from a comparison of these waveforms. Discuss the advantages of using a free wheeling diode.

**2. Attempt any FOUR of the following: 16**

- a) Describe thyristorised induction heating.
- b) Draw symbol and V-I characteristics for:
  - (i) TRIAC
  - (ii) IGBT
- c) Draw circuit diagram of  $3\phi$  series inverter and describe its operation.
- d) With a neat circuit diagram, explain the working principle of Jones Chopper.
- e) Explain the operation of cyclo converter with a neat diagram.
- f) State differences between MOSFET and thyristor inverter.

**3. Attempt any FOUR of the following: 16**

- a) Draw schematic circuit diagram of thyristorized battery charges.
- b) Draw construction of SCR using two transistor model. Explain its operation.
- c) State the application of chopper and list the various control techniques of Chopper.
- d) What is converter? List the types of converter. State the function of free wheeling diode in converters.
- e) Describe the working of resistance welding method with diagram.
- f) Sketch output voltage output current source current and thyristor current waveform for type C chopper indicate the conduction of various devices.

4. a) **Attempt any THREE of the following:** **12**
- i) Describe the principle of dielectric heating. Give any two applications.
  - ii) State different methods to control the output voltage of inverter. Explain PWM method.
  - iii) Differentiate between single and three phase controlled converter on the basis of efficiency, ripple factor RMS values and average values.
  - iv) Draw the circuit diagram and explain the variable frequency control of induction motor.
- b) **Attempt any ONE of the following:** **6**
- i) Describe operation of  $3\phi$  full controlled bridge converter with R load using neat circuit diagram. Sketch different i/p, o/p waveform.
  - ii) Sketch circuit diagram of auxiliary commutated chopper. Explain its operation using related waveform.
5. **Attempt any FOUR of the following:** **16**
- a) What are different turn-on methods of SCR? Explain any one method.
  - b) State the criteria for selection of single phase and three-phase inverter for required application.
  - c) Describe the circuit diagram and operation of DC static circuit breaker.
  - d) Describe use of thyristor in static VAR compensation.
  - e) Explain the SCR turn off process with waveforms of voltage and current.
  - f) Draw symbol and characteristics of GTO, LASCR, power semiconductor and its application.

**6. Attempt any FOUR of the following:****16**

- a) Describe the working of close loop speed control method for A.C. series motor and D.C series motor.
  - b) Write the specifications/rating of SCR:
    - (i) Voltage.
    - (ii) Current
    - (iii) Power
    - (iv) Temperature.
  - c) Draw circuit for single phase full wave converter with RL load and draw its load voltage and current waveform.
  - d) Draw and describe the operation of parallel inverter.
  - e) State the meaning of commutation. Explain class B method of commutation.
  - f) Discuss the working of a load commutated chopper with relevant voltage and current waveforms.
-