

22221

21819

3 Hours / 70 Marks

Seat No.

| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|
| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Define the term 'Magnetomotive force' and 'permeability' related to magnetic circuits.
- (b) Draw sinusoidal AC waveform and show the Amplitude and Time period on it.
- (c) An inductive coil takes 10 A when connected to 250 V; 50 Hz mains. The power consumed is 1 kilowatt. Find power factor and reactive power.
- (d) Explain balanced load and unbalanced load in 3-phase system.
- (e) Draw schematic diagram of D.C. shunt motor and D.C. series motor. State the meaning of terminal marking on it.
- (f) State at least two applications of :
 - (i) Brushless D.C. motor
 - (ii) Servo motor
- (g) State the function of MCB and ELCB in Electrical Installation System.

[1 of 4]

P.T.O.

2. Attempt any THREE of the following :

12

- Explain Faraday's laws of electromagnetic induction. Explain how can the direction of induced emf be found.
- Calculate the impedance; current; active power and power factor for a series circuit having a resistance of 10Ω and capacitance of $100 \mu\text{F}$ fed from single phase, 200 V ; 50 Hz A.C. supply.
- Describe an autotransformer. Explain the advantages and disadvantages of autotransformer as compared to a two winding transformer.
- Describe the principle of working of three phase induction motor. How the direction of rotation of 3-phase induction motor can be obtained ?

3. Attempt any THREE of the following :

12

- Find the currents in each branch of circuit shown in Fig. 3(a) using mesh analysis.

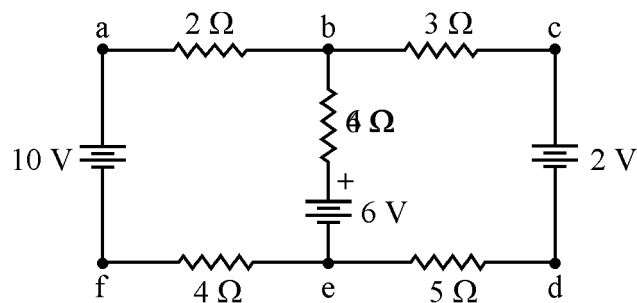


Fig. - 3(a)

- A load consisting of three identical impedances of $10 \angle -45^\circ \Omega$ connected in Delta is fed from a 220 V ; 3-phase source. Find
 - Magnitude of phase and line currents.
 - Total power supplied to the load.
- Compare squirrel cage 3-phase induction motor with slip ring 3-phase induction motor. (four points)
- State the various types of earthing and explain any one type with its neat sketch.

4. Attempt any THREE of the following :**12**

- (a) Define Dynamically induced emf and statically induced emf. Differentiate between them.
- (b) State the various speed control methods of D.C. shunt motor. Explain any one method with circuit diagram.
- (c) Explain necessity of starter for three phase induction motor. State various types of starter used for 3-phase induction motor.
- (d) Describe the maintenance procedure of the fractional Horse Power Motors.

5. Attempt any TWO of the following :**12**

- (a) A metal-filament lamp rated at 750 watt; 100 V is to be used on a 230 V; 50 Hz supply; by connecting a capacitor of suitable value in series. Determine :
 - (i) The capacitance required in μF
 - (ii) The phase angle
 - (iii) The power factor and its nature
 - (iv) Apparent power
 - (v) Reactive power
 - (vi) Draw phasor diagram for the same
- (b) Derive the emf equation of transformer. Write the equation for transformation ratio. State the value of transformation ratio for step down and step up transformer.
- (c) Explain with neat sketch; the basic principle of operation; reversal of rotation and applications of universal motor.

P.T.O.

6. Attempt any TWO of the following :**12**

- (a) A coil is connected to a 250 V; 50 Hz A.C. supply. It is found that magnitude and phase angle of current are 10 A and 30° lagging. Find :
- (i) Resistance of coil
 - (ii) Inductance of coil
 - (iii) Active power in the ckt
 - (iv) Reactive power in the ckt
 - (v) Draw impedance triangle of the ckt
 - (vi) Draw power triangle of the ckt.
- (b) List the various types of single phase induction motor. Explain with schematic diagram, the principle of operation and applications of any one type of single phase induction motor.
- (c) (i) State the function of fuses in Electrical circuit. **(2)**
- (ii) What are the various types of fuses ? **(2)**
- (iii) Compare fuse with MCB. **(2)**
-