

22232

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each Section on separate answer sheet.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

**Section – I**

**1. Attempt any SIX of the following :**

**12**

- (a) State Faraday's law of electromagnetic induction.
- (b) Define permeability and reluctance.
- (c) Define phase angle and power factor.
- (d) Define MMF and leakage factor.
- (e) State concept of power triangle.
- (f) Define power & energy.
- (g) Define RMS value & Average value.

**2. Attempt any THREE of the following : 12**

- (a) Define Autotransformer. Explain working of autotransformer.
- (b) Define (i) Self induced emf (ii) mutually induced emf and give their equations.
- (c) Draw and explain series R-L-C circuit.
- (d) State different methods for starting of induction motor. Explain any one method.
- (e) Compare autotransformer and 1- $\phi$  two-winding transformer.

**3. Attempt any TWO of the following : 12**

- (a) Explain construction and working principle of single phase ac motor. Give emf equation of single phase ac motor.
- (b) State various types of FHP motors. Explain the construction of any one FHP motor.
- (c) Given a sinusoidal voltage equation,  $v = 169.8 \sin 377 t$   
Find
  - (i) Maximum voltage
  - (ii) Frequency
  - (iii) Time period
  - (iv) RMS voltage
  - (v) Average voltage
  - (vi) Angular velocity

**Section – II****4. Attempt any FIVE of the following : 10**

- (a) Compare analog and digital IC. (any 2 points)
- (b) Draw the symbol of (i) Zener diode (ii) LED.
- (c) State the need of filters.
- (d) Define (i) PIV (ii) Ripple factor.
- (e) List different types of Signals.
- (f) Give applications of capacitors.

**5. Attempt any THREE of the following :****12**

- (a) Draw and explain ideal current source.
- (b) Explain working of half-wave rectifier and draw its waveforms.
- (c) Explain cut-off region, saturation region and active region in characteristics of transistors.
- (d) Explain CE configuration of transistors with input and output characteristics.
- (e) Explain Zener diode as a voltage regulator.

**6. Attempt any TWO of the following :****12**

- (a) List types of bipolar devices. Explain transistor as a switch and amplifier.
  - (b) List types of filters. Explain 'C' type of filter.
  - (c) Find the resistor value from the given colour code or vice versa.
    - (i) Red, Red, Red, Gold
    - (ii) Brown, Black, Brown, Silver
    - (iii)  $1\text{M}\Omega \pm 5\%$
-

