

22346

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any FIVE of the following: 10
- a) Draw symbol of :-
- (i) NPN transistor
- (ii) PNP transistor
- b) List various transistor biasing methods.
- c) Draw symbol of :-
- (i) FET-P channel
- (ii) EMOSFET-N channel.
- d) Define collector efficiency of power amplifier.
- e) State Barkhausen criteria for sustained oscillation.
- f) Compare linear and Non-linear wave shaping circuits.  
(Any two points.)
- g) Draw circuit of zener diode as voltage regulator.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Define  $\alpha$ ,  $\beta$  and  $\gamma$  with respect to transistor configuration. State relation between  $\alpha$  and  $\beta$ .
  - b) Draw circuit diagram of FET biasing.
    - (i) Self-bias method
    - (ii) Voltage divider bias.
  - c) Describe FET as an amplifier with circuit diagram.
  - d) Describe UJT as relaxation oscillator with neat circuit diagram.
- 3. Attempt any THREE of the following:** **12**
- a) Draw the circuit diagram of two stages R-C coupled amplifier and describe it's working.
  - b) Draw construction and describe working of N-channel JFET with neat sketch.
  - c) Describe the working of transistorized crystal oscillator with the help of circuit diagram.
  - d) Describe the working of transistor as a switch and give the application of it.
- 4. Attempt any THREE of the following** **12**
- a) Draw the block diagram of DC regulated power supply and describe the working of each block.
  - b) Compare power amplifiers- class A, class B class AB and class C on the basis of:
    - (i) Angle of conduction.
    - (ii) Position of Q point.
    - (iii) Efficiency.
    - (iv) Distortion in output voltage.

- c) Define the terms with respect of JFET.
- (i) Pinch – off voltage
  - (ii) Dc drain resistance.
  - (iii) Transconductance
  - (iv) Amplification factor.
- d) Compare CB, CE, CC on the basis of following points:-
- (i) Input resistance
  - (ii) Output resistance
  - (iii) Current gain
  - (iv) Voltage gain.

**5. Attempt any TWO of the following**

**12**

- a) In common emitter configuration if  $\beta=150$  leakage current  $I_{CEO} = 100\mu\text{A}$  and base current is  $0.5\text{mA}$  determine  $I_C$  and  $I_E$ . Draw CE configuration circuit diagram.
- b) List four applications of wave shaping circuits. Describe the working of RC integrator with neat waveforms.
- c) Build the circuit diagram to get  $+10V_{dc}$  and  $-10V_{dc}$  using IC 7810 and IC 7910 along with rectifier. Calculate load regulation if regulator produces  $10.2\text{ V}$  and  $10\text{ V}$  output at no-load and full-load conditions respectively.

**6. Attempt any TWO of the following:****12**

- a) Single stage class B amplifier is operating with  $1\text{K}\Omega$  load. A dc meter in the collector reads  $10\text{mA}$ . How much signal power is delivered to the load?
  - b) In a single stage voltage amplifier, voltage gain without feedback is 80, input resistance ( $R_i$ ) =  $800\Omega$  and output resistance ( $R_o$ ) is  $8\text{K}\Omega$ . If 20% output voltage is feedback in series with input, determine  $A_{vf}$ ,  $R_{if}$  and  $R_{of}$  of negative feedback amplifier.
  - c) The dc level of  $+3\text{V}$  is to be added to the given input signal ( $V_i = 5 \sin \omega t$ ). Name the circuit required for this and describe the working principle along with circuit diagram and input-output waveforms.
-