

312310

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. Attempt any FIVE of the following :

10

- (a) Define the potential difference. State its unit.
- (b) Define linear and non-linear network.
- (c) State types of battery.
- (d) Define magnetic flux. State its unit.
- (e) Give two types of capacitor and give one example of each.
- (f) Define electromagnetic induction.
- (g) Draw symbol of Alternating current and Direct current.
- (h) Define Internal Voltage Drop.



2. Attempt any THREE of the following :**12**

- (a) State the factors which effect temperature on resistance.
- (b) Three capacitors 1 μF , 2 μF & 4 μF respectively are connected in a circuit. Determine the equivalent capacitance when they are connected in (i) Series (ii) Parallel.
- (c) Draw B-H curve for magnetic and non-magnetic material. Draw Hysteresis loop for hard steel and soft steel.
- (d) State and explain in detail Faraday's laws of Electromagnetic Induction.

3. Attempt any THREE of the following :**12**

- (a) Draw symbol and characteristics of Ideal and Practical voltage source.
- (b) Define :
 - (i) Loop
 - (ii) Mesh
 - (iii) Node
 - (iv) Branch
- (c) Differentiate series magnetic circuit and parallel magnetic circuit.
- (d) Write types of inductors and applications of each.

4. Attempt any THREE of the following :**12**

- (a) A resistance of 50 ohm is connected in parallel with 25 ohm. If current through the combination is 10 Ampere. Calculate current through each resistance.
- (b) Draw a practical set up to plot charging and discharging curves of a capacitor through a resistor. Draw the curves.

312310

[3 of 4]

- (c) Explain in detail (i) Statically induced emf. (ii) Dynamically induced emf.
- (d) Define the terms : (i) MMF (ii) Ampere-Turns (AT) (iii) Reluctance (iv) Permeance.
- (e) Calculate the inductance and energy stored in magnetic field of air cored coil of 300 cm long, 60 cm diameter and wound with 5000 turns and carrying 8 A current.

5. Attempt any TWO of the following :

12

- (a) Discuss in detail the heating effect, magnetic effect and chemical effect of electric current.
- (b) Give any six points of comparison between electric circuit and magnetic circuit.
- (c) Two coils A of 1000 turns and B of 1200 turns are such that 60% flux produced by A links with B. A current of 4 A in coil A produces a flux of 0.05 Wb and in coil B of 0.075 Wb. Find (i) L_1 (ii) L_2 (iii) M (iv) K.

6. Attempt any TWO of the following :

12

- (a) Find the current through $5\ \Omega$ resistor using Kirchhoff's law, (Figure No. 01).

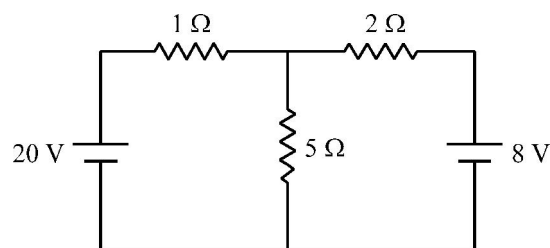


Fig. No. – 1

P.T.O.

312310

[4 of 4]

- (b) Derive the expression for energy stored in capacitor with the help of diagram.
 - (c) Define self-inductance and prove that $L = N^2/S$ where N = Number of turns & S = reluctance & L = self-inductance.
-