

# 313303

**24225**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

- 
- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answer with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following: 10**
- a) Write the base of the following number systems. Decimal, Binary, Octal and Hexadecimal.
  - b) Draw symbol and write the truth table of NAND gate.
  - c) State the necessity of multiplexer.
  - d) Write excitation table of T-Flip-Flop.
  - e) List any four features of SSD memory.
  - f) Design half subtractor circuit.
  - g) State the difference in logic of EX-OR and EX-NOR gate.

P.T.O.

2. Attempt any THREE of the following: 12
- a) Convert the following –
    - i)  $(429)_{10} = (?)_{BCD}$
    - ii)  $(2.45)_{10} = (?)_2$
    - iii)  $(AF)_{16} = (?)_8$
    - iv)  $(1011010)_2 = (?)_{16}$
  - b) State and prove De Morgan's theorems.
  - c) Describe function of full adder circuit with its truth table, K-map simplification and logic diagram.
  - d) What is modulus of counter? Design MOD-7 counter.
3. Attempt any THREE of the following: 12
- a) What is Race around condition? How can it be overcome?
  - b) Realize the logic operations of AND, OR, NOT gates using only NAND gates.
  - c) Design 16:1 multiplexer using 4:1 multiplexers.
  - d) Draw the block diagram and explain the working of successive approximation method of ADC.
4. Attempt any THREE of the following: 12
- a) State Duality theorem. Prove that AND laws and OR laws are dual of each other.
  - b) Give any two specifications of DAC. Draw the circuit diagram of weighted resistor DAC and give the expression for output.
  - c) Draw the logical circuit diagram of BCD to 7-segment decoder and write its truth table.
  - d) Compare weighted resistor DAC and R-2R DAC. (Any four points)
  - e) Minimize the following expression using K-map.  
 $F(A, B, C, D) = \pi (1, 4, 6, 9, 11, 12, 14, 15).$

5. Attempt any TWO of the following: 12
- a) Define SOP form and POS form of Boolean expression. Convert  $F(A, B, C) = \Sigma m(1, 4, 5, 6, 7)$  in standard POS form.
  - b) Design a mod-10 asynchronous counter. Draw the timing diagram.
  - c) Compare combinational and sequential logic circuit. (Any six points)
6. Attempt any TWO of the following: 12
- a) Design 3-bit synchronous counter and draw output waveform.
  - b) Compare the following. (Any three points) –
    - i) Volatile with Non-volatile memory
    - ii) SRAM with DRAM memory.
  - c) Convert the following –
    - i)  $(5C7)_{16} = (?)_{10}$
    - ii)  $(2598)_{10} = (?)_{16}$
    - iii)  $(10110)_2 = (?)_{10} = (?)_{16}$ .
-