

313325

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following:

10

- a) Define –
 - i) Kirchoff's voltage law
 - ii) Kirchoff's current law.
- b) Draw –
 - i) Practical voltage source
 - ii) Ideal current source.
- c) State –
 - i) Maximum Power transfer theorem
 - ii) Reciprocity theorem.

P.T.O.

- d) Write equation for ABCD parameters in terms of voltage and current.
- e) Define and state equations for –
 - i) Active power
 - ii) Reactive power
- f) Draw phasor diagram for RL series circuit. Give equation for resultant impedance.
- g) State condition for resonance in R-L-C series circuit.

2. Attempt any THREE of the following: 12

- a) Define superposition theorem. Write the steps for finding current through an element using super position theorem.
- b) Draw the phasor diagram, impedance triangle and power triangle for series R-L-C circuit for condition $X_L < X_C$.
- c) Derive expression for resonant frequency for series RLC resonant circuit.
- d) Give steps to convert practical voltage source to practical current source.


3. Attempt any THREE of the following: 12

- a) Draw star and delta circuits. Write equation to convert a star circuit to corresponding delta circuit.
- b) State Thevenin's theorem. Give steps to find current through resistance using Thevenin's theorem.
- c) Define low pass filter. Draw its frequency response. Give circuit of RC low pass filter and expression for cut off frequency.
- d) Compare series and parallel resonant circuits on the basis of –
 - i) Resonating frequency
 - ii) Impedance
 - iii) Current
 - iv) Magnification.


4. Attempt any THREE of the following:

12

- a) Using Mesh analysis find current through 4Ω resistance. Refer Figure No. 1.

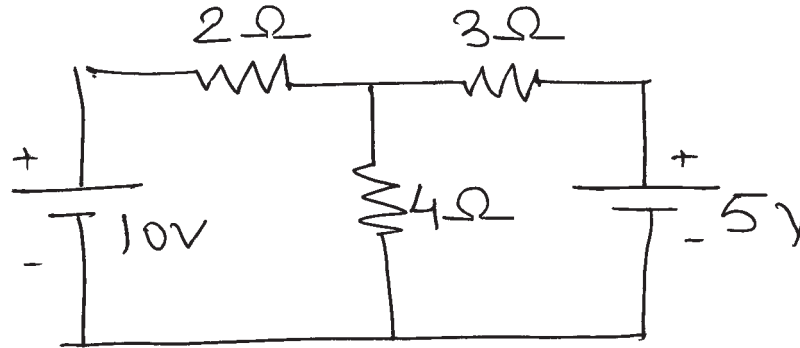Fig. No. 1

- b) Obtain Thevenin's equivalent circuit at A and B for the network shown in Figure No. 2

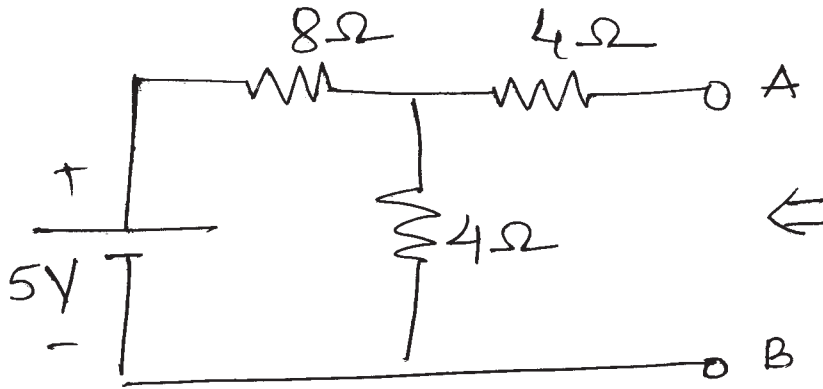Fig. No. 2

- c) Explain Z parameter of two port network in detail.
- d) A coil of resistance 50Ω and inductance 0.1 H are connected in series with $100\mu\text{f}$ capacitor supplied with 230V , 50Hz A.C. supply. Calculate voltage across each and draw complete phasor diagram.

- e) A coil having 10Ω resistance and 0.1H inductance is connected across 230V , 50Hz A.C. supply.

Calculate –

- i) Impedance
- ii) Current
- iii) Power factor
- iv) Power absorbed by the coil.

5. Attempt any TWO of the following:

12

- a) Draw two port network for the following configurations –
- i) Cascade configuration
 - ii) Series configuration
 - iii) Parallel configuration.
- b) Calculate current through 6Ω resistance using Norton's theorem
Refer Figure No. 3.

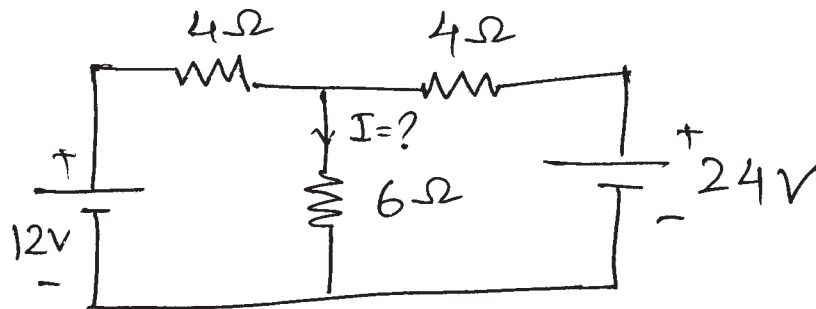


Fig. No. 3

- c) A series RC circuit takes a current of 2.7A when connected 240V , 50Hz A.C. Supply and consumes 350 watts.


Calculate –

- i) Resistance
- ii) Capacitance
- iii) Power factor.


6. Attempt any TWO of the following:

12

- a) For the following circuit; find value of R using NODAL analysis
Refer Figure No. 4

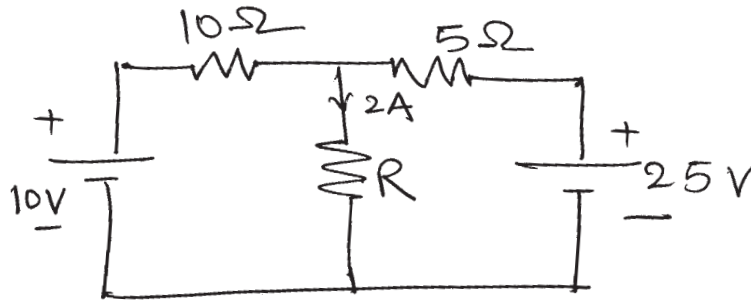Fig. No. 4

- b) Using superposition theorem find current in 3Ω resistor in Figure No. 5. State any two drawbacks of super position theorem.

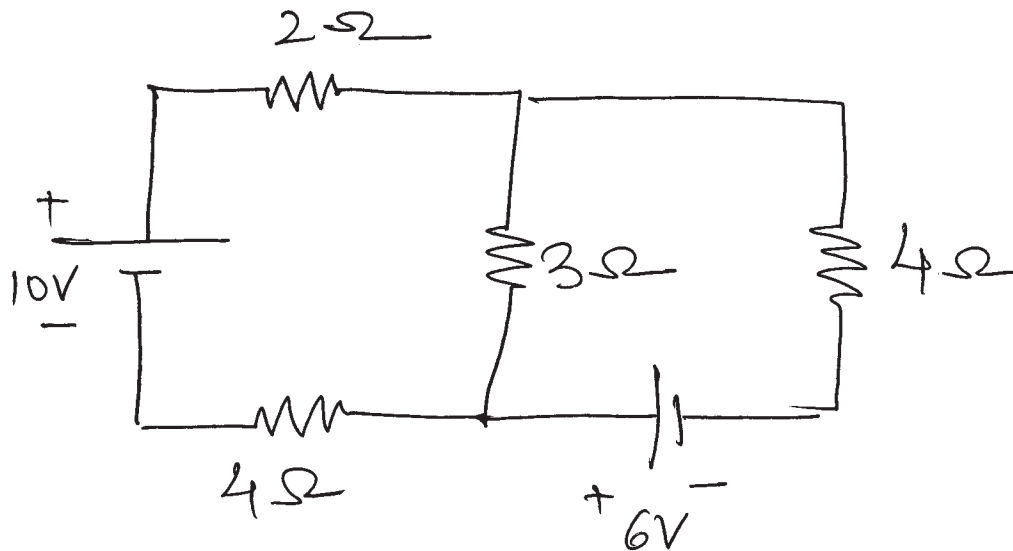Fig. No. 5

- c) A coil of resistance 20Ω and inductance 2000 mH is in parallel with variable capacitor. The voltage of supply is 200V and frequency 10^6Hz .

Calculate –

- Value of C to give resonance
- Q of the coil
- Dynamic resistance of circuit.