

314324

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answers with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. **Attempt any FIVE of the following :** **10**
- a) Convert $(A2F)_{16}$ to Decimal number system.
 - b) For 2 input EX-OR gate –
 - i) Draw symbol
 - ii) Write Truth Table
 - c) State the purpose of the ‘preset’ and ‘clear’ inputs in a flip-flop.
 - d) Define –
 - i) Address Bus
 - ii) Data Bus
 - e) List Four features of microcontroller 8051.

P.T.O.

- f) Identify the direct addressing instruction from the following instructions.
- i) MOV A, #0AFH
 - ii) MOV 0E5H, @RO
 - iii) MOV R2, 45H
 - iv) ADD A,45H
- g) If the starting address of an external 2K RAM is 1000H, Find the ending address write its memory map.

2. Attempt any THREE of the following :

12

- a) Explain half adder using a logical diagram and its truth table.
- b) Implement a full subtractor using a multiplexer and write its truth table.
- c) Compare Harvard and Von - Neumann architecture with respect to –
 - i) memory structure
 - ii) complexity
 - iii) speed of execution
 - iv) examples
- d) Explain the following directives with example –
 - i) ORG
 - ii) DB
 - iii) EQU
 - iv) END

3. Attempt any THREE of the following :**12**

- a) Perform the subtraction using 2'S Complement methods.
 $(85)_{10} - (32)_{10}$
- b) Explain the operation of an R-S flip-flop using NAND gates only with its truth table.
- c) Write the alternative function of Port-3 pins of 8051.
- d) Explain the following instruction :
 - i) DAA
 - ii) DIV AB
 - iii) CJNE A, data, rel
 - iv) SWAP A

4. Attempt any THREE of the following :**12**

- a) Perform the BCD Addition. $(17)_{10} + (56)_{10}$
- b) Explain the term race around condition in J-K flip flop. Suggest a suitable method to overcome it.
- c) Draw logical pin diagram of 8051 and explain function of \overline{EA} , ALE.
- d) Explain the following addressing modes in the 8051 microcontroller using ADD instruction?
 - i) Immediate addressing mode
 - ii) Register addressing mode
 - iii) Direct addressing mode
 - iv) Indirect addressing mode
- e) Identify the input and out devices
 - i) LED
 - ii) Relay
 - iii) LCD
 - iv) Stepper motor and

Draw the interfacing diagram of 8 LEDs connected to port 2 of 8051.

5. Attempt any TWO of the following :**12**

- a) Design a 4 bit asynchronus counter using JK flip flop, write it's truth table and sketch waveforms.
- b) Explain internal and external memory organisation of 8051.
- c) Describe a system to interface two $2k \times 8$ -bit RAM chips with the 8051 microcontroller. Provide the memory map of the system along with a diagram of the interfacing.

6. Attempt any TWO of the following :**12**

- a) Realize the AND, OR gate using only NAND gates and NOR gates.
 - b) Find the status of CY and AC flags for each of the following.
 - i) `MOV A, #3FH`
`ADD A, #45H`
 - ii) `MOV A, #0FFH`
`SETB C`
`ADDC A, #00H`
 - iii) `CLR C`
`MOV A, #0FFH`
`ADDC A, #01H`
`ADDC A, #00H`
 - c) Draw and explain an interfacing diagram of stepper motor with 8051 using ports.
-