

22208

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each Section on separate answer sheet.
 - (3) Answer each next main Question on a new page.
 - (4) Illustrate your answers with neat sketches wherever necessary.
 - (5) Figures to the right indicate full marks.
 - (6) Assume suitable data, if necessary.


Marks

SECTION - I

- 1. Attempt any SIX of the following : 12**
- (a) Define (i) Potential difference (ii) Permeability.
 - (b) Define average value & RMS value. Give its mathematical formula.
 - (c) State the Faraday's law of electromagnetic induction.
 - (d) Draw B-H curve.
 - (e) State the types of transformer.
 - (f) Define transformation ratio of transformer. Give its mathematical formula.
 - (g) Give the applications of single phase motor. (any four)
- 2. Attempt any THREE of the following : 12**
- (a) Explain the working of Autotransformer.
 - (b) Compare star connected system & delta connected system.



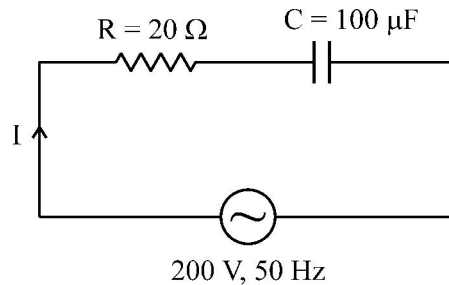- (c) A capacitor of capacitance $100 \mu\text{F}$ is connected in series with resistor of resistance 20Ω . If the combination is connected across 200 V , 50 Hz AC supply, calculate - (i) Impedance of circuit (ii) Current in the circuit.



- (d) Explain the construction & working of single phase AC motor.

3. Attempt any TWO of the following :

12

- Derive the EMF equation of single phase transformer. State the applications of single phase transformer.
- Derive the equations of self inductance & mutual inductance.
- A sinusoidal voltage with equation $V = 173 \sin (314 t - 30^\circ)$ Volt is applied to load. Calculate –
 - Maximum voltage
 - RMS voltage
 - Frequency
 - Time period
 - Phase
 - Angular frequency

SECTION - II

4. Attempt any FIVE of the following :

10

- Give the examples of Active components & Passive components.
- Compare analog IC & digital IC.

- (c) Draw a symbol of capacitor & inductor.
- (d) Define rectifier. State the types of rectifier.
- (e) Compare PN junction diode & Zener diode.
- (f) State the operating regions of transistor.

5. Attempt any THREE of the following :

12

- (a) Draw the following signals and explain the parameters of each signal :
 - (i) Sinusoidal signal
 - (ii) Square
- (b) Compare half-wave rectifier, full-wave centre tap rectifier & bridge rectifier.
(4 points)
- (c) Draw & explain V-I characteristics of zener diode.
- (d) Explain transistor as a switch with circuit diagram.

6. Attempt any TWO of the following :

12

- (a) Calculate values of resistor using following colour codes :
 - (i) orange orange brown gold
 - (ii) brown black green gold
 - (iii) yellow violet yellow silver
 - (b) Draw a circuit diagram of bridge rectifier with capacitor filter and explain its operation with waveforms.
 - (c)
 - (i) Define α & β of transistor. Derive the relation between α & β .
 - (ii) Draw output characteristics of BJT in Common Emitter (CE) configuration & show all the operating regions.
-

