

22213

24225

3 Hours / 70 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answers with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. **Attempt any FIVE of the following :** **10**
- a) Draw the symbol of
 - i) Zener Diode
 - ii) LED
 - b) Name the circuit to obtain D.C. signal from A.C. signal.
 - c) Draw the symbol of PNP and NPN transistor.
 - d) Draw the pin configuration of IC7810.
 - e) Define oscillator and its types.
 - f) List the different number system in digital Electronics.
 - g) State the application of Laser Diode.

P.T.O.

- 2. Attempt any THREE of the following :** **12**
- a) Sketch circuit diagram and input output waveform of full wave rectifier. State its efficiency.
 - b) Compare CB, CE and CC configuration (Any four points).
 - c) Sketch the block diagram of D.C. regulated power supply. State the function of each block.
 - d) Sketch circuit diagram of Hartely Oscillator. State expression for frequency of oscillation.
- 3. Attempt any THREE of the following :** **12**
- a) Draw block diagram of T and D Flip-Flop with truth table.
 - b) Sketch reverse biased characteristic of zener diode and PN junction diode. Write comment on these characteristics.
 - c) Sketch circuit diagram and input output waveform of bridge wave rectifier.
 - d) Describe the working of NPN transistor.
- 4. Attempt any THREE of the following :** **12**
- a) Draw input output characteristics of CE configuration.
 - b) Sketch circuit diagram of crystal oscillator. State its any two advantages.
 - c) Draw OR gate and AND gate using Universal Gates.
 - d) Explain the working of PN junction diode in forward and reverse biased mode.
 - e) Explain with circuit diagram operation of zener diode as a voltage regulator.

5. Attempt any TWO of the following : 12

- a) In full wave bridge rectifier $V_m = 10V$, $R_L = 10K\Omega$. Find out VDC, IDC, ripple factor and PIV.
- b) In a common base connection, current amplification factor α is 0.9. If the emitter current is 1MA, determine the value of base current and collector current.
- c) Sketch functional block diagram of IC723 and explain each block in detail.

6. Attempt any TWO of the following : 12

- a) Sketch circuit diagram of RC phase shift oscillator if the value of capacitor $C = C_1 = C_2 = C_3 = 5 \text{ P.F.}$ and frequency of the oscillation is 800Hz.
Calculate the value of resistor R ($R = R_1 = R_2 = R_3$).
 - b) Convert :
 - i) $(384)_8 = (?)_2$
 - ii) $(513)_{10} = (?)_2$
 - iii) $(225)_{10} = (?)_{16}$
 - c) Define α , β and γ of transistor and give the relation between α , β and γ transistor.
-