

22216

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :

10

- (a) Sketch energy band diagram of insulator and semiconductor.
- (b) State types of JFET and draw its symbol with terminal names.
- (c) Draw symbol of NPN and PNP transistor.
- (d) State any two applications of FET.
- (e) Define : Load Regulation and Line Regulation.
- (f) Draw basic block diagram of a DC regulated power supply.
- (g) Define the term 'knee-voltage' of P-N junction diode. Give knee voltage of Si diode.

2. Attempt any THREE of the following :

12

- (a) Describe experimental set-up for operation of P-N junction diode in forward bias. Draw its characteristics.
- (b) Sketch input and output characteristics of CE configuration. Label various regions on characteristics.



- (c) Sketch circuit diagram of transistorized series voltage regulator and explain its working.
- (d) Explain the concept of DC load line and operating point.

3. Attempt any THREE of the following :

12

- (a) State the values of the following parameters with reference to full wave bridge rectifier :
 - (i) Ripple Factor
 - (ii) Efficiency
 - (iii) TUF
 - (iv) PIV
- (b) Sketch circuit diagram of positive biased clipper using diode and explain its working.
- (c) Derive relationship between transconductance (g_m), amplification factor (μ) and drain resistance (r_d) of FET.
- (d) State any four applications of regulated D.C. power supply.

4. Attempt any THREE of the following :

12

- (a) Draw circuit diagram for π filter and explain its working with waveform.
- (b) Explain working of NPN transistor with neat circuit diagram.
- (c) For common base (CB) configuration of BJT, if $I_E = 2 \text{ mA}$ and $I_B = 20 \mu\text{A}$, calculate value of I_C and current gain α (alpha).
- (d) Compare EMOSFET and DMOSFET.
- (e) With the help of reverse characteristics of zener diode, explain its use as a regulator.

5. Attempt any TWO of the following :**12**

- (a) Explain drain characteristics of JFET with ohmic region, saturation region cut-off region and breakdown region.
- (b) An AC supply of 230 V is applied to HWR through a transformer with turns ratio of 10 : 1. Find (i) average DC output voltage, (ii) average DC output current (iii) PIV of diode, also (iv) rms value of voltage and current. (Assume $R_L = 10 \text{ k}\Omega$)
- (c) Sketch constructional diagram of LED and state its three applications.

6. Attempt any TWO of the following :**12**

- (a) Describe classification of solids on the basis of energy band diagram.
 - (b) Sketch the circuit diagram of center-tap full-wave rectifier and explain its working with input and output waveforms.
 - (c) Explain with circuit diagram voltage divider biasing method for BJT.
-

