

22221

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE :

10

- (a) Define the term :
 - (i) Magnetomotive Force
 - (ii) Permeability
- (b) Define the power factor. State its value for purely resistive circuit.
- (c) Explain the principle of operation of a d.c. motor.
- (d) Explain balanced load and unbalanced load in 3 ϕ .
- (e) Draw circuit diagram of 1 ϕ split phase I.M.
- (f) Give any two application of universal motor.
- (g) State the function of MCB and ELCB.

2. Attempt any THREE :

12

- (a) Differentiate between electrical circuit and magnetic circuit (Any four).
- (b) Derive the EMF equation of a 1 ϕ transformer.



- (c) Calculate the impedance, current, active power & P.F. for a series circuit having a resistance of $10\ \Omega$ and capacitance of $100\ \mu\text{F}$ fed from single phase, 200 V, 50 Hz A.C. supply.
- (d) State the different types of fuses. Explain operation of fuse.

3. Attempt any THREE :**12**

- (a) Draw and explain B-H curve of a magnetic material.
- (b) Draw a circuit diagram of 3ϕ star connected load. Label I_{ph} , I_L , V_{ph} and V_L on it.
- (c) Draw the schematic diagram of :
 - (i) DC shunt motor
 - (ii) DC series motor
- (d) State the various types of earthing and explain any one type with its neat sketch.

4. Attempt any THREE :**12**

- (a) Explain the concept of Dynamically and Statically induced emf.
- (b) With neat sketch, explain speed control of DC shunt motor by flux control method.
- (c) Draw the schematic diagram of shaded pole motor and state its principle of operation.
- (d) State relation between phase and line current and voltages in balanced star and delta connection.
- (e) Draw a neat sketch and explain working of any one type of stepper motor.

5. Attempt any TWO :**12**

- (a) A metal-filament lamp rated at 750 watt; 100 V is to be used on a 230 V, 50 Hz supply by connecting a capacitor of suitable value in series. Determine :
- (i) The capacitance required in μF .
 - (ii) Phase Angle
 - (iii) Power Factor
 - (iv) Apparent Power
 - (v) Reactive Power
 - (vi) Draw phasor diagram.
- (b) Three similar coils each of resistance of $20\ \Omega$ and an inductance of 0.1 H are connected in star to the 3ϕ , 440 V, 50 Hz supply system. Find the phase current, line current, phase voltage, power consumed.
- (c) Draw constructional sketch of DC motor, mention each part on it and state basic principle of motor.

6. Attempt any TWO :**12**

- (a) A sinusoidal voltage of 48 V is applied in series with resistance of $4\ \text{k}\Omega$. Determine I_{max} , I_{Average} , form factor.
- (b) For a capacitor start, Induction run single phase IM :
- (i) Show the schematic representation.
 - (ii) Explain its principles of working.
 - (iii) Any two applications.
- (c) Compare Switch Fuse Unit (SFU) and Fuse Switch Unit (FSU).
-

