

22225

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.

**Marks**

1. **Attempt any FIVE of the following :** **10**
  - (a) State any two advantages of Integrated circuits.
  - (b) Write PIV ratings of diode for half wave and full wave centre tap Rectifier.
  - (c) Justify why ' $\alpha$ ' is less than unity.
  - (d) Define Amplification factor and transconductance of JFET.
  - (e) Define Active and Passive components.
  - (f) Define Active and Passive Transducers.
  - (g) State selection criteria for Transducers.
2. **Attempt any THREE of the following :** **12**
  - (a) Explain voltage source with diagram.
  - (b) Explain zener diode as a voltage regulator with diagram.
  - (c) Draw neat labelled construction of LED & explain its working principle.
  - (d) Differentiate BJT & FET.
3. **Attempt any THREE of the following :** **12**
  - (a) Draw symbol & neat labelled construction of MOSFET.
  - (b) Draw a sketch & describe the working of pressure transducer.
  - (c) State different types of resistors & state any four specifications of resistors.
  - (d) Explain the working of single stage RC coupled amplifier with diagram.




**4. Attempt any THREE of the following :****12**

- (a) Draw a sketch & describe the working of temperature transducer.
- (b) Differentiate between P-N junction diode & zener diode.
- (c) Derive relation between ' $\alpha$ ' & ' $\beta$ ' of a transistor.
- (d) When  $V_{GS}$  of FET changes from  $-3.3$  V to  $-3.0$  V, the drain current changes from  $1.1$  mA to  $1.5$  mA, Find the value of transconductance.
- (e) Draw block diagram of regulated power supply & explain its working.

**5. Attempt any TWO of the following :****12**

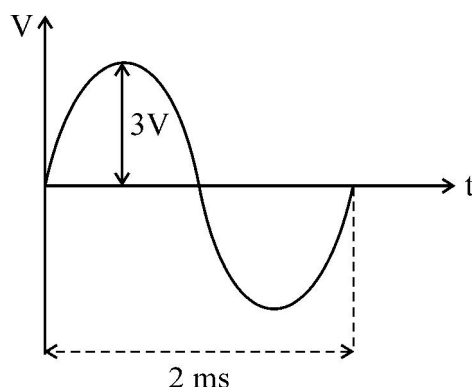- (a) Solve the following :
  - (i) Define wavelength & frequency.
  - (ii) In the waveform shown in figure-1.



Determine its Amplitude, frequency, phase & wavelength.

- (b) In CE configuration, if  $\beta = 99$ , leakage current  $I_{CEO} = 100 \mu\text{A}$ . If the base current is  $0.7$  mA, determine the collector current & emitter current.
- (c) In full wave Rectifier (Bridge type)  $V_m = 20$  V,  $R_L = 15 \text{ k}\Omega$ , Find out  $V_{DC}$ ,  $I_{DC}$ , ripple factor & PIV.

**6. Attempt any TWO of the following :****12**

- (a) Draw neat labelled Transfer characteristics of JFET. Differentiate Depletion type MOSFET & Enhancement type MOSFET.
  - (b) State the applications of BJT, FET & photodiode.
  - (c) With suitable diagram, explain the steps to measure the temperature of any metal using transducer.
-