

22323

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks**1. Attempt any FIVE of the following :****10**

- (a) State any two Boolean law with expression.
- (b) Define and draw the logical symbol of demultiplexer.
- (c) Draw the circuit of one-bit memory cell.
- (d) State the function of Segment register.
- (e) Define basic gates with their symbols.
- (f) Give example of any two types of addressing mode.
- (g) List features of 8086 Microprocessor.

2. Attempt any THREE of the following :**12**

- (a) Implement a two input OR gate using NAND gates only.
- (b) Convert the given SOP form into POS form :

$$Y(A, B, C, D) = (\bar{A} \cdot BC) + (B \cdot \bar{C}\bar{D}) + (\bar{A}\bar{B})$$



- (c) Explain J-K flip-flop with the help of neat diagram. Write its Truth Table.
- (d) Explain rules to simplify Boolean expression using K-map.

3. Attempt any THREE of the following :

12

- (a) Explain with justification NOR gate as universal gate.
- (b) Write an assembly language program to perform addition of two 16-bit numbers.
- (c) Draw waveforms for positive and negative edge triggering with proper labelling. Identify two situations where these triggering can be used.
- (d) Simplify $Y = F(A, B, C, D)$

$$= \Sigma m(1, 2, 8, 9, 10, 12, 13) + d(4, 5)$$

using K-map and write expression.

4. Attempt any THREE of the following :

12

- (a) Interpret the following program and specify output for following situations :


MOV BX, 55F9H

MOV AX, 3A69H

- (1) Masking of higher Nibble of AX
- (2) Rotate left through carry contents of BX by 4 position.
- (3) Shift left contents of AX, by 6 position.
- (4) Add AX, BX
- (b) Describe the construction of half-adder using K-map.
- (c) Compare combinational & sequential circuit.
- (d) Explain the process of physical address calculation with suitable example.
- (e) Reduce the Boolean expression & draw logical diagram for reduced expression $Y = ABC + \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$

5. Attempt any TWO of the following :**12**

- (a) Given the following logic diagram in fig (1). Write truth table. Identify equivalent gate for the obtained truth table :

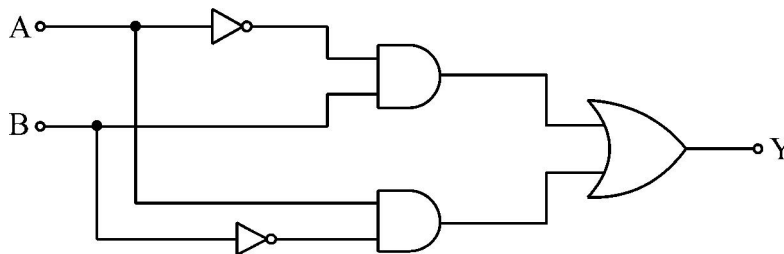**fig (1)**

- (b) Draw Flag register format of 8086 Microprocessor. Explain TF, DF, CF, IF Flags.
- (c) Write an assembly language program for finding smallest number from the array of ten number. (Assume suitable data)

6. Attempt any TWO of the following :**12**

- (a) Draw architectural block diagram of 8086 Microprocessor and describe the function of each block.
- (b) Design half subtractor using NOR gate only. Write truth table.
- (c) Differentiate between CISC & RISC and justify each of them in practice.
-

