

22324

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- 
- Instructions* – (1) All Questions are *Compulsory*.  
(2) Illustrate your answers with neat sketches wherever necessary.  
(3) Figures to the right indicate full marks.  
(4) Assume suitable data, if necessary.  
(5) Use of Non-programmable Electronic Pocket Calculator is permissible.  
(6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any FIVE of the following : 10
- a) Define impedance and power factor.
  - b) Define Active power and Reactive power.
  - c) Define Bandwidth of parallel resonance circuit.
  - d) Draw a three phase voltage waveform with respect to time.
  - e) State The four important steps to solve node analysis.
  - f) State Thevenin's theorem.
  - g) State Norton's theorem.

P.T.O.

2. Attempt any THREE of the following :

12

- A resistance of  $100\Omega$  and  $50\mu\text{F}$  capacitor are connected in series across  $200\text{V}$ ,  $50\text{Hz}$ . Find the voltage across resistance and capacitor.
- Calculate supply current and power factor, if impedance  $Z_1 = (3 + j4)\Omega$  and  $Z_2 = (4 + j3)\Omega$  are connected in parallel across  $200\text{V}$ ,  $50\text{Hz}$  supply. Calculate supply current and power factor.
- State the voltage and current relationship in terms of line and phase value for three phase star connected system and also write the equation for total power in terms of line and phase values of voltage and current.
- Reduce the following network to a single delta form made up of three resistance only.

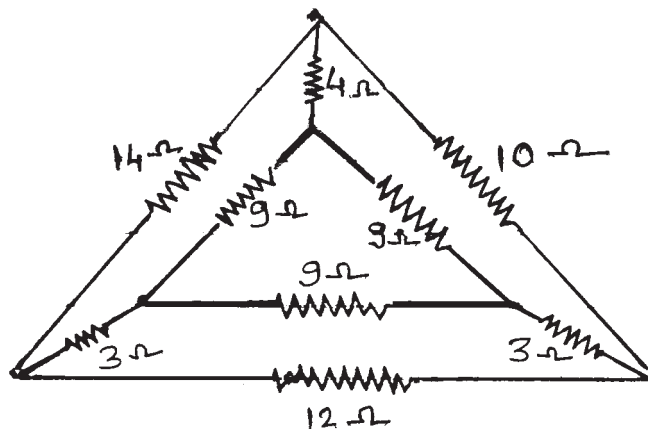


Fig. No. 1

3. Attempt any THREE of the following :

12

- Derive the expression of resonant frequency in RLC series circuit.
- A coil having resistance of  $10\Omega$  and Inductance of  $0.1\text{H}$  is connected in parallel with a capacitor of  $10\mu\text{F}$  across a  $200\text{V}$ ,  $50\text{Hz}$  supply. Find the current taken from the supply and overall power factor. Draw a neat phasor diagram.
- Three resistance of  $15\Omega$ ,  $12\Omega$ , and  $18\Omega$  are connected in delta. Find equivalent value of them if they connect in star.

- d) Find the current through  $20\Omega$  Resistor of the following Fig. No. 2 using Node Analysis.

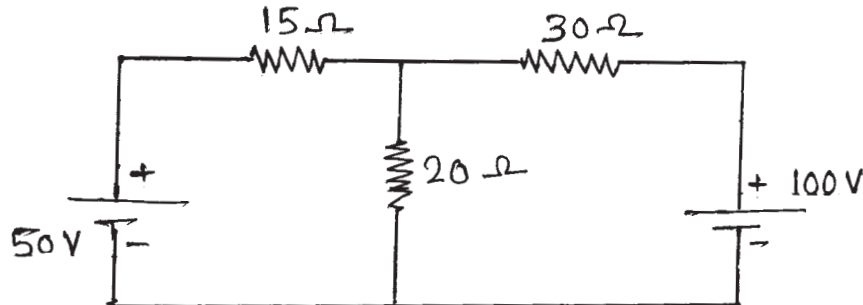


Fig. No. 2

- e) Find the current through  $5\Omega$  Resistor of the following using Thevenin's theorem.

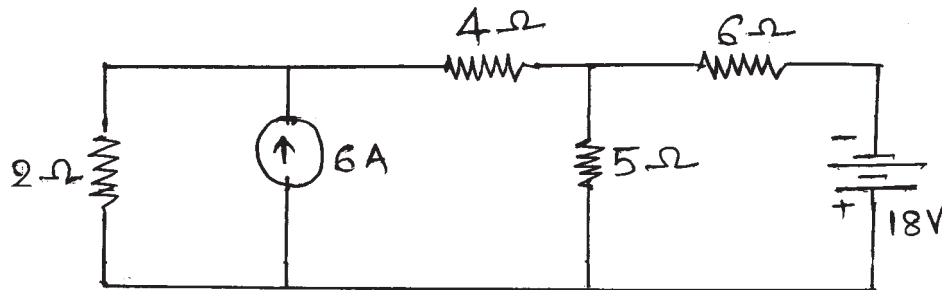


Fig. No. 3

4. Attempt any THREE of the following :

12

- a) A series circuit consist of  $R = 14\Omega$ ,  $L = 0.07H$  and  $C = 210\mu F$ . Find –
  - i) Resonance frequency
  - ii) Quality factor
- b) A single AC circuit containing resistor of  $30\Omega$  and inductor of  $0.15H$  are connected in parallel across  $230V$ ,  $50\text{ Hz}$  supply. Determine –
  - i) Admittance
  - ii) Circuit current
  - iii) Power factor
  - iv) Power consumed

- c) State the meaning of three phase balance and unbalance load.
- d) State and explain Reciprocity theorem.

5. Attempt any TWO of the following :

12

- a) Define quality factor for RLC parallel circuit and also derive the expression for the Q - factor related to parallel circuit.
- b) Find the current through  $10\Omega$  Resistor of the circuit using Mesh analysis.

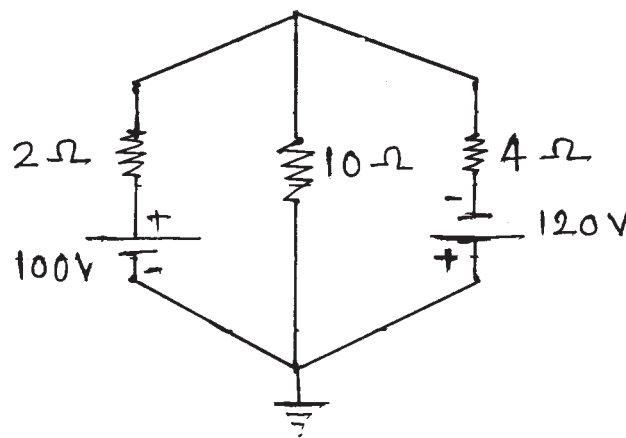


Fig. No. 4

- c) Find the current flowing through  $3\Omega$  resistor using Norton's theorem.

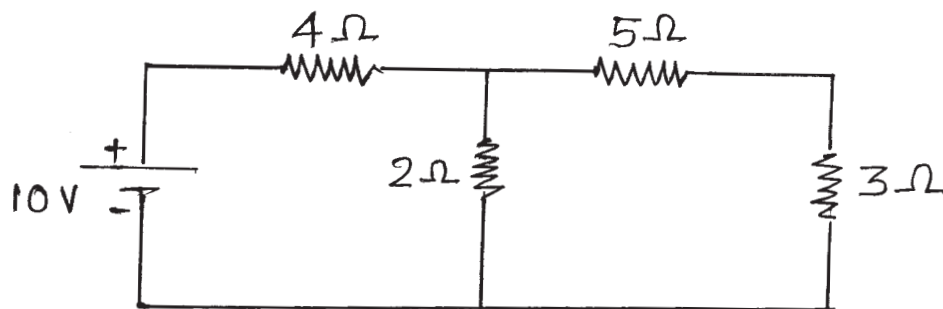
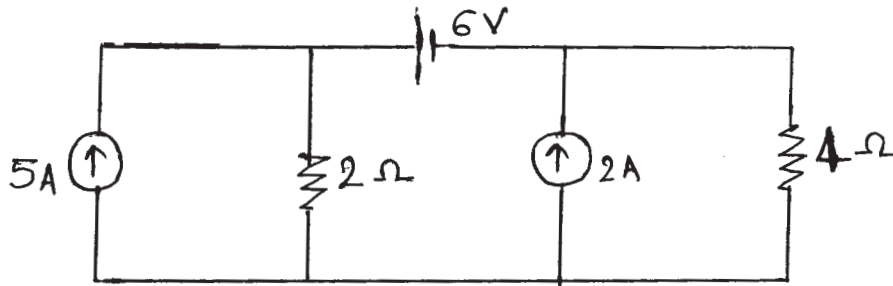


Fig. No. 5

**6. Attempt any TWO of the following :****12**

- a) For a series RLC circuit consisting of  $R = 16\Omega$ ,  $X_L = 18\Omega$  and  $X_C = 6\Omega$  supplied with 100V, 50 Hz supply. Determine –
- Circuit Impedance and circuit current
  - Circuit power factor and power consumed by the circuit.
- b) Three identical coils, each having resistance of  $15\Omega$  and inductance of 0.03 H are connected in Delta across three phase, 400 V, 50 Hz, supply. Calculate –
- Phase current
  - Line current
  - Power factor
  - Total power consumed
- c) Find the current through  $4\Omega$  resistor using Superposition theorem.

**Fig. No. 6**

---