

22326

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw the symbol and VI characteristics of Power MOSFET.
- (b) Draw the V-I characteristics of the Power transistor and show all the region.
- (c) State the types of protection circuits.
- (d) Give the types of SCR turn on methods.
- (e) Define firing angle and conduction angle.
- (f) Define transfer time and backup time of UPS.
- (g) Draw the block diagram of SMPS.

2. Attempt any THREE of the following :

12

- (a) Describe the construction of IGBT with neat sketch.
- (b) Draw the V-I characteristics of SCR with neat sketch and explain its forward blocking and conduction mode.
- (c) Explain the operation of R triggering with neat circuit diagram.
- (d) Explain the operation of single phase half controlled Rectifier with RL Load.



- 3. Attempt any THREE of the following : 12**
- (a) Explain two transistor analogy of SCR with neat diagram.
 - (b) Explain the operation of single phase fully controlled rectifies with RL load.
 - (c) Explain the operation of Burglar alarm with circuit diagram.
 - (d) Explain the operation AC circuit breaker.
- 4. Attempt any THREE of the following : 12**
- (a) Draw a neat labelled V-I characteristics of DIAC and explain it.
 - (b) Describe triggering of SCR using UJT relaxation oscillator.
 - (c) State the effect of source impedance in controlled rectifier operation with circuit diagram.
 - (d) Describe the emergency lighting system with neat diagram.
 - (e) Describe the temperature controller using SCR.
- 5. Attempt any TWO of the following : 12**
- (a) Draw VI characteristics of GTO and explain its operation with neat sketch.
 - (b) Explain Class C commutation with circuit diagram and waveforms.
 - (c) Explain half controlled bridge rectifier with R load with its circuit diagram and waveform.
- 6. Attempt any TWO of the following : 12**
- (a) Explain auxiliary commutation with a neat circuit diagram.
 - (b) Draw the symbol and characteristics of the UJT, SCS, LASCR.
 - (c) Explain single phase full wave Midpoint (M2) controlled converter with R Load with necessary waveforms and circuit diagram.
-