

22330

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answer with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following: 10
- a) Define –
 - i) Admittance
 - ii) Conductance
 - b) Draw the phasor diagram of R-L series circuit.
 - c) Define Q factor for series RLC circuit.
 - d) Write the formula for delta to star conversion.
 - e) Draw –
 - i) Ideal voltage source
 - ii) Practical current source.
 - f) State maximum power transfer theorem.
 - g) Write equation of open circuit Z parameters.

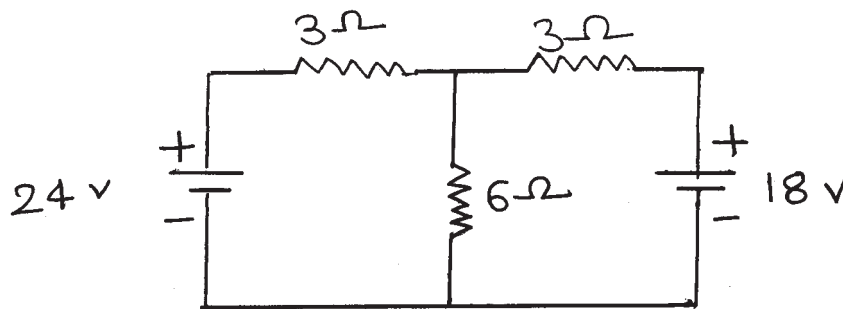
P.T.O.

2. Attempt any THREE of the following: 12

- a) Draw circuit of series R-C circuit, its phasor diagram, waveform of voltage and current in the circuit.
- b) Compare series and parallel resonance on the basis of –
 - i) Resonant frequency
 - ii) Impedance
 - iii) Current
 - iv) Magnification.
- c) Write steps to convert practical voltage source into practical current source.
- d) State superposition theorem. Write steps to find current in an element using superposition theorem.

3. Attempt any THREE of the following: 12

- a) Explain concept of initial and final condition in switching circuits for elements R and L.
- b) Drive expression for resonant frequency of R-L-C series circuit.
- c) Find the current in 6Ω resistor in the circuit shown in Figure No. 1 using mesh analysis.


**Fig. No. 1**

- d) State the condition for maximum power transfer theorem. Write steps to find current in the load by maximum power transfer theorem.

4. Attempt any THREE of the following:

12

- a) A series resistance of 20Ω , inductance of 0.2H and capacitance of $100\ \mu\text{F}$ are connected in series across a $220\ \text{V}$, $60\ \text{Hz}$ supply. Determine –
- Impedance
 - Current
 - Active power
 - Apparent power.
- b) An R-C series circuit consists of $R = 10\Omega$ and $C = 200\ \mu\text{F}$. It is connected across $250\ \text{V}$, $50\ \text{Hz}$ 1ϕ AC supply. Calculate the value of power consumed by the circuit.
- c) Two impedances $Z_1 = 10 + j5$ and $Z_2 = 8 + j9$ are connected in parallel across a voltage source of $V = 200 + j0$. Calculate the circuit current and branch currents. Draw the vector diagram.
- d) Using source transformation technique find resultant current I through the circuit given in Figure No. 2.

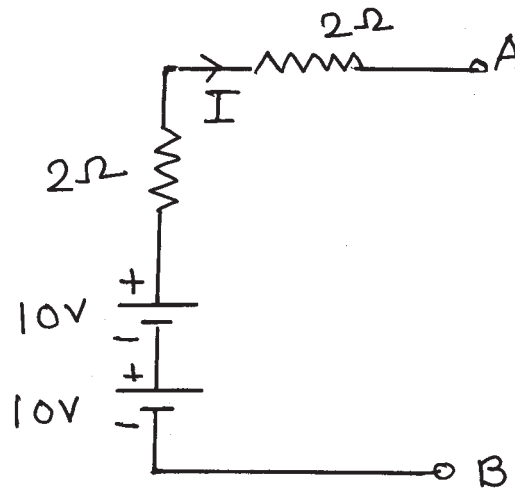Fig. No. 2

- e) Find the current in 100Ω resistance of Figure No. 3 using superposition theorem.

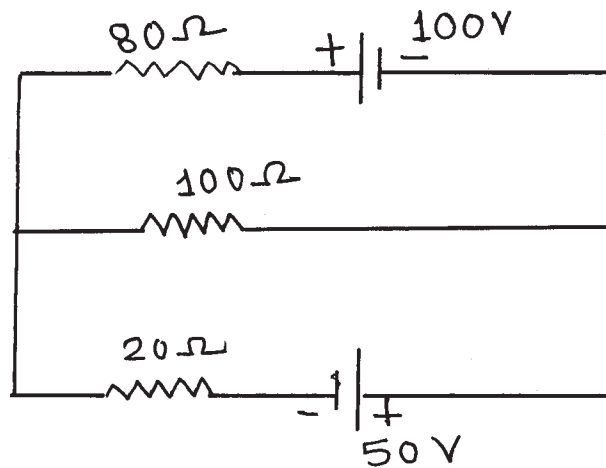
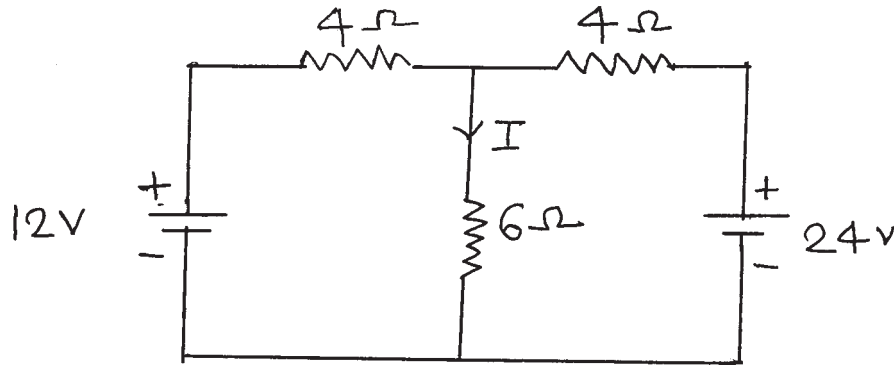


Fig. No. 3

5. Attempt any TWO of the following:

12

- a) A circuit having a resistance of 5Ω , inductance of 0.4 H and capacitance in series connected across 100 V , 50 Hz supply. Calculate –
- Value of capacitance to give resonance
 - Impedance
 - Current at resonance
 - Voltage across resistor
 - Voltage across inductor
 - Q factor of resonance.
- b) Find current through 6Ω resistor in circuit given in Figure No 4 using Thevenin's theorem.


**Fig. No. 4**

- c) Draw the two port network and determine the indicated parameter for the following configuration –
- Cascade configuration
 - Series configuration
 - Parallel configuration.


6. Attempt any TWO of the following:

12


- a) Find current in 40Ω and 10Ω resistor in circuit given in Figure No. 5 using nodal analysis method.

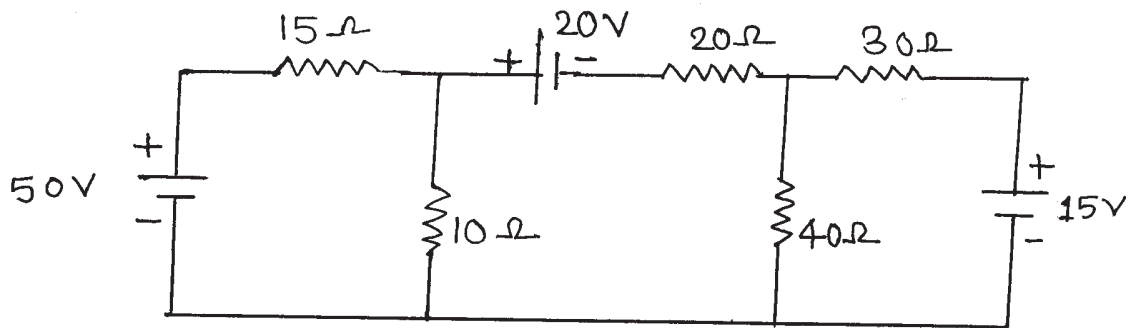**Fig. No. 5**

- b) Verify the reciprocity theorem for the network given in Figure No. 6.

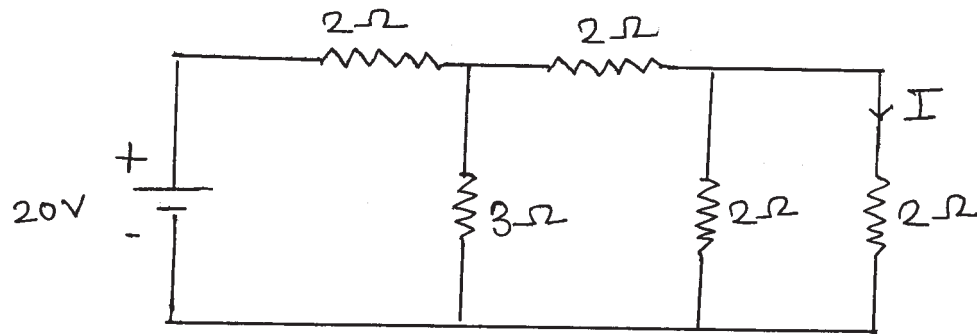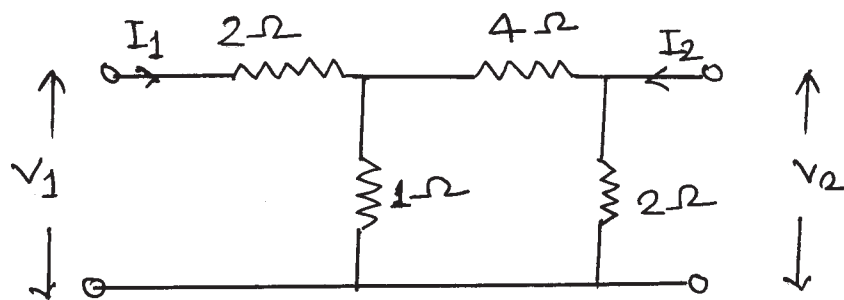Fig. No. 6

- c) Find Z parameters for the network given in Figure No. 7.

Fig. No. 7