

22421

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks**1. Attempt any FIVE of the following :****10**

- (a) Construct OR gate using NAND gate.
- (b) Write the excitation table for T-F/F.
- (c) Implement D flip-flop using JK flip-flop. Write its truth table.
- (d) Realize the following equations using NAND gates only :

$$Y = (A + B) \cdot (B + C)$$

- (e) Identify direct addressing instructions from following instructions :

(i) MOV R₀, R₅(ii) MOV R₀, #75H(iii) MOV R₀, 80H

(iv) ADD A, 45H



- (f) If initial content of accumulator is 66H, find out the new content of accumulator after execution of the instruction

RR A

- (g) State the function of LCD display pins

(i) R/W

(ii) RS

2. Attempt any THREE of the following :

12

- (a) Define following terms related to logic families :

(i) Noise Margin

(ii) Fan-out

(iii) Fan-in

(iv) Power Dissipation

- (b) Draw logic diagram of 8 : 1 MUX and give it's truth table.

- (c) Design full adder using K-map. Draw circuit diagram with truth table.

- (d) State and explain De-Morgan's 2nd theorem.

3. Attempt any THREE of the following :

12

- (a) List out any four assembler directives and state their functions.

- (b) Draw neat labelled interfacing diagram of 8051 with stepper motor.

- (c) Explain race around condition in JK Flip-Flop and how it is eliminated ?

- (d) Write the alternate function of port 3 pins of 8051 microcontroller.

4. Attempt any THREE of the following :

12

- (a) Explain the following instructions :

(i) SWAP A

(ii) MUL AB

(iii) DAA

(iv) DIV AB

- (b) Explain Power Saving options (i) Power down mode (ii) Idle mode of 8051.

- (c) Minimize the following Boolean expression using K-map and realize it using the basic gates.

$$Y(A, B, C, D) = \Sigma m(1, 3, 5, 9, 11, 13)$$

- (d) Prove NAND gate as universal gate with suitable diagrams.
- (e) Draw the architecture of 8051 and label various blocks.

5. Attempt any TWO of the following :

12

- (a) Develop an ALP for interfacing of LED's with port 2 of 8051. Draw interfacing for the same.
- (b) Develop an ALP to arrange ten numbers stored in internal memory locations starting from 50H location in ascending order.
- (c) Explain internal and external memory organisation of 8051.

6. Attempt any TWO of the following :

12

- (a) Explain functions of all pins of port 0, port 1, port 2 of 8051 microcontroller.
- (b) Develop an ALP to generate square wave of 2 kHz at port pin P2.1. Draw flow chart for it.
- (c) Construct 3 bit asynchronous up-counter using flip-flop. Draw its timing diagram.
-

