

22433

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following : 10
- a) Draw single input balanced output configuration of differential amplifier.
 - b) State virtual ground concept of op-amp.
 - c) Identify the type of filter for given frequency response characteristics. shown in Fig. No. 1.

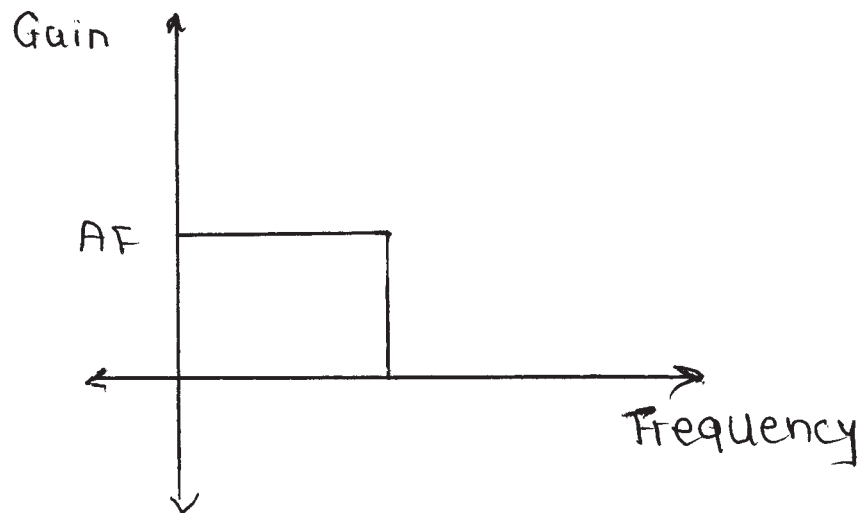


Fig. No. 1

P.T.O.

- d) Draw the pin diagram of IC 555.
- e) Define –
 - i) Roll off rate
 - ii) Cut off frequency
- f) List linear and non linear op-amp circuit.
- g) Draw the V to I converter with grounded load using op-amp.

2. Attempt any THREE of the following : 12

- a) State four application of instrumentation amplifier.
- b) If $R_1 = 2K\Omega$, $R_F = 100 K\Omega$, $V_{CC} = + 15V$ and rms input voltage $V_i = 50mV$ calculate output voltage in inverting and non-inverting mode.
- c) Draw the first order low pass butterworth filter with frequency response. Give the expression for cut off frequency of filter.
- d) Differentiate between integrator and differentiator.

3. Attempt any THREE of the following : 12

- a) Draw ideal and practical transfer characteristics of op-amp.
- b) Explain the instrumentation amplifier with three op-amps.
- c) Draw the circuit diagram of wein bridge oscillator using IC741 and give expression for frequency of oscillation.

- d) Draw the circuit diagram of OP-AMP based filter circuit which fulfill following response. Refer Fig. No. 2.

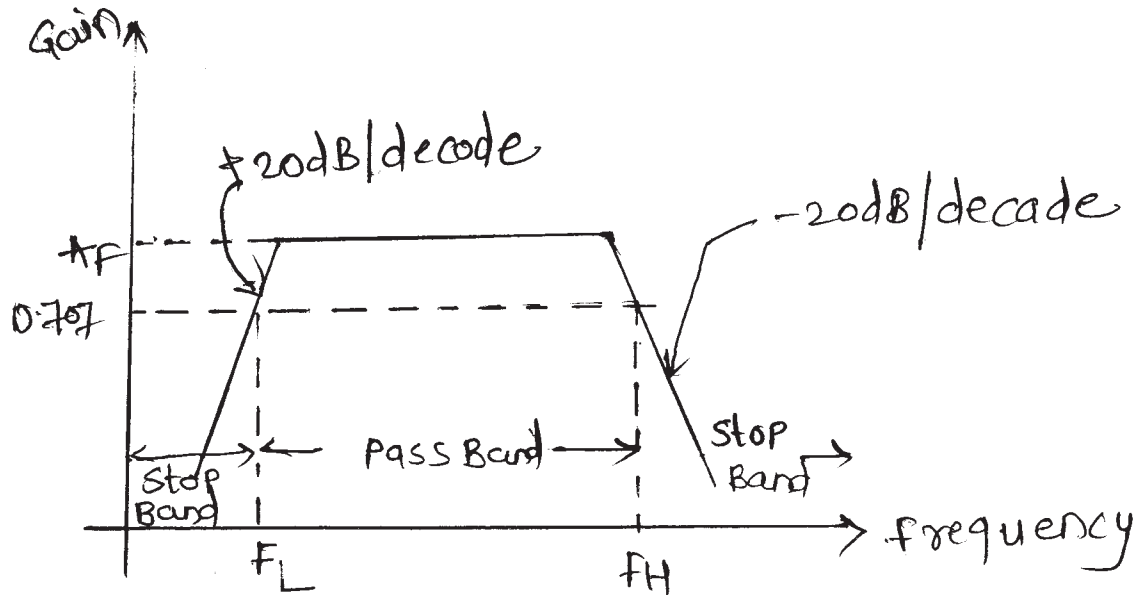


Fig. No. 2

4. Attempt any THREE of the following : 12
- Draw the log amplifier and antilog amplifier using op-amp.
 - Compare open loop and closed loop configuration of op-amp.
 - Construct and draw the circuit to get output voltage $V_0 = 3V_1 + 2V_2$ where V_1 and V_2 are input voltage.
 - List advantages of active filter over passive filter.
 - Draw and describe circuit diagram of RC phase shift oscillator.
5. Attempt any TWO of the following : 12
- Draw and explain ideal differential amplifier. State its four configuration.
 - Compare monostable, bistable and astable multivibrator.
 - Suggest op-amp based circuit to convert square wave to triangular wave and draw the input-output waveforms.

6. Attempt any TWO of the following :

12

- a) Identify the circuit diagram. Draw its input-output waveforms and also give its output voltage equation. Refer Fig. No. 3.

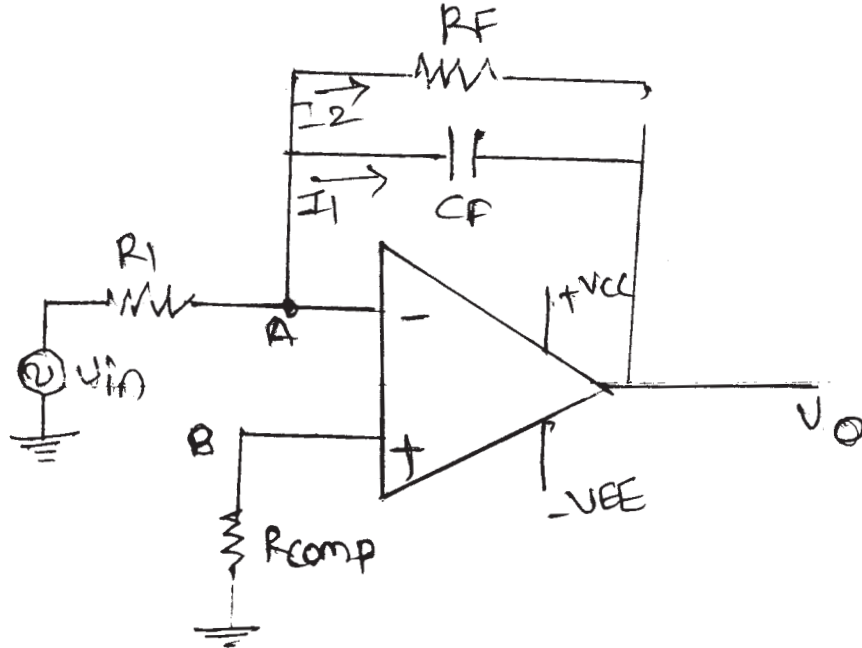


Fig. No. 3

- b) Construct and draw the circuit to get output voltage $V_o = -10V_{in}$ where v_{in} is input voltage.
- c) Explain the operation of notch filter with neat diagram and waveform.