

22526

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
  - (8) Use of steam tables, logarithmic, Mollier's chart is permitted.

**Marks**

**SECTION-I**

**1. Attempt any FIVE :**

**5 × 2 = 10**

- (a) State the need of automation.
- (b) Draw only block diagram of PLC.
- (c) Draw a ladder diagram to ON a lamp if either switch A or switch B is actuated.
- (d) Give list of any four relay type instructions with their symbols.
- (e) State the three traffic control signals with their use.
- (f) State the functions of seal in circuit w.r.t. PLC.
- (g) List the functions of Data acquisition in SCADA system.



**2. Attempt any THREE :****3 × 4 = 12**


- (a) Draw ladder diagram for stepper motor in clockwise direction.
- (b) Describe the working of Proportional-Integral Derivatives (PID) controller.
- (c) Describe the operation of solid state relay with neat diagram.
- (d) Draw ladder diagram for OR & AND gate.

**3. Attempt any THREE :****3 × 4 = 12**

- (a) List any two advantages & any two disadvantages of PLC.
- (b) Explain block diagram of SCADA. Identify different components of it.
- (c) Write the ladder program for 24 hour clock.
- (d) Explain with block diagram, the working of soft starter.

**SECTION-II****4. Attempt any THREE :****3 × 4 = 12**

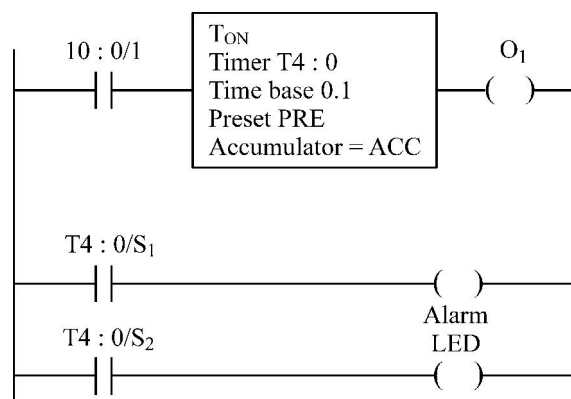- (a) Develop power & control circuit diagram to control forward & reverse motion of 3 $\phi$  Induction motor.
- (b) In the given ladder diagram, the alarm is ON for 10 sec. After 10 sec. the LED is ON. What will be the value of PRE & what are S<sub>1</sub>, S<sub>2</sub> & O<sub>1</sub> bits ?



- (c) State the functions of PLC memory w.r.t. types, speed of execution.

- (d) Develop ladder diagram for following sequences :
- When NO START PB is pressed Motor  $M_1$  starts & after 10 seconds Motor  $M_2$  starts.
  - When NC STOP, PB is pressed both motor  $M_1$ ,  $M_2$  stops immediately.
- (e) List the different applications of DCS (Distributed Control System) system.

**5. Attempt any TWO :**


**2 × 6 = 12**

- Explain the working of PLC based bottle filling system with the help of ladder diagram.
- Develop control & power circuit diagram of hoist control & mill.
- Draw block diagram of analog input module of PLC. State function of each block.

**6. Attempt any TWO :**

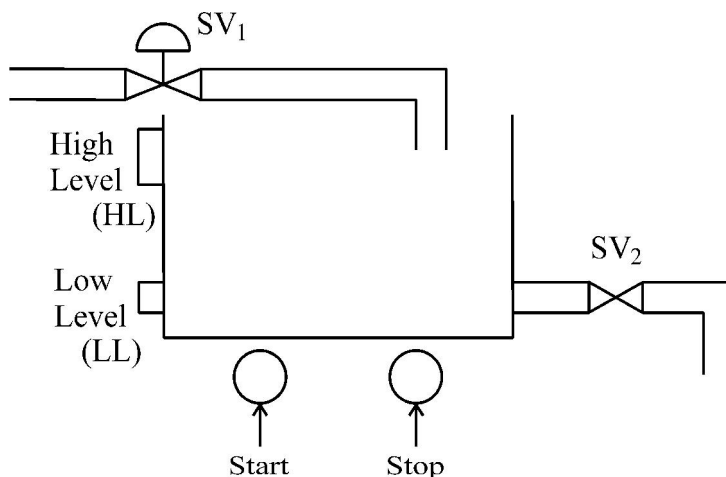**2 × 6 = 12**

- Describe the PLC based water level controller.
  - When start button is pressed process starts, when stop button is pressed process stops ?
  - If level is low,  $SV_1$  is open &  $SV_2$  is closed.
  - When level is high,  $SV_1$  is closed &  $SV_2$  is open.



- (b) Explain the instruction  $T_{ON}$  &  $T_{OFF}$  with timing diagram.
  - (c) Discuss proximity sensor with its four applications.
-