

22529

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw equivalent circuit of π network.
- (b) List out the role of Power System Engineer.
- (c) List out factors affecting proximity effect.
- (d) State significance of inductance & capacitance.
- (e) Give the formula for generalised circuit constant for T network.
- (f) $Z = 50 \angle 70^\circ$ & $Y = 412 \times 10^{-4} \angle 90^\circ$

Calculate generalised circuit constant "A".

- (g) Give the formula for co-ordinates of centre and radius of receiving end circle diagram.



2. Attempt any THREE of the following :

12

- Summarise advantages of Per Unit system.
- Calculate inductance of each conductor of 1 ϕ line having dist. 3m apart and radius of conductor is 20 mm.
- Determine GCC for resultant network when two networks are connected in series.
- A 220 kV transmission line has following constant. $A = 0.8\angle 3^\circ$, $B = 100\angle 75^\circ \Omega/\text{ph}$. Determine max power that can be received if voltage is maintained at 220 kV at both ends.

3. Attempt any THREE of the following :

12

- Develop reactance diagram for given power system as shown in Fig. 1 consider generator rating as base.

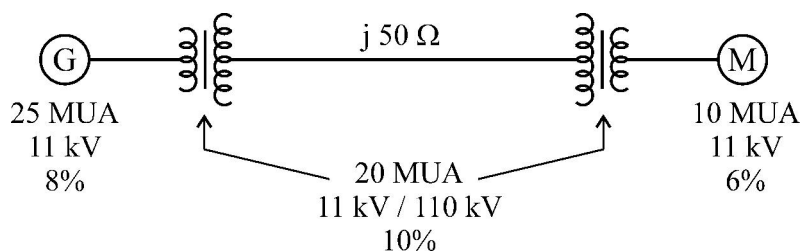


Fig.-1

- Describe skin effect & state factors affecting skin effect.
- Explain the concept of generalised circuit constant.
- A 400 kV transmission line has constant $A = 0.8\angle 2^\circ$, $B = 80\angle 70^\circ \Omega/\text{ph}$. Determine power at unity pf that can be delivered if voltage at both ends is maintained at 400 kV.

4. Attempt any THREE of the following :

12

- (a) Derive the condition for max. power at receiving end.
- (b) 3 ph transmission line has conductors mounted at corners of triangle with sides 3M, 5M & 6M. Diameter of conductor is 20 mm. Calculate inductance of each conductor.
- (c) 3 ϕ transmission line with impedance $32.9\angle 72.35^\circ \Omega/\text{ph}$ & admittance is $2.827 \times 10^{-4} \text{ mha/Ph}$ delivers load of 35 MW, 132 kV, 0.8 pf lag. Use π method & determine ABCD constants.
- (d) 3 ϕ line has following parameters $A = D = 0.9\angle 0.4^\circ$, $B = 99\angle 76.86^\circ$ sending end and receiving end, voltage is maintained at 220 kV & load angle is 9° . Calculate sending end active & reactive power.
- (e) Prove that $AD - BC = 1$.

5. Attempt any TWO of the following :

12

- (a) Define self GMD & calculate self GMD for conductor each having radius "r" arrangement as given in fig.-2.

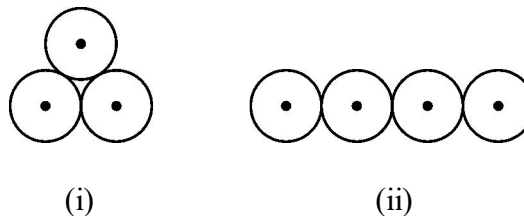


Fig.-2

- (b) Describe step by step procedure for drawing receiving end circle dia.
- (c) A 275 kV line has constant $A = 0.92\angle 1.8^\circ$, $B = 110\angle 77^\circ$ & $V_R = 275 \text{ kV}$. Calculate sending end voltage if load is 200 kW, 0.8 pf lag.

6. Attempt any TWO of the following :

12

- (a) Derive the condition for max power at sending end.
 - (b) Describe need of reactive power compensation equipments. List out types of reactive power compensation equipments with its application.
 - (c) Describe benefits of generalised circuit constant representation.
-