

22538

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Write any two applications of permanent magnet motor.
- (b) Draw schematic diagram of single phase capacitor run motor.
- (c) State any four advantages of microcontroller based control of drives.
- (d) Draw a neat diagram of single phase full converter drive.
- (e) Draw Speed-Torque characteristics of DC shunt and DC series motor.
- (f) Give any two applications of brushless DC motor.
- (g) Calculate step angle of rotation if a stepper motor has four pairs of phases and six teeth on rotor.

**2. Attempt any THREE of the following :**

**12**

- (a) Describe rotor resistance control technique employed for speed control of induction motor.
- (b) Compare AC drives and DC drives. (Any four points)
- (c) With neat diagram, explain synchronous motor drive using microcontroller.
- (d) Explain the working of phase locked loop control of DC motor with neat diagram.



- 3. Attempt any THREE of the following : 12**
- (a) State the sequence of stages & drives required in each stage for textile mills.
  - (b) With the help of neat diagram, explain voltage source inverter control for speed control of Induction Motor.
  - (c) Draw and explain stepper motor drives employing microcontroller.
  - (d) Draw speed torque characteristics of Induction motor showing all regions.
- 4. Attempt any THREE of the following : 12**
- (a) Explain four braking methods of Induction motor.
  - (b) List various stages involved in paper mill and its speed ratings at each stage.
  - (c) With the help of neat diagram, explain DC motor drive using microcontroller.
  - (d) Give the constructional details of three phase squirrel cage induction motor.
  - (e) Enlist different parameters for selection of a drive.
- 5. Attempt any TWO of the following : 12**
- (a) With the help of neat circuit diagram, explain working of three phase semi converter drive. State equation of average armature voltage.
  - (b) For a single phase dual converter, answer the following :
    - (i) Describe its working with neat diagram.
    - (ii) Interpret with input/output waveforms.
  - (c) For a shaded pole motor, answer the following :
    - (i) Give the constructional details with neat diagram.
    - (ii) State any two applications.
- 6. Attempt any TWO of the following : 12**
- (a) Compare single phase SCR drives with three phase SCR drives. (Any six points)
  - (b) Describe the constructional details of universal motor with neat diagram. State any two advantages and applications of it.
  - (c) Identify the type of chopper for forward motoring & forward braking of DC motor. Justify your answer with neat sketch & waveforms.
-