

22629

24225

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) State the types of Electric Drives.
- (b) List the duty class of motor.
- (c) State the types of SCR controlled drives.
- (d) Draw only circuit diagram of three phase full wave converter.
- (e) List various methods for speed control of AC drives.
- (f) State any four advantages of microprocessor based drives.
- (g) State any two ratings and specifications of stepper motor.

2. Attempt any THREE of the following :

12

- (a) Describe with block diagram the basic elements of electric drive.
- (b) Draw circuit diagram of three phase dual converter using SCR, also draw its voltage and current waveforms.



- (c) Classify the Chopper drives. Draw only circuit diagram of class D chopper.
- (d) Explain with neat diagram the operation of Rotor resistance control using chopper of three phase induction motor.

3. Attempt any THREE of the following :

12

- (a) Describe the speed-torque characteristics of three phase induction motor.
- (b) Compare semi-converter drives and full converter drives on the basis of :
 - (i) Quadrant of operation
 - (ii) Regenerative braking
 - (iii) Power flow
 - (iv) Motor heating
- (c) Draw and describe class A chopper drive.
- (d) Explain with neat block diagram the operation of constant V/F control method.

4. Attempt any THREE of the following :

12

- (a) Draw and describe class B chopper drive.
- (b) State the sequence of stages and drives required in sugar mill.
- (c) Explain with neat block diagram the operation of stator voltage control method for three phase induction motor.
- (d) With the help of block diagram, explain Phase Lock Loop (PLL) control DC motor drive.
- (e) Draw and explain the block diagram of synchronous motor drive using microcontroller.

5. Attempt any TWO of the following :**12**

- (a) The speed of 10 HP, 230 volt, 1200 RPM separately excited DC motor is controlled by single phase full converter. The rated motor current is 40 A and armature resistance R_a is 0.25Ω . The motor voltage constant $K_a\phi = 0.182$ volt/rpm. For the value of $\alpha = 45^\circ$, calculate the following :
- (i) Average armature voltage
 - (ii) Back emf of the motor
 - (iii) Speed of motor
 - (iv) Torque of motor
- (b) State a chopper drive suitable for forward motoring and braking. Draw its circuit diagram and waveform.
- (c) Describe with diagram, the operation of solar and battery powered vehicles.

6. Attempt any TWO of the following :**12**

- (a) Draw circuit diagram of single phase semi-converter using SCR and describe its working with voltage and current waveforms.
- (b) Draw and describe four-Quadrant chopper drive.
- (c) State the sequence of stages involved in Textile Mill. Which type of drive/motor are used in each stage ?
-

