

22208

23242

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each Section on separate answer sheet.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

SECTION – I

1. Attempt any SIX of the following : 12
- (a) Define :
 - (i) M.M.F.
 - (ii) Reluctance
 - (b) Define :
 - (i) Power
 - (ii) Energy
 - (c) Define RMS value & form factor with respect to sinusoidal ac waveform.



- (d) Define Autotransformer.
- (e) State applications of single phase motor (any two).
- (f) Define :
 - (i) Peak factor
 - (ii) Power factor
- (g) State the working principle of single phase transformer.

2. Attempt any THREE of the following :

12

- (a) Draw circuit diagram and phaser diagram for series RL circuit. Write equation for voltage and current for it.
- (b) Explain working of single phase induction motor with neat sketch.
- (c) State (i) Faraday's laws of electromagnetic induction & (ii) Lenz's law.
- (d) For a single phase transformer, Give
 - (i) any two types
 - (ii) any two losses
 - (iii) any two applications
 - (iv) transformation ratio

3. Attempt any TWO of the following :

12

- (a) (i) Define Dynamically induced emf & statically induced emf. Give one example of each.
- (ii) Define self & mutual inductance & give equation of each.

- (b) (i) State relation between V_1 & V_{ph} in case of 3ϕ star connection. If a line voltage of 400 V is applied across star connected load, then find phase voltage.
- (ii) In a R-L Series circuit $R = 15\Omega$ and $L = 0.005$ H. When a 220 V, 50 Hz, 1ϕ AC is applied to it, calculate current flowing through the circuit.
- (c) (i) State principle of single phase transformer.
- (ii) Derive an emf equation of single phase transformer.

SECTION – II

4. Attempt any FIVE of the following : 10

- (a) Compare active & passive components (2 pts).
- (b) Define (i) PIV (ii) Efficiency of rectifiers.
- (c) State types of BJT & their symbols.
- (d) State different types of signals.
- (e) State any two types of filters.
- (f) State cut-off & active region of transistor.

5. Attempt any THREE of the following : 12

- (a) Give symbol of
- (i) Capacitor
- (ii) Inductor
- Give their specifications.
- (b) For an LED –
- (i) draw symbol
- (ii) draw its characteristics
- (iii) write any two applications

- (c) Explain working of fullwave rectifier with waveforms.
- (d) Find value of resistor from the given colour code :
 - (i) Orange, Orange, Orange, Gold
 - (ii) Brown, Black, Orange, Silver

6. Attempt any TWO of the following :

12

- (a)
 - (i) Draw waveform of different signals.
 - (ii) Explain time & frequency domain representation of signals.
 - (b) State need of filter. Explain π filter with neat sketch.
 - (c)
 - (i) Explain input & output characteristics of CE configuration.
 - (ii) Give applications of transistors.
-