

22212

23242

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
  - (7) Preferably, write the answers in sequential order.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Define Current. State its unit.
- (b) State Ohm's law.
- (c) Define Capacitance. State its unit.
- (d) Define magnetomotive force (m.m.f.) and reluctance in magnetic circuit.
- (e) State the relation between magnetic flux density and magnetic field intensity for magnetic material.
- (f) State Lenz's law.
- (g) State any two types of inductors.



**2. Attempt any THREE of the following :** **12**


- (a) Explain with neat diagram Ideal voltage source and Ideal current source.
- (b) Distinguish between linear and non-linear circuits. State one example of each.
- (c) State the difference between breakdown voltage and dielectric strength of dielectric material. Draw the charging and discharging curves for a capacitor (C) connected to d.c. source through a resistance (R) ohm.
- (d) Derive the equation of energy stored in a capacitor.

**3. Attempt any THREE of the following :** **12**

- (a) State the effect of electric current observed in electric bell. State how this effect is produced.
- (b) Explain the effect of temperature on resistance of Conducting and Insulating materials.
- (c) Distinguish between unilateral circuit and bilateral circuit. State one example of each.
- (d) State any four type of capacitors with their applications.


**4. Attempt any THREE of the following :** **12**

- (a) An electric iron of rating 230 V, 500 W is used daily for eight hours. Calculate the number of units consumed by it in the month of 30 days. Also determine the energy charges at a rate of ₹ 7 per unit.
- (b) Calculate the equivalent resistance between point A and D. Also calculate current drawn by source.

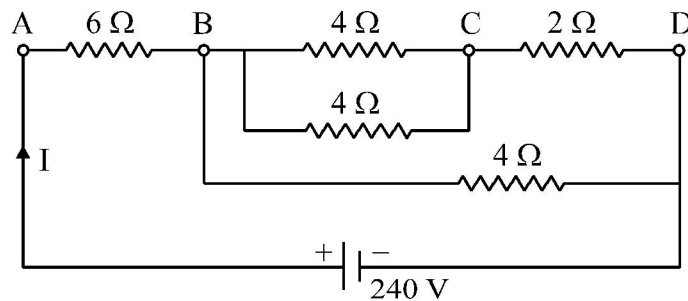

**Figure No. 1**

- (c) Determine the current in  $10\Omega$  resistance by applying Kirchoff's laws.

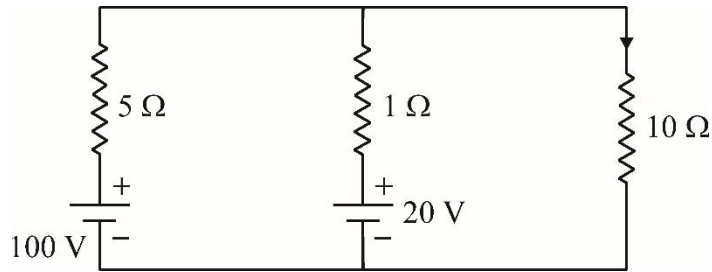

**Figure No. 2**

- (d) Derive the formula for equivalent capacitance ( $C_{eq.}$ ) for three capacitors  $C_1$ ,  $C_2$  and  $C_3$  connected in parallel.
- (e) Three capacitors  $20\ \mu\text{F}$ ,  $30\ \mu\text{F}$  and  $50\ \mu\text{F}$  are connected in parallel across  $250\ \text{V}$  d.c. supply.

Calculate :

- (i) Equivalent capacitance
- (ii) Charge on  $20\ \mu\text{F}$  capacitor

**5. Attempt any TWO of the following :**

**12**

- (a) Draw B-H (Mag. Flux density V/s. Mag. Field intensity) curve for magnetic and non-magnetic material. Draw Hysteresis loop for hard steel and soft steel.
- (b) An iron ring of mean circumference of  $70\ \text{cm}$  and cross sectional area of  $50\ \text{mm}^2$  is uniformly wound by wire of  $1000$  turns carrying  $1.6\ \text{A}$  current. Calculate the value of flux and flux density.  
(Assume  $\mu_r = 1000$ ). Also calculate mmf and field intensity.
- (c) A coil of  $1000$  turns is placed in a changing magnetic field. The magnetic flux linking with the coil is changed from  $0.5\ \text{mWb}$  to  $0.1\ \text{mWb}$  in  $0.04$  second. Calculate the emf induced in it. State the nature of the induced emf.

**6. Attempt any TWO of the following :**

**12**

- (a) Compare electric circuit with magnetic circuit for any six points.

**P.T.O.**

- (b) (i) A coil has an inductance of 0.1 H. The current in the coil is changed from 10A to 5A in 0.01 sec. Calculate the emf induced in it.
- (ii) Compare statically induced emf and dynamically induced emf.
- (c) A field winding of a d.c. electromagnet is wound with 160 turns. Its resistance is 25 ohm and connected to 250 V d.c. supply. The magnetic flux produced by current in coil links to coil and is 0.007 Wb. Calculate the self inductance of the coil and energy stored in magnetic field.
-