

22225

23242

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Draw the symbol of resistor and inductor.
- (b) List any two advantages of JFET.
- (c) Write two applications of Zener diode.
- (d) Define transducers and name two passive transducers.
- (e) State two advantages of Integrated Circuits.
- (f) Draw the symbol of N & P channel MOSFET.
- (g) Draw symbol of LED and Zener diode.

**2. Attempt any THREE of the following :**

**12**

- (a) Determine the value of resistance with following colour code :
  - (i) Red, Black, Brown, Gold
  - (ii) Brown, Red, Black, Silver



- (b) Draw and explain forward biased V-I characteristic of P-N Junction diode.
- (c) Draw circuit diagram of transistor as switch and describe its working.
- (d) A JFET has a drain current of 5 mA. If  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(OFF)} = -6 \text{ V}$ . Find value of (i)  $V_{GS}$  (ii)  $V_P$

**3. Attempt any THREE of the following :**

**12**

- (a) Draw the circuit diagram and describe the working of transistor as an amplifier.
- (b) Draw neat and labelled DC load line of transistor. Mention importance of Q point if it is at center and at cutoff.
- (c) Define rectification. List types of rectifiers.
- (d) Draw a sketch and describe the working of potentiometer as a resistive transducer.


**4. Attempt any THREE of the following :**

**12**

- (a) In CE configuration if  $\beta = 100$ , leakage current  $I_{CEO} = 100 \mu\text{A}$ , base current is 0.2 mA, determine collector current  $I_C$  and emitter current  $I_E$ .
- (b) Draw block diagram of regulated power supply. Draw the waveforms at the output of each block.
- (c) Draw the constructional details of n-channel JFET and describe the working principle.
- (d) State any four selection criteria of transducer.
- (e) Draw circuit diagram of bridge full wave rectifier and describe its working.

**5. Attempt any TWO of the following :****12**

- (a) Draw output characteristic of CE configuration. Define  $\alpha$  and  $\beta$  of transistor.
- (b) List types of filter. Draw the circuit diagram of C filter and describe its working.
- (c) (i) List types of signal.  
(ii) In the waveform shown in Fig. (1), state its (i) peak amplitude (ii) frequency.

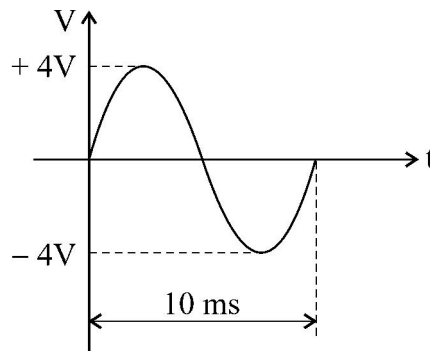**Fig. (1)****6. Attempt any TWO of the following :****12**

- (a) (i) Differentiate BJT and JFET (any three points).  
(ii) Differentiate JFET and MOSFET (any three points).
- (b) Draw the drain characteristic and transfer characteristic of JFET.
- (c) Draw construction of photo diode and phototransistor. State any two difference between them.

