

22324

23242

3 Hours / 70 Marks

Seat No. 

--	--	--	--	--	--	--	--

- 
- Instructions* – (1) All Questions are *Compulsory*.  
(2) Answer each next main Question on a new page.  
(3) Illustrate your answers with neat sketches wherever necessary.  
(4) Figures to the right indicate full marks.  
(5) Assume suitable data, if necessary.  
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.  
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. **Attempt any FIVE of the following:** **10**
- a) Draw impedance triangle for R-L series circuit.
  - b) State relations of star connection.
  - c) Define :
    - i) RMS value
    - ii) Average value
  - d) Define conductance and susceptance related to AC circuit and state their units.
  - e) Distinguish clearly between loop and mesh.
  - f) State the value of internal resistance of
    - i) Ideal voltage source and
    - ii) Ideal current source
  - g) State maximum power transfer theorem.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) With neat diagram, explain the phasor representation of sinusoidal quantity.
  - b) For a parallel circuit consisting of an inductive branch (R-L) in parallel with a capacitive branch (RC), draw phasor diagram and derive equation for resonant frequency.
  - c) With the help of neat phasor diagram, derive the relationship between line and phase values of voltage in balanced delta connection.
  - d) Give the expression for star to delta and delta to star transformation.
- 3. Attempt any THREE of the following:** **12**
- a) For series R-L-C circuit, draw neat circuit diagram. State the conditions for RLC series circuit. Draw phasor diagram and voltage triangle impedance triangle for any one condition.
  - b) State any four properties of Parallel Resonance.
  - c) With neat labeled diagram, explain unbalanced star connected load.
  - d) With neat circuit diagram, explain how to convert a practical voltage source into an equivalent practical current source.
  - e) Explain the concept of “duality” in electric circuit with one example.
- 4. Attempt any THREE of the following:** **12**
- a) A series R-L-C circuit has  $R = 5\Omega$ ,  $L = 10 \text{ mH}$  and  $C = 15 \mu\text{F}$ . Calculate
    - i) Resonant frequency
    - ii) Q-factor of the circuit
    - iii) Bandwidth
    - iv) Voltage magnification
  - b) Explain the “Current Magnification” in parallel resonant circuit consisting of inductive branch (RL) in parallel with a pure capacitor (C). Derive equation for it.

- c) Draw waveform of three-phase voltages. Draw phasor diagram for these voltages. Write equations for instantaneous values of these voltages. Express these voltages in polar form.
- d) State and explain "Reciprocity theorem".

5. Attempt any TWO of the following:

12

- a) A coil having resistance of  $5 \Omega$  and an inductance of  $0.2 \text{ H}$  is connected in parallel with a series combination of  $10 \Omega$  resistor and  $80 \mu\text{F}$  capacitor. If supply voltage is  $230 \text{ V}$ ,  $50 \text{ Hz}$ , determine :
- Total circuit impedance
  - Total current taken by the circuit
  - Power factor of the circuit
  - Branch currents
  - Power consumed by the circuit
- b) Using mesh analysis, find current in  $5 \Omega$  resistor in the network shown in Fig. No. 01.

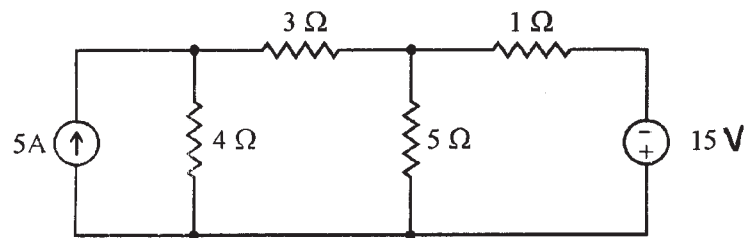


Fig. No. 01.

- c) Find the current in  $8 \Omega$  resistor in the network shown in Fig. No. 02. by using Thevenin's theorem.


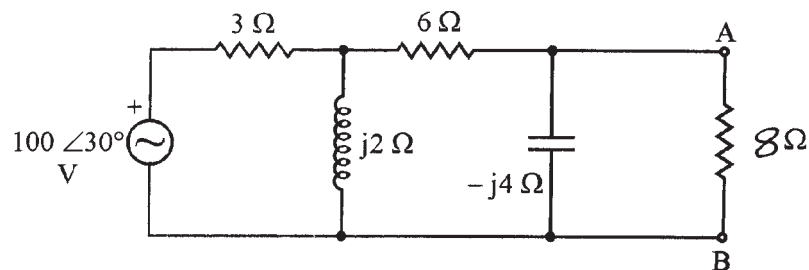


Fig. No. 02.

6. Attempt any TWO of the following:

12

- a) For a series R-L-C circuit consisting of  $R = 5\Omega$ ,  $L = 0.01\text{ H}$  and  $C = 10\ \mu\text{F}$  supplied with 230 V, 50 Hz supply, determine -
- Circuit impedance
  - Circuit current
  - Circuit power factor
  - Active power
  - Reactive power
  - Apparent power
- b) A star connected capacitive load is supplied from 3 phase, 415 V, 50 Hz supply. If the line current is 15 A and total 3 phase power taken from supply is 30 kW, find
- Power factor
  - Resistance in each phase
  - Capacitance in each phase
- c) Determine the voltage 'V' across  $5\ \Omega$  resistor in network shown in Fig. No. 03. using superposition theorem.

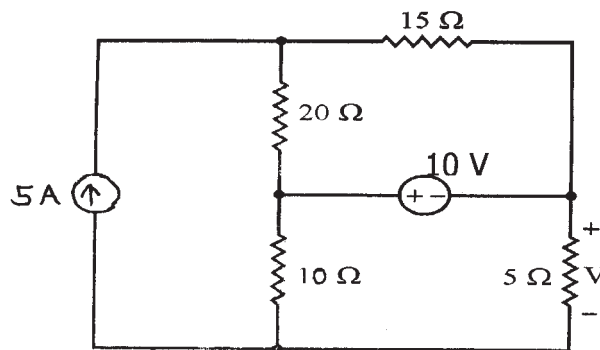

**Fig. No. 03.**

---