

22326

23242

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Draw the symbol of power transistor and IGBT.
- (b) State the applications of IGBT (any two).
- (c) Draw the symbol of PUT and DIAC.
- (d) Give the types of gate triggering.
- (e) Define :
  - (i) Conduction angle
  - (ii) Firing angle
- (f) State the need of UPS.
- (g) Define transfer time and back up time of UPS.



**2. Attempt any THREE of the following : 12**

- (a) Describe with neat sketch the constructional details of IGBT.
- (b) Interpret the V-I characteristics of UJT with sketch.
- (c) Explain with sketch the operation of class C commutation.
- (d) Explain with circuit diagram of single phase mid-point controlled rectifier with R-load.

**3. Attempt any THREE of the following : 12**

- (a) Draw a neat labelling V-I characteristics of SCR and explain the region.
- (b) Explain the operation of UJT relaxation oscillator circuit with diagram.
- (c) Draw a neat diagram of 1  $\phi$  half wave controlled rectifier with RL load. Give its operation.
- (d) Draw the circuit diagram of battery charger using SCR and explain its working.

**4. Attempt any THREE of the following : 12**

- (a) Give comparison of SCR & TRIAC.
- (b) Explain the operation of R triggering circuit with a diagram.
- (c) Explain with circuit diagram the operation of single phase full bridge controlled rectifier with R load.
- (d) Explain speed control of the motor by using TRIAC with the help of circuit diagram.
- (e) Explain working of AC circuit breaker using SCR with circuit diagram.

**5. Attempt any TWO of the following :****12**

- (a) Draw symbols and V-I characteristics of the following devices :
- (i) LASCR
  - (ii) DIAC
  - (iii) PUT
  - (iv) SCS
  - (v) TRIAC
  - (vi) UJT
- (b) For a class D commutation, answer the following :
- (i) Explain the operation with a circuit diagram.
  - (ii) Interpret with waveforms.
- (c) Explain the modes of operations in TRIAC with quadrant diagram.

**6. Attempt any TWO of the following :****12**

- (a) 1  $\phi$  half controlled rectifier supplied with voltage  $V = 300 \sin 314 t$ , and load resistance is  $100 \Omega$  find :
- (i) Average output DC voltage
  - (ii) Load current (for  $\alpha = 60^\circ$  and  $\alpha = 100^\circ$ )
- (b) Draw full bridge and half bridge configuration with common cathode.
- (c) Explain the operation of SMPS with a neat block diagram.
-

