

22329

23242

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Define the following terms related to single stage common emitter amplifier
 - (i) Voltage gain
 - (ii) Bandwidth
- (b) List the advantages of class B push pull amplifier over class A amplifier (any two).
- (c) State advantages of negative feedback (any four).
- (d) State the need of oscillator.
- (e) State the condition in $(1 + A\beta)$ which a feedback amplifier must satisfy in order to be stable.
- (f) State the working principle of SMPS. Also state any two merits of SMPS.
- (g) List the applications of Direct coupled amplifier (any two).

2. Attempt any THREE of the following :

12

- (a) Answer the following questions with respect to double tuned voltage amplifier :
 - (i) Draw the circuit diagram for it.
 - (ii) State the advantages of double tuned voltage amplifier.
- (b) Describe a single stage amplifier with current series feedback.
- (c) Draw the functional block diagram of IC 723. State any two features of IC 723.



- (d) In a simple UJT sweep circuit, the resistance and capacitance are $100\text{ K}\Omega$ and $0.4\ \mu\text{F}$ respectively. The ratio of the peak-point voltage and the supply voltage is 0.57. Find the frequency of sweep.

3. Attempt any THREE of the following :

12

- (a) Differentiate between voltage amplifier and power amplifier with respect to
 (i) Definition (ii) Input resistance
 (iii) Current gain (β) (iv) Type of coupling
- (b) Describe transformer coupled Class A power amplifier with the help of circuit diagram and state the expression for dc power input, ac power output and efficiency.
- (c) Study the **figure 1** of RC phase shift oscillator and answer the following questions :

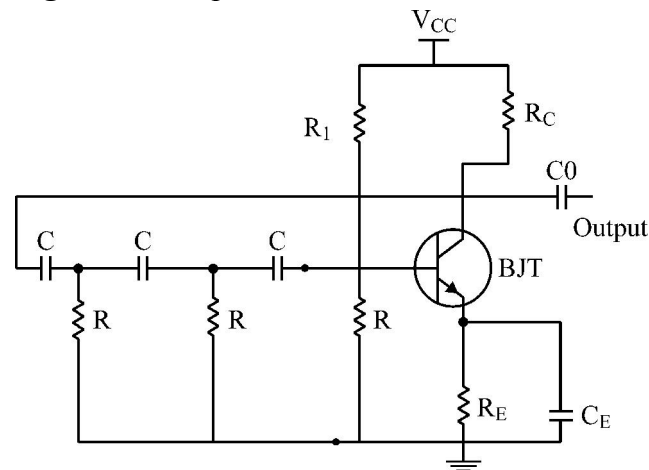


Fig. No. 1

- (i) State the working principle of it.
- (ii) State the expression for the frequency of oscillations and the minimum gain of the amplifier for sustained oscillations.
- (d) Study the **figure 2** and answer the following questions :

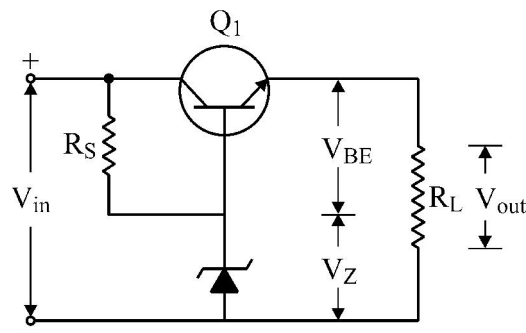


Fig. No. 2

- (i) Identify the circuit.
- (ii) How this circuit will regulate the output voltage if load is changed ?

4. Attempt any THREE of the following :

12

- Describe Class-AB push pull power amplifier with the help of circuit diagram.
- Describe two stage transformer coupled amplifier with the help of circuit diagram.
- Describe voltage shunt feedback amplifier with the help of circuit diagram.
- The ac equivalent circuit of a crystal has values : $L = 1 \text{ H}$, $C = 0.01 \text{ pF}$, $R = 1000 \Omega$ and $C_m = 20 \text{ pF}$. Calculate series and parallel resonant frequencies of the crystal.
- Study the **figure 3** of series regulator and answer following questions :

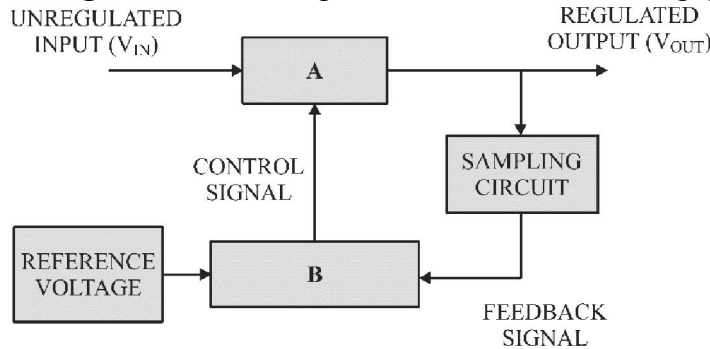


Fig. No. 3

- Identify the blocks A and B.
- State the function of sampling circuit and reference voltage.

5. Attempt any TWO of the following :

12

- Describe the working of Miller Sweep circuit with the help of circuit diagram. Also draw the input and output waveforms.
- Study the **figure 4** of direct coupled class A power amplifier and answer following questions :

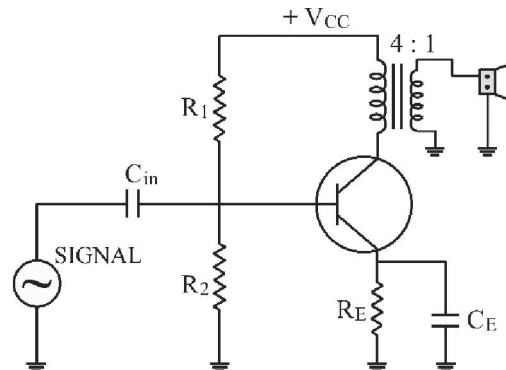


Fig. No. 4

- Draw the graphical representation to show the operation in terms of a.c. load line.
- State the functions of C_{in} and C_E .
- List the advantages and disadvantages of it (any two of each).

- (c) Describe the working principle of common source FET amplifier with the help of circuit diagram. Also draw the a.c. equivalent circuit of a common source amplifier.

6. Attempt any TWO of the following :

12

- (a) Study the **figure 5** and answer following questions :

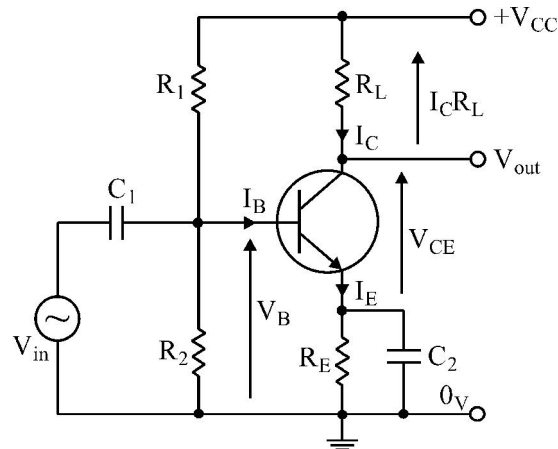


Fig. No. 5

- (i) Identify and redraw the circuit diagram.
 - (ii) State the functions of R_1 , R_2 , C_1 and C_2 .
 - (iii) Draw the input and output waveforms.
- (b) Justify that the negative feedback amplifier increases bandwidth, decreases noise and decreases distortion.
- (c) Differentiate between class-B and class-AB power amplifier with respect to
- (i) Angle of conduction
 - (ii) Position of Q point
 - (iii) Distortion in output voltage
 - (iv) Efficiency
 - (v) Power dissipation in transistor and
 - (vi) Application
-