

22524

23242

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Draw diagram of:
 - i) Busbar reactor
 - ii) Generator reactor
 - b) Give any two advantages of SF6 C.B.
 - c) Draw the symbol and state function of C.B.
 - d) Define Plug setting multiplier and Time setting multiplier.
 - e) Write any two different fault occurs in alternator.
 - f) What do you mean by incipient faults.
 - g) List any two faults occurs in 3ϕ I.m.

P.T.O.

- 2. Attempt any THREE of the following: 12**
- a) Write any eight causes of fault occurrence in the power system.
 - b) Explain construction of H.R.C. Fuse.
 - c) Draw neat circuit diagram of solenoid type relay.
 - d) State the requirement of transmission line protection.
- 3. Attempt any THREE of the following: 12**
- a) Write essential features of good protective system.
 - b) Distinguish between C.B. and Isolator.
 - c) Draw neat sketch of Buchholz relay.
 - d) Draw neat sketch of single phase preventer for 3- ϕ Induction Motor.
- 4. Attempt any THREE of the following: 12**
- a) What is reactor? Classify reactors on the basis of their location.
 - b) State the specification of CT and PT as protective transformers.
 - c) Draw neat sketch of percentage differential protection of a transformer.
 - d) Explain the principle of time graded protection of feeders using IDMT over current relays.
 - e) Explain with a neat sketch pilot wire protection scheme applied to transmission line.

5. Attempt any TWO of the following:**12**

- a) Draw and explain a neat circuit diagram of vacuum circuit breaker. State any two advantages of it.
- b) Determine the time of operation of a 1A, 3 seconds over current relay having plug setting of 125% and a time multiplier of 0.6. The supplying CT is rated 400: 1A and fault current is 400A. The relay characteristics is as given below.

PSM	1.3	2	4	8	10	20
Time of operation in seconds	30	10	5	3.3	3	2.2

- c) A - 3 phase 33/6.6 KV, star - delta transformer is protected by merz price circulating current relay if the CTs on the low voltage side have a ratio of 300/5. Determine the ratio of CTs on the high voltage side. Draw a neat diagram and indicate the values at appropriate places.

6. Attempt any TWO of the following:**12**

- a) For a 10 MVA, 132 KV / 6.6 KV power transformer with delta-star connections, obtain CT ratio for the differential protection scheme to circulate a current of 5A in the pilot wires. Draw schematic diagram for the given configuration.
- b) Explain with a neat sketch the operation of attracted armature type relay. Also give its two merits and demerits.
- c) Draw the construction diagram of ELCB and explain how ELCB gives protection against earth leakage fault.
