

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :** (1) All Questions are *compulsory*.
 (2) Answer each next main Question on a new page.
 (3) Illustrate your answers with neat sketches wherever necessary.

Marks**1. Attempt any TEN :****20**

- (a) Convert (i) $(28.56)_{10} = (?)_2$ (ii) $(372)_8 = (?)_{10}$
- (b) Draw logic diagram of tristate buffer with active low enable and active high enable.
- (c) Draw truth table for logic gates represented by following IC's :
- (i) IC7400
 (ii) IC7402
- (d) State triggering methods in digital circuits (any two)
- (e) Identify SOP and POS equations :
- (i) $AB + CD$
 (ii) $(A + B)(C + D)$
- (f) Differentiate between RAM & ROM (2 points)
- (g) List any two non-weighted codes.
- (h) Add the binary numbers (1011) & (1100)
- (i) Find Y_1 & Y_2 for Fig. 1 & Fig. 2 respectively.

**Fig. 1****Fig. 2**

- (j) Define universal shift register.
- (k) Draw symbol of TFF & write its truth table.
- (l) Implement given logic equation using basic gates $Y = A\bar{B} + \bar{A}B$.
- (m) Prove that $AB + A\bar{B} = A$, using laws of Boolean Algebra.
- (n) Draw 3 variable K-map format.

2. Attempt any FOUR :

16

- (a) Subtract $(1101)_2$ from $(1110)_2$ using 1's & 2's complement method.
- (b) Two square waves of 4 kHz & 8 kHz are applied as the inputs of AND gate & NAND gate. Draw the output waveform in each case.
- (c) Design 1 : 32 De MUX using 1 : 8 De MUX.
- (d) Write down excitation table of JK & DFF.
- (e) Describe 3 bit R-2R ladder DAC with neat diagram.
- (f) Compare Static RAM & Dynamic RAM (any 4 points)

3. Attempt any FOUR :

16

- (a) Perform the following operations :
 - (i) $(1001)_2 \times (1101)_2$
 - (ii) $(1001)_2 / (11)_2$
- (b) Compare TTL, ECL & CMOS logic families (any 4 points)
- (c) Realize following expression using MUX :

$$f = \sum_m (0, 3, 5, 9, 11, 15)$$
- (d) Describe operation of PISO shift register with neat circuit diagram.
- (e) Compare single slope ADC with dual slope ADC w.r.t.
- (f) Draw organization of 4×4 memory and label it.

4. Attempt any FOUR :**16**

(a) Perform BCD addition :

(i) $(45)_{10} + (33)_{10}$

(ii) $(57)_{10} + (26)_{10}$

(b) Define following characteristics of logic families :

(i) fan in

(ii) fan out

(iii) Propagation delay

(iv) Power dissipation

(c) Design 32 : 1 MUX using 16 : 1 MUX.

(d) Draw logic diagram for 3 bit up-down counter.

(e) Simplify given SOP equation using K map

$$Y = \sum_m (0, 1, 2, 3, 5, 7, 8, 9, 11)$$

(f) Write advantages (any 3) and disadvantage (any 1) of dual slope ADC.

5. Attempt any FOUR :**16**

(a) Define priority encoder. Draw the generalised block diagram of priority encoder.

(b) Compare R-2R ladder DAC with weighted resistor DAC (any 4 points)

(c) Explain the operation of TTL logic NAND gate. Draw the circuit diagram.

(d) Design MOD-6 counter using IC 7490.

(e) Compare combinational circuit with sequential circuit (any 4 points)

(f) Compare EPROM and EEPROM (any four points).

P.T.O.

6. Attempt any FOUR :**16**

- (a) Implement $Y = f(A, B, C) = \sum_m(0, 1, 2, 6, 7)$ using suitable DeMUX & logic gates.
 - (b) State the use of preset and clear terminal in a Flip-flop.
 - (c) Draw 3 bit synchronous up counter. Write its truth table.
 - (d) Draw 4 bit weighted resistor DAC and give expression for output voltage.
 - (e) Describe successive approximation ADC with neat diagram.
 - (f) Describe the operation of 1 dig it BCD adder using IC 7483.
-