

WINTER-2018 EXAMINATION

Subject Code:

22221

Model Answer

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills)
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub	Answer	Marking	
	Q. N.		Scheme	
1.		Attempt any <u>FIVE</u> of the following:	10 M	
	a	State Faraday's laws of Electromagnetic induction.		
		Ans:		
		First Law: Whenever change in the magnetic flux linked with a coil or conductor, an		
		EMF is induced in it. OR Whenever a conductor cuts magnetic flux, an EMF is induced	01	
		in conductor.		
		Second Law: The Magnitude of induced EMF is directly proportional to (equal to) the		
		rate of change of flux linkages.	01	
		a = -N da		
		$e = \frac{dt}{dt} d\psi$		
	b	Define: (i) Amplitude (ii) Cycle with reference to AC waveform.		
		Ans:		
		1. Amplitude: It is defined as the maximum or peak value attained by an	01	
		alternating quantity during its positive or negative half cycle.		
		2. Cycle with reference to AC waveform: A complete set of variation of an		
		alternating quantity which is repeated at regular interval of time is called as a	01	
		cycle. OR Each repetition of an alternating quantity recurring at equal intervals is		
		known as a cycle.		
	c	Define: (i) Phase (ii) Phase Difference.		
		Ans:		
		1. Phase: It is the instantaneous angle covered by a sinusoidal waveform with	01	
		respect to positive zero crossing.		
		2. Phase Difference: It is the difference, expressed in degrees or radians, between	01	
		two waves having the same frequency and referenced to the same point in time.		
	d	Define: (i) Phase Voltage (ii) Line Voltage with reference to polyphase A.C. circuits.		
		Ans: Phase Voltage: The RMS value of the voltage between any lines to neutral point is	01	
		called as phase voltage.		
		Line Voltage: The RMS value of the voltage between any two lines is called as line	01	
		voltage.		



	e	State how to reverse the rotation of 3-phase induction motor.				
		Ans:				
		Di	rection of rotation of a three phase	I.M. can be changed by interchanging any	02	
		two supp	ly terminals i.e. by reversing the dire	ction of rotating magnetic field.		
	f	State any two applications of DC servomotor.				
		Ans:				
		1) C	1) CNC machines			
		2) R	obotic arms		02	
		3) Pi	ck and Place machines			
		4) Auto focus mechanism of camera				
		5) A	ntenna position control			
	g	State the	principle of operation of ELCB.			
		Ans:				
		Operatio	on of ELCB (Earth Leakage Circui	t Breaker) :		
			It works on principle of relaying w	hen the current in the earth path exceeds a		
		set valu	e. Under normal conditions (IL-IN)	= II is very low or nearly zero. The CT	02	
		surround	ing the phase and neutral senses the	differential current under earth fault and	02	
		register	the CB to operate (open). The	is value exceeds a preset value then the		
		FLCB	pens	is value exceeds a preset value, then the		
		ELCD 0	pens.			
			The ELCB detects fault currents fro	by live to the Earth (ground) wire within		
		the insta	llation it protects. If sufficient voltage	ge appears across the ELCB's sense coil, it		
		will sw	itch off the power, and remain off	until manually reset. A voltage-sensing		
		ELCB d	oes not sense fault currents from live	FI CB does not sense fault currents from live to any other earthed body		
		Attempt any THREE of the following:				
2.		Attempt	any THREE of the following:	to any other cartied body.	12 M	
2.	a	Attempt Compare	any <u>THREE</u> of the following: e electric circuit with magnetic cir	cuit on the basis of any two similarities	12 M	
2.	a	Attempt Compare and any	any <u>THREE</u> of the following: e electric circuit with magnetic cir two differences. Any Four Point ex	cuit on the basis of any two similarities spected : (1 Mark each)	12 M	
2.	a	Attempt Compare and any Ans:	any <u>THREE</u> of the following: e electric circuit with magnetic cir two differences. Any Four Point ex	rcuit on the basis of any two similarities spected : (1 Mark each)	12 M	
2.	a	Attempt Compare and any Ans: Sr.	any <u>THREE</u> of the following: e electric circuit with magnetic cir two differences. Any Four Point ex Electric circuit	cuit on the basis of any two similarities spected : (1 Mark each) Magnetic circuit	12 M	
2.	a	Attempt Compare and any Ans: Sr. No.	any <u>THREE</u> of the following: e electric circuit with magnetic cir two differences. Any Four Point ex Electric circuit	rcuit on the basis of any two similarities spected : (1 Mark each) Magnetic circuit	12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1	any <u>THREE</u> of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is	recuit on the basis of any two similarities spected : (1 Mark each) Magnetic circuit The magnetic circuit in which	12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1	any <u>THREE</u> of the following: e electric circuit with magnetic cir two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current.	could only only only only only only only only	12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1 2	any <u>THREE</u> of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the	recuit on the basis of any two similarities pected : (1 Mark each) Magnetic circuit The magnetic circuit in which magnetic flux flow MMF is the driving force in the	12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1 2	any THREE of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts.	recuit on the basis of any two similarities spected : (1 Mark each) Magnetic circuit The magnetic circuit in which magnetic flux flow MMF is the driving force in the magnetic circuit. The unit is ampere	12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1 2	any <u>THREE</u> of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts.	recuit on the basis of any two similarities pected : (1 Mark each) Magnetic circuit The magnetic circuit in which magnetic flux flow MMF is the driving force in the magnetic circuit. The unit is ampere turns.	12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1 2 3	any <u>THREE</u> of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric	recuit on the basis of any two similarities pected : (1 Mark each) Magnetic circuit The magnetic circuit in which magnetic flux flow MMF is the driving force in the magnetic circuit. The unit is ampere turns. There is flux φ in the magnetic circuit	12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1 2 3	any THREE of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric circuit which is measured in	<th colum<="" column="" th=""><th>12 M</th></th>	<th>12 M</th>	12 M
2.	a	Attempt Compare and any Ans: Sr. No. 1 2 3	any <u>THREE</u> of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric circuit which is measured in amperes.		12 M	
2.	a	Attempt Compare and any Ans: Sr. No. 1 2 3 4	any THREE of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric circuit which is measured in amperes. The flow of electrons decides the	<th column="" control="" coul<="" could="" th=""><th>12 M 04</th></th>	<th>12 M 04</th>	12 M 04
2.	a	Attempt Compary and any Ans: Sr. No. 1 2 3 4	any <u>THREE</u> of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric circuit which is measured in amperes. The flow of electrons decides the current in conductor.	rcuit on the basis of any two similarities pected : (1 Mark each) Magnetic circuit The magnetic circuit in which magnetic flux flow MMF is the driving force in the magnetic circuit. The unit is ampere turns. There is flux φ in the magnetic circuit which is measured in the weber. The number of magnetic lines of force decides the flux.	12 M 04	
2.	a	Attempt Compary and any Ans: Sr. No. 1 2 3 4 5	any THREE of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric circuit which is measured in amperes. The flow of electrons decides the current in conductor. Resistance (R) opposes the flow	<th column="" control="" coul<="" could="" td=""><td>12 M 04</td></th>	<td>12 M 04</td>	12 M 04
2.	a	Attempt Compary and any Ans: Sr. No. 1 2 3 4 5	any THREE of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric circuit which is measured in amperes. The flow of electrons decides the current in conductor. Resistance (R) opposes the flow of the current.	rcuit on the basis of any two similarities pected : (1 Mark each) Magnetic circuit The magnetic circuit in which magnetic flux flow MMF is the driving force in the magnetic circuit. The unit is ampere turns. There is flux φ in the magnetic circuit which is measured in the weber. The number of magnetic lines of force decides the flux. Reluctance (S) is opposed by magnetic path to the flux. The Unit is ampere turn/weber	12 M 04	
2.	a	Attempt Compary and any Ans: Sr. No. 1 2 3 4 5	any <u>THREE</u> of the following: e electric circuit with magnetic cin two differences. Any Four Point ex Electric circuit Path traced by the current is known as electric current. EMF is the driving force in the electric circuit. The unit is Volts. There is a current I in the electric circuit which is measured in amperes. The flow of electrons decides the current in conductor. Resistance (R) opposes the flow of the current. The unit is Ohm	<th column="" current="" iteration="" of="" only="" sec<="" second="" th="" the=""><th>12 M 04</th></th>	<th>12 M 04</th>	12 M 04
2.	a	Attempt Compary and any Ans: Sr. No. 1 2 3 4 5 6	any THREE of the following:e electric circuit with magnetic cincuit wo differences. Any Four Point exElectric circuitPath traced by the current is known as electric current.EMF is the driving force in the electric circuit. The unit is Volts.There is a current I in the electric circuit which is measured in amperes.The flow of electrons decides the current in conductor.Resistance (R) opposes the flow of the current.The unit is OhmR= ρ .1/a.Directly proportional to 1	<th be="" be<="" column="" control="" could="" td="" the=""><td>12 M 04</td></th>	<td>12 M 04</td>	12 M 04
2.	a	Attempt Compare and any Ans: Sr. No. 1 2 3 4 5 6	any THREE of the following:e electric circuit with magnetic cintwo differences. Any Four Point exElectric circuitPath traced by the current is known as electric current.EMF is the driving force in the electric circuit. The unit is Volts.There is a current I in the electric circuit which is measured in amperes.The flow of electrons decides the current in conductor.Resistance (R) opposes the flow of the current.The unit is OhmR $= \rho$. $1/a$.Directly proportional to 1.Inversely proportional to 1.	<th be="" be<="" column="" control="" could="" td="" the=""><td>12 M 04</td></th>	<td>12 M 04</td>	12 M 04
2.	a	Attempt Compary and any Ans: Sr. No. 1 2 3 4 5 6	any THREE of the following:e electric circuit with magnetic cintwo differences. Any Four Point exElectric circuitPath traced by the current is known as electric current.EMF is the driving force in the electric circuit. The unit is Volts.There is a current I in the electric circuit which is measured in amperes.The flow of electrons decides the current in conductor.Resistance (R) opposes the flow of the current.The unit is OhmR= p.I/a.Directly proportional to 1.Inversely proportional to a.Depends on nature of material	<th be="" be<="" column="" control="" could="" td="" the=""><td>12 M 04</td></th>	<td>12 M 04</td>	12 M 04
2.	a	Attempt Compary and any Ans: Sr. No. 1 2 3 4 5 6	any THREE of the following:e electric circuit with magnetic cintwo differences. Any Four Point exElectric circuitPath traced by the current is known as electric current.EMF is the driving force in the electric circuit. The unit is Volts.There is a current I in the electric circuit which is measured in amperes.The flow of electrons decides the current in conductor.Resistance (R) opposes the flow of the current.The unit is OhmR= p.I/a.Directly proportional to 1.Inversely Proportional to 1.	<th be="" calculate="" column="" could="" for="" of="" proper<="" properties="" td="" the=""><td>12 M 04</td></th>	<td>12 M 04</td>	12 M 04







	As shown in figure, flux increases from its zero value to maximum value Øm in	
	one quarter of the cycle (i.e. ¹ / ₄ f) sec	
	1.Average rate of change of flux	1/2
	φm	1/4
	2. $\overline{1/4f} = 4 f \phi m \text{ (wb/sec)}$	
	Rate of Change of flux per turn means induced emf, If flux various sinusoidally then r.m.s value of induced emf is obtained by multiplying the average value with form factor	
	$\frac{R.M.S Value}{= -1.11}$	1/2
	average value	
	R.M.S. value of emf /turn = 1.11 x 4 f \emptyset m = 4.44 f \emptyset m	1/2
	R.M.S value in the whole primary winding	1/2
	= (induced emf / turn) x No. of primary turns	
	$E_1 = 4.44 \text{ f} \ \phi m N 1$	
	$\mathbf{E}_1 = 4.44 \mathbf{f} \mathbf{BmAN}_1$	01
	$OR E_1 = 4.44 \ \phi m \ f N_1$	
	R.M.S. value in the secondary winding	01
	$\mathbf{E}_2 = 4.44 \text{ f Bm A N}_2$	U1
	$\begin{array}{c} \mathbf{OR} \qquad \mathbf{E}_1 = 4.44 \ \phi m \ \mathbf{IN}_2 \end{array}$	
d	Draw neat circuit diagrams and describe the methods of speed control of D.C.	
	Ans.	
	For DC shunt motor following is the equation for speed control	
	$k \times F$	
	$N \propto \frac{\kappa \times L_b}{L}$	
	Φ	
	Where,	
	Eb is backing EMF and Ψ is the flux.	
	ED is related to armature voltage as $v = ED + IaRa$ The speed of dc shunt motor is directly proportional to armature voltage and inversely proportional to flux	
	Armature voltage control method:	
		02
	electricaleasy.com	
	In this method armature voltage is controlled and it directly controls the speed below reted speed of motor	
	rated speed of motor.	



		Flux control method:	
		I + - M electricaleasy.com	02
		In this method, field current is controlled which controls the speed above rated speed. Decrease in field current increases the speed.	
3.		Attempt any <u>THREE</u> of the following:	12 M
	a	 Explain the concept of Dynamically induced emf and Statically induced emf. Ans: Dynamically induced emf: If flux linking with a particular conductor is brought about by moving the coil in stationary field or by moving the magnetic field w.r.t. to stationary conductor. Then the e.m.f. induced in coil or conductor is known as "Dynamically induced e.m.f. E = B 1. v. sinθ volts Statically induced emf: In the Statically induced emf flux linked with coil or winding 	
	b	changes $(d\Phi/dt)$ and coil or winding is stationary such induced emf is called Statically induced emf. $E = -N (d\Phi/dt)$ Draw schematic diagram of elementary 3-phase generator and describe its operation in brief. Draw waveform of 3-phase emfs. Ans:	02
		Phase A Phase C Phase C	02
		The elementary 3-phase 2-pole synchronous generator is shown in the figure. It has a stator equipped with 3 coils displaced 120 deg from each other. The rotor produces magnetic field. It has electromagnets which are excited by supplying dc voltage. The magnetic field produced by rotor induces sinusoidal voltages are generated in the 3 stator phases, displaced 120deg in time and having a frequency directly related to rotor speed.	02



	c	Compa	re Squirrel Cage Induction Motor	and Slip Ring Induction Motor on the		
		basis of	any four points. (Any four points ea	ch 1 Mark)		
		Ans:				
		Compa	rison:			
		Sr.	Squirrel Cage Induction Motor	Slip Ring Induction Motor		
		1 NO.	Deterising the forms of home	Doton is in the form of 2 physinding		
		1	No aling ring and hmachag	Rotor is in the form of 5-ph winding		
		2	External registance connet	External resistance can be connected		
		5	be connected	External resistance can be connected		
		4	Small or moderate starting torque	High Starting formue	04	
		5	Starting torque is of fixed	Starting torque can be adjust		
		6	Simple construction	Completed construction		
		7	High efficiency	Low efficiency		
		8	Less cost	More cost		
		9	Less maintenance	Frequent maintenance due to slip-ring		
				and brushes.		
		10	Size is compact for same HP	Relatively size is larger		
		11	Speed control by stator control	Speed can be control by stator &		
			method only	rotor control method		
	d	State ty	pes of fuses and describe the operati	ion of fuse. (Any Two Types expected: 1		
		Mark e	ach)			
		Ans:				
		Types o	of Fuses:			
		1.	Kewirable Fuses			
		2. 2	HRC Fuse			
		5. 4	D type Cartridge Euse			
		4. 5	Link Type Fuse			
		5. 6	Blade and Bolted type Fuses		02	
		0. 7.	Striker type Fuse		•-	
		8.	Switch type Fuse			
		9.	HV (High Voltage) Fuses			
		10.	Cartridge Type HRC Fuse			
		11.	Liquid Type HRC Fuse			
		12.	Expulsion Type HV Fuse			
		Operati	ion of Fuse:			
		1. 1	To break the circuit under fault condition	on.		
		2. To provide overcurrent protection to the circuit.				
		3.	To provide short circuit protection to the	ne circuit.		
4		4.	1 o provide safety to the users.		10 M	
4.		Attemp	t any <u>IHREE</u> of the following:		12 M	
	a	Draw h	vsteresis loop and define: (i) Magnet	ic hysteresis and (ii) Hysteresis loss.		
		Ans:				
		Magnet	tic Hysteresis: Defined as the loop that	at is generated by measuring the magnetic	01	
		flux (Bx	(A) of a ferromagnetic material while t	he magnetizing force (H) is changed.		
		Hystere	esis loss: It is the loss associated with	hysteresis loop. It is defined as the power	01	
		consum	ed by the magnetic domains for changi	ng the orientation after every half cycle.		











 Ans:	
V(t) $= 200 sin(3/4t)$ $= 200 sin(3/4t)$	
current in the circuit i(t) $i(t) = \frac{V(t)}{r} = \frac{200 \operatorname{Sin}(314t)}{r} = 4 \operatorname{Sin}(314.2t)$	
$: i(t) = 4 \sin(314t)$	
$\begin{array}{c} \text{Compare with} \\ \hline (l+) = \ \mbox{Im} \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \$	
i) Peak current Ip = 4A	
ii) Arevage Current = 0.637 Ip = 0.637 × 4A	06
$= 2 - 54 \cdot 5 \cdot A$	
(ii) RMS current = $\frac{1}{100} \frac{1}{100} \frac{1}{100} = \frac{1}{100} \frac{1}{100} = \frac{1}{100} \frac{1}{100} \frac{1}{100} = \frac{1}{100} \frac{1}{100} \frac{1}{100} \frac{1}{100} = \frac{1}{100} \frac{1}{10$	
$ir)$ freq. d current $f = \frac{\omega}{2\pi} = \frac{314-2}{2\pi} = \frac{50 \text{ Hz}}{2}$	
V) Angular Frequency = w = 314.2 rad/see	
Vi) Equation for inst value of current	
$i(t) = 4 \sin(314-2t)$	
Three defined in pedances, each having resistance of 20 s2 and capacitance of 20 μ F in series, are connected in star to the 3-phase, 415 volt, and 50 Hz supply. Determine: (i) Capacitive reactance, (ii) Impedance per phase (iii) Phase voltage (iv) Phase current (v) Power factor (vi) Total 3-phase power consumed by the load. Ans: 415v, 50n 415v, 50n 415v, 50n 415v, 50n 1 e = 20n 1 e = 20ne 1 e = 20 e = 120 2 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 100 2 e = 20 e = 20 e = 20 e = 100 2 e = 20	06
(a) $V_{Ph} = \frac{V_{L}}{V_{2}} = \frac{415V}{V_{2}} = 239.60V$	
$= 2p_{0} = 160.74 = 1000$	
(5) $PF = \cos \varphi = \cos \cos \varphi = \cos \varphi$	
(6) 10 Tal spin power = $\sqrt{3} \times 415 \times 1.5 \times 0.12$	
= 134.22 W = 0.1342 KW	





Or equivalent dia.



		Applications of stepper motor:		
		(Any two applications are accepted from following or equivalent 1 Mark each		
		point)		
		1.Suitable for use with computer controlled system		
		 Widely used in numerical control of machine tools. Tape drives 		
		4. Floppy disc drives		
		5. Computer printers		
		6. X-Y plotters	02	
		7. Robotics		
		8. Textile industries		
		9. Integrated circuit fabrication		
		10. Electric watches		
		11. In space craft's launched for scientific explorations of planets.		
		12 Automotive		
		13 Food processing		
		14 Packaging		
6		Attempt any TWO of the following:	12 M	
0.		Attempt any <u>rwo</u> of the following.		
	a	A series R-L circuit, consisting of a resistance of 100 Ω and an inductance of 0.6 H,		
		is connected to 230 V, 50 Hz supply mains.		
		Determine :		
		(i) Inductive reactance (ii) Circuit impedance (iii) Circuit current (iv) Circuit power		
		factor (v) Power consumed by the circuit (vi) Reactive power		
		Ans:		
		Va) (n) & lour		
		=230, 5042 3 0.64		
		i) Inductive Reactance XL= 2077L		
		= 2-17.50×0.4		
		= 188.49 J		
		îi) Impedance z = V R ² + X ²		
		$= \sqrt{(100)^2 + (188.49)^2}$	06	
		- 213·37 ~	VU	
		$iii)$ current = $\frac{V}{Z} = \frac{230}{213.37} = 1.074$		
		$\hat{r}\gamma$ $PF = \frac{R}{2} = \frac{100}{213\cdot 37} = 0.4686 \ lag.$		
		v) Power = VI cos 9 = 230×107×0.4686		
		= 115-33 W		
		Vi) Reactive Power = Q = VISing		
		= 230× 1-07× 213.49 (×)		
		= 217.40 VAR		



b	State any two applications of following each motor. Describe the reason of using	
	these motors in their respective applications.	
	(i) Shaded Pole Induction Motor	
	(ii) Universal Motor	
	(iii) AC Servo Motor	
	Ans:	
	i) Applications of Shaded Pole Induction Motor: (Any Two expected: 1 Mark each)	
	1. In clocks	
	2. Exhaust fans	
	3. Hair dryers	02
	4. Timing motors	
	ii) Applications of Universal Motor: (Any Two expected: 1 Mark each)	
	1) Mixer 2) Food processor 3) Heavy duty machine tools 4) Grinder 5) Vacuum	
	cleaner 6) Refrigerators 7) Driving sewing machines 8) Electric Shavers 9) Hair	02
	dryers 10) Small Fans 11) Cloth washing machine 12) Portable tools like blowers,	
	drilling machine, polishers etc.	
	iii) Applications of AC servo motor : (Any Two expected: 1 Mark each)	
	1. Robotics	
	2. Conveyor Belts	
	3. Camera Auto Focus	
	4. Robotic Vehicle	
	5. Solar Tracking System	02
	6. Metal Cutting & Metal Forming Machines	
	7. Antenna Positioning	
	8. Woodworking/CNC	
	9. Textiles	
	10. Printing Presses/Printers	
	11. Automatic Door Openers	
c	Describe the necessity of earthing and explain the methods of reducing earth	
	resistance.	
	Ans:	
	Necessity of Earthing: (Any I wo points are expected)	
	1. To provide an alternative pain for the leakage current to flow towards earth.	
	2. To save numan me from danger of electrical snock due to leakage current.	03
	5. To provide sefe path to dissipate lightning and short circuit currents	02
	 4. To provide sale path to dissipate lighting and short circuit currents. 5. To provide stable platform for operation of consitive electronic equipment's. 	
	5. To provide stable platform for operation of sensitive electronic equipment s. Methods of reducing earth resistance: (Any four points are expected)	
	1 By adding mixture of salt and water to the certh pit	
	2. By adding salt, charcoal and sand mixture to the pit	
	2. By adding sait, charcoar and said mixture to the pit.	04
	A By burying the ground plate as deep as possible	04
	5. By baying parallel ground plates with a distance of 10m between grounds	
	6 By using solt charceal ate to reduce resistivity	
	o. By using sait, charcoar etc., to reduce resistivity.	