

17664

11819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. (A) Attempt any THREE : 12
- (a) Enlist any four automation tools used in process. State need of SCADA.
  - (b) Draw a PLC wiring diagram for :
    - (1) Two push button switches.
    - (2) Draw 230 V AC operated motors.
  - (c) Draw the I/o addressing format of PLC.
  - (d) Describe with diagram sourcing input module.
- (B) Attempt any ONE : 6
- (a) (i) Differentiate relay control and PLC control on the basis of complexity of hardware and speed. (2 pt.)  
(ii) Explain the word redundancy with diagram. List the types of redundancies.
  - (b) Draw and explain block diagram of DC input module.

**2. Attempt any TWO :****16**

- (a)
  - (i) Name any four PLC languages.
  - (ii) List the sequences instructions of PLC & explain it with suitable example.
- (b) There are four outputs – R, S, T & U. Draw the ladder diagram for following conditions :-
  - (i) R goes off when stop s/w is pressed.
  - (ii) S goes off 7 seconds after R.
  - (iii) T goes off 6 seconds after R.
  - (iv) U goes off 2.5 seconds after S.
- (c) A thumb wheel switch (rotary encoder) is connected to the four input's of PLC. When timer is off, load thumbwheel data as a preset value of timer. When the timer times out, start motor 1.

**3. Attempt any FOUR :****16**

- (a) List the types of PLCs state the number of input/outputs in each type.
- (b) Define automation. State need of automation.
- (c) Explain one shot & latch type instruction.
- (d) Draw & explain block diagram of analog input module.
- (e) Enlist any four parameters to be considered while PLC installation. Describe Grounding.

**4. (A) Attempt any THREE :****12**

- (a) Explain with waveforms down counter.
- (b) Explain the following speciality I/o modules :
  - (i) Communication Module
  - (ii) RTD i/p Module

- (c) Explain LIM and NEG instruction of PLC.
- (d) How MCR (Master control relay) provides safety to PLC ?

**(B) Attempt any ONE :****6**

- (a) Draw block diagram of PLC and explain the function of power supply.
- (b) Draw and explain wiring diagram of sinking and sourcing output module.

**5. Attempt any TWO :****16**

- (a)
  - (i) Draw block diagram of DC output module.
  - (ii) List the selection criteria of I/o modules.
- (b)
  - (i) Explain functional block diagram (FBD) in detail.
  - (ii) Draw a ladder diagram for three floor system having following Condition's when the up motor is ON, down motor should be off and vice versa, having three push buttons  $C_1$ ,  $C_2$ ,  $C_3$  and three limit switches  $LS_1$ ,  $LS_2$ ,  $LS_3$ .
- (c) Explain briefly speed control of DC Motor using programmable drives.

**6. Attempt any FOUR :****16**

- (a) Draw diagram of stepper motor control module.
  - (b) Draw and explain format of off timer with waveforms.
  - (c) State PLC maintenance guidelines.
  - (d) Explain any four logical instruction in detail.
  - (e) Illustrate fault detection technique for LED status of input and output module.
-

