



22208

11819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :*
- (1) All questions are **compulsory**.
 - (2) Answer each Section on **separate** answer sheet.
 - (3) Illustrate your answers with neat sketches **wherever** necessary.
 - (4) Figures to the **right** indicate **full** marks.
 - (5) Assume suitable data, if **necessary**.

Marks

SECTION – I

1. Attempt **any six** of the following. 12
 - a) Define term :
 - i) EMF
 - ii) Current
 - b) State Lenz's law.
 - c) State the relationship between line and phase values for 3 phase delta connected balanced load.
 - d) State the significance of power factor.
 - e) State emf equation of single phase transformer.
 - f) State the application of single phase motor.
 - g) Define term :
 - i) Transformation ratio
 - ii) Turns ratio.
2. Attempt **any three** of the following. 12
 - a) State and explain Faraday's law of electromagnetic induction.
 - b) State the difference between electric and magnetic circuit (four points).
 - c) Draw and explain construction of two winding transformer.
 - d) Explain working of autotransformer. State its any two applications.
3. Attempt **any two** of the following . 12
 - a) Explain -self induced emf, mutual induced emf.
 - b) A resistance of 50 Ω and inductance 0.1 H are connected in series across 230 V, 50 Hz supply mains. Determine :
 - i) Inductive reactance
 - ii) Impedance
 - iii) Power factor

P.T.O.



- iv) Current
 - v) Angular frequency
 - vi) Power consumed by circuit.
- c) State different power in ac circuit. State its formulae and units. Draw power triangle for series R-L ac circuit.

SECTION – II

4. Attempt **any five** of the following. 10
- a) State the classification of capacitor.
 - b) Draw symbol of ideal and practical voltage and current sources.
 - c) State the applications of PN Junction diode. (any two)
 - d) Draw the symbol
 - i) NPN BJT
 - ii) PNP BJT
 - e) State the different types of filter.
 - f) Derive relationship between α and β .
5. Attempt **any three** of the following. 12
- a) Find the colour code for given resistance value.
 - i) $120\text{ K}\Omega, \pm 20\%$
 - ii) $2.2\text{ M}\Omega, \pm 5\%$
 - b) State difference between CB, CE and CC configuration.
 - c) Draw circuit diagram and input-output waveform for center tap full wave rectifier with π filter.
 - d) Draw the waveform for given signal.
 - i) Triangular wave
 - ii) Square wave with representing time period.
6. Attempt **any two** of the following. 12
- a) i) State the difference between active and passive components.
ii) State the dielectric materials used for capacitor.
 - b) i) State the difference between PN Junction diode and Zener diode.
ii) Define term-static and dynamic resistance for PN Junction diode.
 - c) Draw and explain circuit diagram and output characteristics for CE configuration of Bipolar junction transistor.
-