

312310

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

**1. Attempt any FIVE of the following :**


**10**

- (a) Define conductivity & state it's unit.
- (b) State Ohm's law applied to an electrical circuit & express it in the form of equation.
- (c) Define dielectric strength for a capacitor and give its unit.
- (d) Define the following terms :
  - (i) MMF
  - (ii) Reluctance
- (e) Define Magnetic Hysteresis.
- (f) State Lenz's law.
- (g) List the different types of battery with its one application each.



**2. Attempt any THREE of the following :****12**


- (a) Draw the symbol & characteristics of Ideal Voltage Source & Practical Voltage Source.
- (b) Find the equivalent resistance between terminal A & B shown in Fig. No. 1 given below :

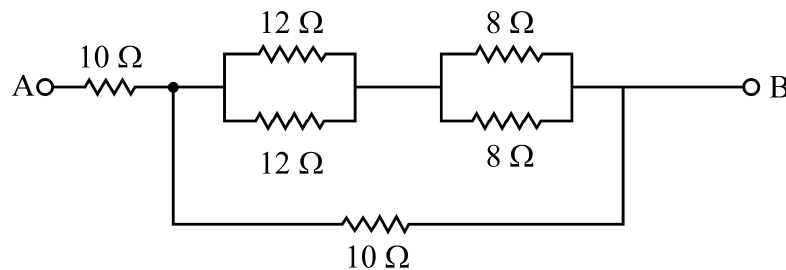**(Fig. No. 1)**

- (c) Plot charging voltage and current curves of capacitor, also write expression for them.
- (d) Explain Heating effect of electric current with its application.

**3. Attempt any THREE of the following :****12**

- (a) Describe the effect of temperature on Resistance.
- (b) State and explain Kirchoff's voltage law.
- (c) Three capacitors  $14\ \mu\text{F}$ ,  $16\ \mu\text{F}$  and  $18\ \mu\text{F}$  are connected in circuit. Find equivalent capacitance when they are connected in
- Series
  - Parallel
- (d) Find the current (I) flowing through  $6\ \Omega$  resistor shown in Figure No. 2 using KVL.

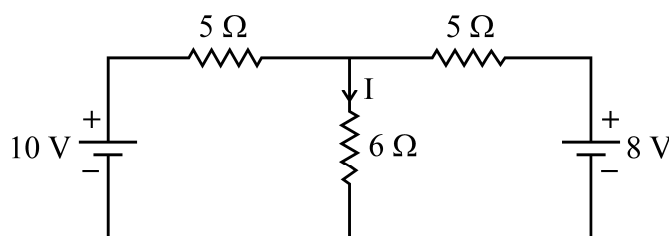**(Fig. No. 2)**

**4. Attempt any THREE of the following :****12**

- (a) Define electric work and electric power. Give their SI units.
- (b) Derive expression for energy stored in a capacitor with the help of neat diagram.
- (c) Explain construction of lead acid battery with neat sketch.
- (d) Draw and label series magnetic circuit and parallel magnetic circuit.
- (e) Compare statically induced emf and dynamically induced emf on following four points :
  - (i) Movement of coil or magnet
  - (ii) Current
  - (iii) Expression of induced emf
  - (iv) Application

**5. Attempt any TWO of the following :****12**

- (a) Define following terms :
  - (i) Active and Passive Network
  - (ii) Linear and Non-linear circuit
  - (iii) Unilateral and Bilateral circuit
- (b) Draw hysteresis loop for hard steel, cast steel and sheet steel, also write one application for each material.
- (c) A coil consisting of 200 turns is placed in the magnetic field of 0.6 mWb. Calculate the average emf induced in a coil when it is moved in 0.08 seconds from the given field of 0.2 mWb. If the resistance of coil is  $200\ \Omega$ , find the induced current in the coil.

**6. Attempt any TWO of the following : 12**

(a) Compare Electric circuit and Magnetic circuit stating three similarities and three dissimilarities.

(b) (i) State various types of inductor. 3

(ii) Derive energy stored in magnetic field. 3

(c) If a coil of 2000 turns is linked with a flux of 0.04 weber, when carrying current of 20 A

Calculate :

(i) Inductance of a coil

(ii) Induced emf if current is uniformly reversed in the coil in 0.02 seconds.

---