313324

12425 03 Hours / 70 Marks Seat No. I <thI</th> I <thI</th> <thI</th> I <thI</

Instructions – (1) All Questions are Compulsory.

- (2) Answer each next main Question on a new page.
- (3) Illustrate your answer with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1.Attempt any <u>FIVE</u> of the following:10

- a) Define the terms related to power amplifiers:
 - i) Gain
 - ii) Bandwidth.
- b) State the function of the level shifting stage. Used in Op-Amp.
- c) State advantages of negative feedback in respect to
 - i) Bandwidth
 - ii) Input resistance
 - iii) Output resistance
 - iv) Gain stability.

- d) Compare oscillator and amplifier on the basis of
 - i) Type of feedback used
 - ii) Need of input signal.
- e) Define terms related to filters
 - i) Roll off rate
 - ii) Pass band.
- f) Draw labelled pin diagram of Op-Amp IC 741.
- g) Write the function of
 - i) IC 555
 - ii) IC 565.

2. Attempt any THREE of the following:

12

12

- a) Define oscillator. State the Barkhavsen's criteria for the generation of sustained oscillations.
- b) Explain the working of class A power amplifier with the help of circuit diagram and waveforms.
- c) Name amplifier configuration in which virtual ground is present. Explain virtual ground concept with suitable diagram.
- d) In closed loop Inverting amplifier, Vin = 1 Vpp sinewave at 1 KHz, $R_1 = 470\Omega$, $RF = 4.7k\Omega$. Determine the value of output voltage Vo. Also sketch input and output voltage waveforms.

3. Attempt any THREE of the following:

- a) Define following parameters of Op-Amp. Also write its ideal and typical value
 - i) CMRR
 - ii) Slew Rate.
- b) Draw ideal and practical frequency response of
 - i) Low pass filter
 - ii) High pass filter.
- c) Design RC phase shift oscillator using IC 741 to produce a sinusoidal output signal at fo = 1 kHz. Draw designed circuit.

12

12

d) Class A power amplifier has an output power of 2W. If amplifier has an efficiency of 25%, the determine the total power drawn from the supply.

4. Attempt any THREE of the following:

- a) Describe the working of non-inverting Zero Crossing Detector with the help of circuit diagram and waveforms.
- b) Compare active filters and passive filters. (Any four points)
- c) Name the distortions occurred in class B push pull amplifier. Write the method to overcome these distortions. Draw waveform of these distortions.
- d) Draw the block diagram of PLL. State the function of each block.
- e) Compare class A, class B, class C and class AB power amplifier on the basis of
 - i) Conduction angle of transistor
 - ii) Location of Q point.
 - iii) Efficiency
 - iv) Collector current waveform.

5. Attempt any <u>TWO</u> of the following:

- a) In Schmitt trigger circuit, $R_1 = 100\Omega$, $R_2 = 56k\Omega$, Vin = $1V_{p-p}$ sinewave and Op-Amp is 741 with saturation voltages = ±14V. Determine:
 - i) Upper threshold Voltage (Vut)
 - ii) Lower threshold Voltage (Vlt)
 - iii) Hysteresis Voltage (Vhy).
- b) Write two applications of PLL. Explain any one of them with suitable block diagram and waveforms.
- c) Design second order Low Pass Butter worth filter with higher cutoff frequency $f_H = 1$ KHz. Draw designed circuit and sketch it's frequency response.

P.T.O.

313324

6. Attempt any TWO of the following:

- a) Describe the working principle of Hartley Oscillator using IC 741 with circuit diagram. Derive it's formula for frequency of oscillation (Fo).
- b) Design second order high pass Butterworth filter with cut off frequency = 10 kHz. Draw designed circuit and sketch it's actual frequency response.
- c) Design Astable multivibrator using IC 555 with the frequency of 2 kHz and duty cycle = 50%. Also draw designed circuit. (Assume C = 0.1μ F).

12