

313325

12425

03 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following: 10
- a) Define the terms:
 - i) Mesh
 - ii) Node
 - b) State the reciprocity theorem.
 - c) Write the formula for following Z-parameters:
 - i) Z_{11}
 - ii) Z_{21}
 - d) What is pass band and stop band of filter?
 - e) Draw the phasor diagram for purely inductive circuit.
 - f) Define resonance in series RLC circuit. State the resonant frequency of series resonant circuit.
 - g) Draw well labeled diagram showing variation of impedance in parallel resonant circuit.

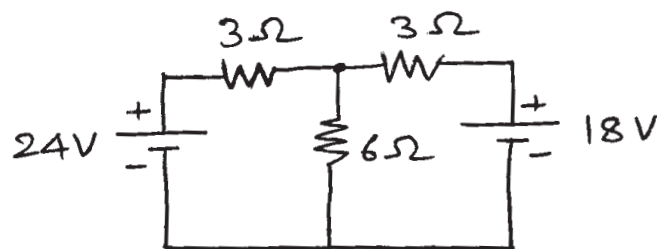
P.T.O.

2. Attempt any THREE of the following:**12**

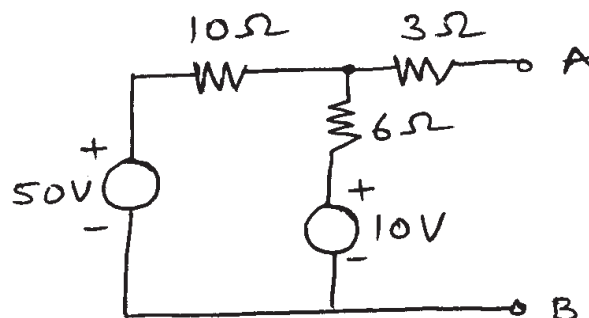
- a) Explain with suitable example, procedure to convert voltage source into its equivalent current source.
- b) State Superposition Theorem. List the drawbacks of superpositions theorem. (Any two)
- c) Give the comparison in between T and π attenuators. (Any four points)
- d) A coil consists of 0.08H inductance with resistance of 40Ω connected to 230V , 50Hz supply. Find:
 - i) Impedance
 - ii) Reactance
 - iii) Current
 - iv) Power factor

3. Attempt any THREE of the following:**12**

- a) Find the current in 6Ω resistor in the circuit shown in the Fig. No. 1.

**Fig. No. 1**

- b) Obtain Thevenin's equivalent circuit for the network shown in the Fig. No. 2.

**Fig. No. 2**

- c) For a 1Φ series RC circuit:
- Draw the circuit diagram.
 - Write voltage and current equation.
 - Draw impedance triangle
 - Draw phasor diagram.
- d) Explain the variation of current and power factor in R-L-C series resonant circuit.

4. Attempt any THREE of the following:

12

- a) Determine the equivalent resistance between terminals A and B for a circuit shown in Fig. No. 3.

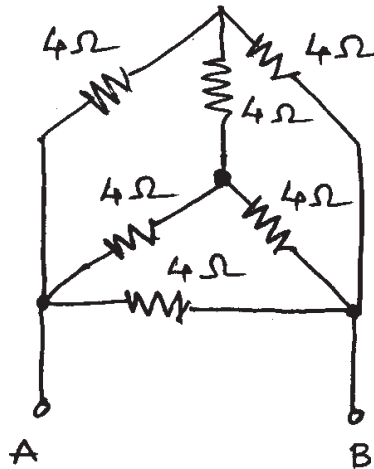


Fig. No. 3

- b) Calculate the current flowing through 5Ω resistor using Norton's theorem for the circuit shown in the Fig. No. 4.

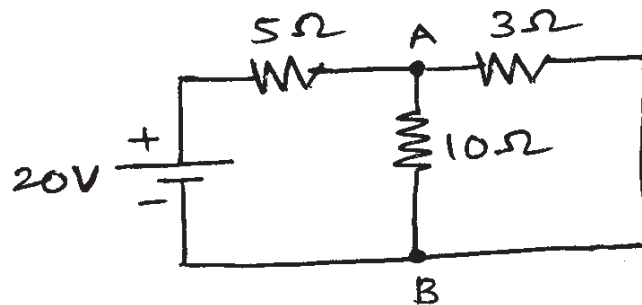


Fig. No. 4

- c) Find short circuit admittance (Y) parameters for the network shown in the Fig. No. 5.

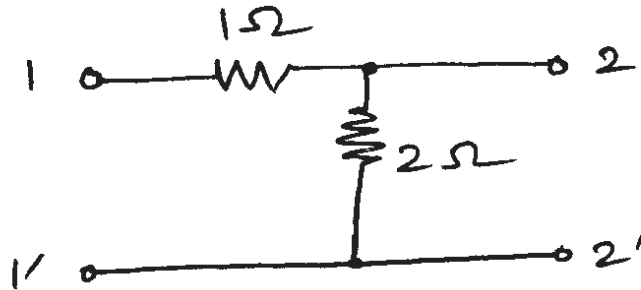


Fig. No. 5

- d) A coil of resistance 10Ω and inductance 0.1H is connected in series with capacitor of $150\mu\text{F}$ across 200V , 50Hz supply. Calculate:
Inductive reactance (X_L), Capacitive reactance (X_C), Impedance (Z) and Current (I).
- e) A R - L - C series circuit with resistance of 20Ω , inductance of 0.25H and capacitance of $100\mu\text{F}$ is supplied with 250V , 50Hz supply. Determine:
- Resonant Frequency
 - Current at resonance
 - Power factor
 - Quality factor

5. Attempt any TWO of the following:

12

- a) Use nodal analysis to calculate the power dissipation across 4Ω resistor for the circuit shown in the Fig. No. 6.

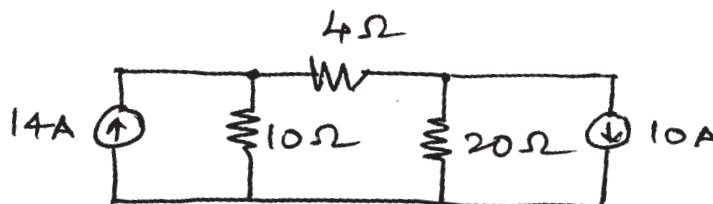


Fig. No. 6

- b) Determine the value of load resistance R_L when load resistance draws maximum power for the circuit shown in Fig. No. 7. Also find the value of maximum power delivered to it.

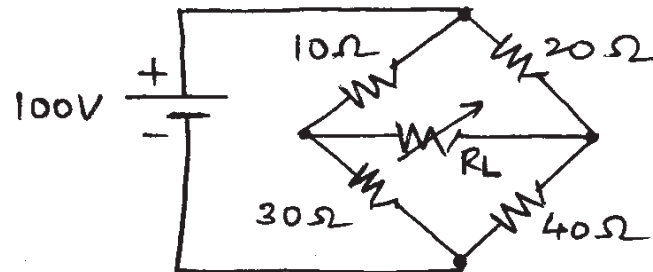


Fig. No. 7

- c) A coil with an inductance of 0.01H and a resistance of 2Ω is connected in parallel with capacitor of $714\mu\text{F}$. Above circuit produces resonance when connected across 230V , 50Hz supply. Determine total current and current in each branch.

6. Attempt any TWO of the following:

12

- a) Use superposition theorem to find current through 4Ω resistor for the circuit shown in Fig. No. 8.

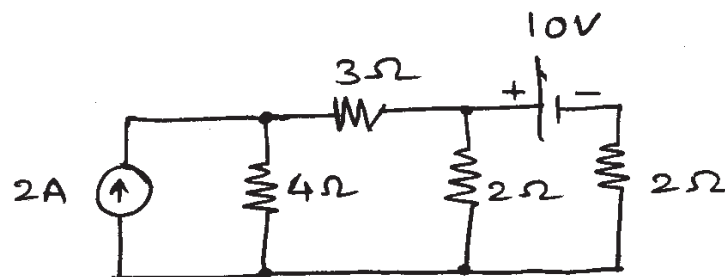


Fig. No. 8

- b) Find ABCD parameters for the network shown in the Fig. No. 9. Comment on reciprocity and symmetry of the network.

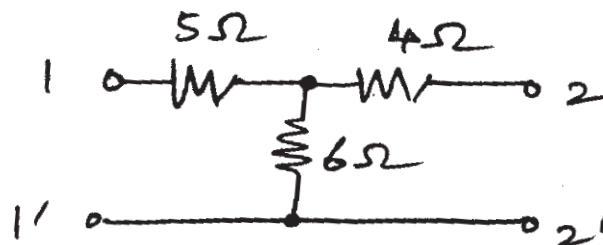


Fig. No. 9

- c) Compare series and parallel resonant circuit on the basis of:
- i) Resonant Frequency
 - ii) Impedance at resonance
 - iii) Current at resonance
 - iv) Magnification
 - v) Power factor
 - vi) Application
-