

22526

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw the symbol of following :
 - (i) Push button
 - (ii) Proximity switch
 - (iii) Pressure switch
 - (iv) Limit switch
- (b) Draw block diagram of PLC.
- (c) List any two input and output device used in conjunction with PLC.
- (d) Draw ladder diagram for NAND gate operation.
- (e) Give the full form of SCADA and HMI.
- (f) Draw ladder diagram of seal in circuit.
- (g) Draw ladder diagram of X-OR gate operation.



2. Attempt any THREE of the following : 12

- (a) Develop the control circuit for star-delta starter used for starting a 3 ϕ induction motor.
- (b) Explain with block diagram digital output module of PLC.
- (c) Develop ladder diagram and wiring diagram for DOL starter with OLR contact.
- (d) Explain the following relay type instruction :
 - (i) IF-open
 - (ii) IF close with its symbol

3. Attempt any THREE of the following : 12

- (a) Explain Count UP [CTU] instruction with timing diagram.
- (b) Distinguish between PLC and SCADA on any four points.
- (c) Develop the ladder diagram for ON/OFF temperature control.
- (d) Classify timers of PLC and explain retentive ON timer in detail.

4. Attempt any THREE of the following : 12

- (a) Draw the ladder diagram for PLC based water level controller.
- (b) Classify and explain the PLC available in the market.
- (c) Explain with block diagram working of soft starter.
- (d) Explain the working of DOL starter control circuit of an induction motor.
- (e) Draw the block diagram of analog input module of PLC. State the function of each block.

5. Attempt any TWO of the following : 12

- (a) Develop a generalized DCS architecture for control of a plant.
- (b) Explain the working of PLC based bottle filling system with help of ladder diagram.
- (c) Develop control and power circuit diagram of hoist control and mill.

6. Attempt any TWO of the following : 12

- (a) Explain instruction T_{ON} and T_{OFF} timer with timing diagram.
 - (b) Explain the following speciality modules of PLC :
 - (i) Communication module
 - (ii) PID controller module
 - (iii) Stepper motor control module
 - (c) Develop the ladder diagram for stepper motor control.
-

