

22527

12425

3 Hours / 70 Marks

Seat No.

|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) List any two applications of SIT.
- (b) Classify inverter based on the connection.
- (c) Draw symbol and VI characteristics of FCT.
- (d) List the types of high frequency heating.
- (e) List types of Dual converter.
- (f) List the control strategies used in chopper.

**2. Attempt any THREE of the following :**

**12**

- (a) Compare step up and step down chopper (any four points).
- (b) Draw circuit diagram of three phase to single phase cycloconverter and draw the input/output waveform.
- (c) Describe working principle of dielectric heating with suitable block diagram.
- (d) Explain the operation of basic parallel inverter with circuit diagram.



- 3. Attempt any THREE of the following : 12**
- (a) Compare Class A and class B Chopper (any four points).
  - (b) Identify a suitable chopper for producing the output in first and second quadrant and explain its operation.
  - (c) Explain the operation of single phase to single phase cycloconverter with neat diagram.
  - (d) Draw circuit diagram of single phase full bridge inverter with RL load and explain its operation.
- 4. Attempt any THREE of the following : 12**
- (a) The applied DC voltage of Class A chopper is 200 V and load resistance of 50  $\Omega$ . Calculate average output voltage if duty cycle is 0.4.
  - (b) Explain the working principle of single phase dual converter with circulating current mode.
  - (c) Explain the operation of McMurray half bridge inverter with circuit diagram.
  - (d) Explain working principle of single phase series inverter with circuit diagram.
- 5. Attempt any TWO of the following : 12**
- (a) Explain the operation of battery charger control with neat circuit diagram.
  - (b) Explain the operation of Jone's chopper with neat circuit diagram.
  - (c) Draw input and output waveform of cycloconverter to produce  $1/5^{\text{th}}$  of input frequency. Show the firing sequence of thyristors in the relevant waveform. Also list the application of cycloconverter.
- 6. Attempt any TWO of the following : 12**
- (a) Justify IGBT as a voltage controlled device with characteristics.
  - (b) Draw the circuit diagram of DC static circuit breaker and explain its operation.
  - (c) Explain the operation of static VAR compensation system with neat diagram.
-