

22538

12425

3 Hours / 70 Marks

Seat No.

|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) State any four applications of – universal motor.
- (b) State any four ratings of stepper motor.
- (c) State any four applications of shaded pole motor.
- (d) Draw neat diagram of single phase full converter.
- (e) Draw electrical diagram of DC series motor.
- (f) State any four applications of compound motor.
- (g) Write any four advantages of microprocessor based drives.

**2. Attempt any THREE of the following :**

**12**

- (a) Explain the operation of rotor resistance control of three phase induction motor.
- (b) Draw and explain chopper controlled DC Drive.
- (c) Draw only the block diagram of control of DC motor using microprocessor.
- (d) Describe the stepper motor drive using microcontroller with neat sketch.



**3. Attempt any THREE of the following : 12**

- (a) Explain with neat diagram stator voltage control of 3 phase IM.
- (b) Explain with neat diagram V/F control of 3 phase IM.
- (c) Draw only the block diagram of microprocessor based synchronous motor drive.
- (d) Explain with neat diagram the working of capacitor start single phase AC motor.

**4. Attempt any THREE of the following : 12**

- (a) State the sequence of stages and drives required in each stage of sugar mill.
- (b) State the braking methods of induction motor. Explain any one method with neat diagram.
- (c) Draw and explain the working of PLL based DC Drive.
- (d) State starting methods of induction motor. Explain any one of them.
- (e) Draw the block diagram of basic element of drive. Explain each block in short.

**5. Attempt any TWO of the following : 12**

- (a) Draw only the circuit diagram of 3 phase dual converter.
- (b) Draw neat diagram of single phase semi-converter to control speed of DC motor. Explain its working with voltage and current waveforms.
- (c) Draw electrical circuit diagram of single phase resistance split AC motor. Explain its working. State any two applications of it.

6. Attempt any TWO of the following :

12

- (a) Draw and explain reversible SCR drive.
  - (b) Draw electrical circuit diagram and speed V/S torque characteristics of DC shunt motor. Explain why it is called as constant speed (constant flux) motor.
  - (c) State the sequence of stages and drives required in each stage of textile mill.
-

