

22629

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.

Marks

1. Attempt any FIVE of the following :

10

- (a) Define Group drive and Multimotor drive.
- (b) Draw speed torque characteristics of DC series motor.
- (c) List any four advantages of converter controlled drives.
- (d) Draw circuit diagram of single phase semiconverter drives.
- (e) Draw block diagram of stator voltage control method of three phase induction motor.
- (f) Enlist any four functions performed by microcontroller in speed control of drives.
- (g) Draw a block diagram of microprocessor based DC motor controller.

2. Attempt any THREE of the following :

12

- (a) State the factors that should be considered for selection of drive.
- (b) Compare single phase and three phase converter drive (Any four points).
- (c) Describe the working of Class C chopper drive with neat diagram and waveforms.
- (d) State the principle of slip power recovery system. Also draw its block diagram.



- 3. Attempt any THREE of the following : 12**
- (a) Draw torque Vs speed/slip characteristics of Induction motor showing all regions. Explain it.
 - (b) Draw circuit diagram & Input/Output waveforms for single phase full wave converter.
 - (c) Compare Class A and Class B chopper drive (Any four points).
 - (d) Describe role of drives in sugar mills.
- 4. Attempt any THREE of the following : 12**
- (a) Identify the type of chopper drive for reversible regenerative braking of DC motor. Explain its working with quadrant diagram.
 - (b) With the help of block diagram, explain V/F control for speed control of Induction motor.
 - (c) Describe chopper controlled induction motor drive employing rotor resistance control technique.
 - (d) State the advantages of microcontroller based control drives.
 - (e) Describe the block diagram of synchronous motor drive using microcontroller.
- 5. Attempt any TWO of the following : 12**
- (a) Describe the working of three phase dual converter with the help of neat diagram & waveforms.
 - (b) Explain with neat diagram and waveforms, the operation of class D chopper.
 - (c) Draw a neat diagram and explain the working of phase locked loop control of DC motor.
- 6. Attempt any TWO of the following : 12**
- (a) A single phase full converter fed from 230 V, 50 Hz supply provides a variable voltage supply to armature of separately excited DC motor. The specifications of motor are 10 HP, 230 V, 1200 rpm, $R_a = 0.25 \Omega$. Rated motor current is 40 A, motor voltage constant $k_a \phi = 0.172 \text{ V/rpm}$. The firing angle is 30° . For the rated motor current, calculate :
 - (i) Motor torque
 - (ii) Speed of the motor
 - (b) Give detailed classification of chopper based on Quadrants. Describe basic chopper circuit using SCR.
 - (c) List various stages involved in textile mill and its speed ratings and drives used at each stage.
-