

22639

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw NMOS transistor side-view structure with labels.
- (b) List the logical operators in VHDL.
- (c) Write the applications of Test bench.
- (d) Write the meaning of product number XC35400 – 4PQG208C.
- (e) State the concept of zero modeling.
- (f) Draw the symbol and configuration/schematic diagram of Transmission Gate.
- (g) List two examples of sequential and concurrent statements in VHDL.

2. Attempt any THREE of the following :

12

- (a) Draw the block diagram of CPLD. State the function of Logic or Function block. Write two names of Families of CPLD.
- (b) Write the VHDL code for 4-bit adder without instantiation.
- (c) Draw CMOS inverter (1) Circuit diagram (2) Cross section diagram (3) VTC characteristics (4) VTC characteristics with Good NMOS and bad PMOS.
- (d) Write VHDL code for EXOR gate using (1) Behavioural modeling and (2) Data flow modeling.



- 3. Attempt any THREE of the following : 12**
- (a) Explain the estimation process of resistance with layout diagram.
 - (b) Write the pro's and con's of VHDL.
 - (c) Draw the FPGA architecture and state the function of any four blocks.
 - (d) Write VHDL code for 4 : 1 mux.
- 4. Attempt any THREE of the following : 12**
- (a) Compare FPGA, CPLD and ASIC on the basis of – (1) Performance (2) Memory (3) Power consumption (4) Security.
 - (b) Draw the circuit diagram of NAND gate using (1) NMOS and (2) CMOS logic.
 - (c) Draw the cross-section view of CMOS inverter with N-Well OR Twin-tub. State the advantages of Twin-tub process.
 - (d) Define the terms : (1) Noise margin (2) Fan-out (3) Metastability (4) Skew
 - (e) List the delays in VHDL simulation. Explain any one with statement and waveform.
- 5. Attempt any TWO of the following : 12**
- (a) Design FSM circuit for sequence detector 1101 using D-flip-flop.
 - (b) Draw the stepwise diagram for N-well CMOS fabrication process.
 - (c) Write VHDL code for 3 : 8 decoder using case statement.
- 6. Attempt any TWO of the following : 12**
- (a) Explain VLSI design flow for synthesis with neat sketch.
 - (b) (i) Draw the block diagram of Moore machine and Mealy machine FSM. Write the output expression.
(ii) Compare Moore machine and Mealy machine.
 - (c) (i) Write the function of (1) Library and (2) Entity
(ii) Explain different data types used in VHDL.
-