

22320

12425

03 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answers with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following : 10
- a) Write the gray code of given no.
$$(11011)_2 = (?)_{\text{Gray}}$$
 - b) List the different type of ADC.
 - c) Draw block diagram of 4:1 multiplexer and write its truth table.
 - d) State advantages of PLDs.
 - e) Define following characteristics of logic families.
 - i) fan in
 - ii) fan out
 - f) Draw logic diagram of T flip-flop and give its truth table.
 - g) Draw symbol of NAND and NOR Gate with its boolean expression.

P.T.O.

2. Attempt any THREE of the following :**12**

- a) Perform the following substraction using 1's complement method
 - i) $(48)_{10} - (68)_{10}$
 - ii) $(1011)_2 - (101)_2$
- b) Design a Half subtractor circuit using K-map.
- c) Describe the working of 4 bit SISO (Serial in Serial Out) Shift Register with diagram.
- d) Draw the circuit for NoT, OR and AND gate using NAND gate only.
- e) Minimize the following expression using K-map and Draw the ckt. dig.

$$F(A, B, C, D) = \sum m (0, 1, 4, 5, 6, 7, 13, 15)$$

3. Attempt any THREE of the following :**12**

- a) Simplify the following Boolean expression using Boolean laws.

$$y = \overline{AB} + \overline{AC} + B\overline{C}$$
- b) Realize the following function using Demultiplexer.

$$Y_1 = \sum m (1, 2, 7, 9, 12, 14)$$

$$Y_2 = \pi M (3, 5, 8, 11, 15)$$
- c) Compare between PLA and PAL.
- d) Describe the working of clocked JK flip-flop with its truth table and logic diagram.
- e) Draw the block diagram of BCD to seven segment decoder using IC 7447 with truth table of it.

4. Attempt any THREE of the following :**12**

- a) Draw 8 : 1 multiplexer using two 4 : 1 multiplexers.
- b) Draw the block diagram explain the working of 3 bit asynchronous counter with waveform.
- c) Compare the following (Any three point)
 - i) SRAM with DRAM memory.
 - ii) Mux and Demux.
- d) State and prove De-morgan's Theorems. (Any one)
- e) What are BCD numbers ? Perform BCD addition for the following
 - i) $(68)_{10} + (44)_{10}$
 - ii) $(50)_{10} + (36)_{10}$

5. Attempt any TWO of the following :**12**

- a) Convert the following into std. forms.
 - i) $y = \overline{A}B + ABC + \overline{B}C$
 - ii) $y = \overline{B}C + AB$
 - iii) $y = (A + B) \cdot (\overline{B} + \overline{C})$
- b) Compare the parameters of TTL, ECL and CMOS logic families (Any four points)
- c) Design a Mod-6 asynchronous counter with truth table and logic.

6. Attempt any TWO of the following :**12**

- a) Find the Boolean expression for logic circuit given in Fig. No. 1 and reduce it using Boolean algebra.

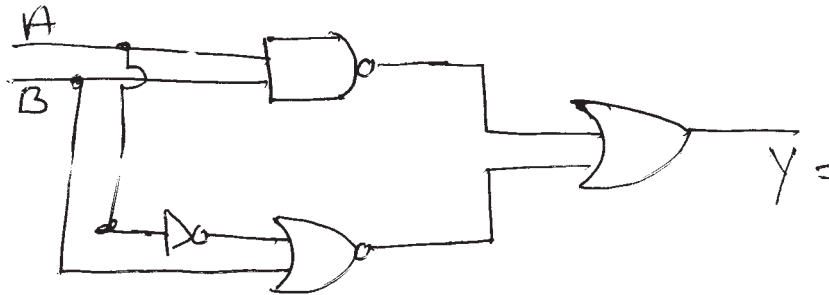


Fig. No. 1

- b) Draw the circuit diagram of 4 bit R-2R Ladder DAC and obtain its output voltage expression.
- c) Explain the working of 3 bit synchronous counter with circuit diagram.
-