22384

12425 3 Hours / 70 Marks

Seat No.

Instructions : (1) All Questions are *compulsory*.

- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
- (8) Use of Steam tables, logarithmic, Mollier's chart is permitted.

Marks 1. Attempt any FIVE of the following : 5 × 2 = 10 (a) List different types of industrial automation. (b) State the need for industrial automation.

- (c) List different manufacturers of PLC.
- (d) State benefits of industrial automation (any four).
- (e) List any two input and output devices used to interface with PLC.
- (f) List communication modules used with PLC.
- (g) State different programming languages used in PLC.

2. Attempt any THREE of the following : $3 \times 4 = 12$

- (a) Draw the block diagram of typical industrial automation system.
- (b) Compare fixed and modular PLC (any four points).



- (c) Draw neat labelled block diagram of generalized PLC and explain the function of each block.
- (d) Describe the factors that must be considered while wiring a PLC.

3. Attempt any THREE of the following : $3 \times 4 = 12$

- (a) Explain scan cycle and scan time with respect to PLC.
- (b) Draw the symbol for OFF delay timer instruction used in PLC in ladder programming and explain the meaning of following :
 - (i) EN (enable) bit (ii) DN (done) bit
- (c) List Data Handling and bit type instruction used in PLC along with their symbols used in ladder program.
- (d) Draw a neat wiring diagram of following I/O devices with appropriate PLC module :
 - (i) PNP Sensor (ii) Solenoid coil

4. Attempt any THREE of the following : $3 \times 4 = 12$

- (a) Explain watchdog function in PLC.
- (b) Draw the ladder diagram for following Boolean expression :
 - (i) Y(A, B, C, D) = A' B + A' D + B' D
 - (ii) Y(A, B, C) = AB + C'
- (c) Explain redundancy concept in PLC.
- (d) List counter instruction used in PLC along with their symbol used in ladder programming.
- (e) List types of PLC memory and describe them in brief.

5. Attempt any TWO of the following :

- (a) Implement 4:1 multiplexer in PLC using ladder diagram.
- (b) Draw the ladder diagram for traffic light control and explain the logic.
- (c) State different control panel accessories of PLC and draw the wiring diagram of pressure switch with PLC i/p module.

6. Attempt any TWO of the following :

- (a) Draw ladder diagram for following logic functions :
 - (i) Two input OR function
 - (ii) Two input AND function
 - (iii) Two input EX-OR function
- (b) Implement 1:8 de multiplexer in PLC using ladder diagram.
- (c) Explain the format of sequencer and analog scaling instructions in PLC.

22384

 $2 \times 6 = 12$

22384