

22310

12425

03 Hours / 70 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

- Instructions –*
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answer with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

SECTION-I

- 1. Attempt any SIX of the following:** **12**
- a) Define:
 - i) Peak factor
 - ii) Power factor.
 - b) State the types of transformers.
 - c) Define:
 - i) Current
 - ii) Potential.
 - d) State any two applications of single phase motor.
 - e) Define:
 - i) Amplitude
 - ii) Phase angle.

P.T.O.

- f) State Fleming's right hand rule.
- g) Write the equation of self inductance. State the meaning of each notation on it.

2. Attempt any THREE of the following: 12

- a) Compare self and mutual induction (Any four points).
- b) Draw and explain construction of transformer.
- c) Explain the construction and working principle of auto transformer.
- d) Explain the construction and working principle of single phase AC motor.

3. Attempt any TWO of the following: 12

- a) Draw and explain series RLC circuit. State any two differences between series and parallel RLC circuit.
- b) A capacitance of $40\mu\text{f}$ and a resistance of 100Ω are connected in series across a 230 V, 50 Hz supply mains. Determine:
 - i) Angular frequency
 - ii) Current
 - iii) Circuit powerDraw circuit diagram.
- c) Explain the working principle of single phase induction motor.

SECTION-II

4. Attempt any FIVE of the following: 10

- a) State specification of resistors.
- b) Draw the symbol of:
 - i) Zener diode
 - ii) LED.
- c) Define parameters – α and β related to BJT.

- d) State the classification of capacitors.
- e) List different types of filter.
- f) State the application of BJT.
- g) List different operating region for BJT.

5. Attempt any THREE of the following: 12

- a) Explain ideal and practical voltage sources with suitable diagram.
- b) Differentiate between centre tapped and bridge full wave rectifier with following parameters:
 - i) No. of diode used
 - ii) PIV
 - iii) Ripple factor
 - iv) Efficiency.
- c) Draw and explain VI characteristics of PN junction diode.
- d) Find the values of resistor from given colour code:
 - i) Red, Red, Orange, Gold.
 - ii) Brown, Green, Yellow, Silver.

6. Attempt any TWO of the following: 12

- a)
 - i) Differentiate between analog and digital IC.
 - ii) State difference between passive and active components.
 - b) Draw and explain half wave rectifier with capacitor shunt and π filter.
 - c)
 - i) State difference between CB, CE and CC configuration with given parameter – i/p resistance, current gain and application.
 - ii) Explain transistor as a switch.
-