

22324

12425

03 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answers with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.


Marks

1. **Attempt any FIVE of the following :** **10**
- a) Define Active and Reactive power with unit.
 - b) Draw the power triangle for R.C. Series circuit.
 - c) Calculate admittance if $z = 6 + j4\Omega$
 - d) State the relationship between line and phase values of voltage and current in star connection.
 - e) Draw the symbol of Ideal and practical current source.
 - f) State Norton's Theorem.
 - g) State maximum power transfer theorem.

P.T.O.

2. Attempt any THREE of the following :**12**

- a) State the meaning of term lagging and leading with necessary waveforms.
- b) Define Quality factor and Bandwidth with its mathematical expression.
- c) State any four advantages of polyphase circuit over single phase circuit.
- d) Using Mesh analysis find current I_1 and I_2 of given circuit below. Refer Fig. No. 1

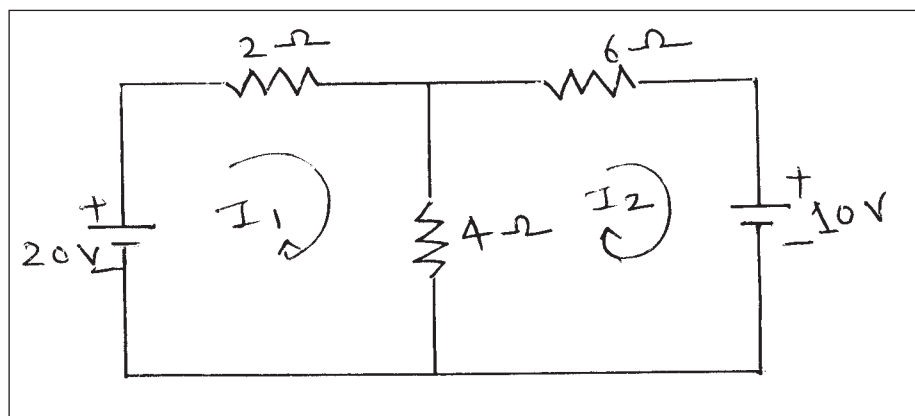**Fig. No. 1****3. Attempt any THREE of the following :****12**

- a) If a resistance of 50Ω and an inductance of 0.1 H are connected in series and the combination is supplied with 230V , 50Hz supply. Calculate impedance, current and power factor.
- b) Impedances $Z_1 = (2 + j4)\Omega$ and $Z_2 = (4 + j3)\Omega$ are connected in parallel across 230V , 50 Hz supply. Calculate supply current and power factor.
- c) Compare star connection with delta connection.

- d) Using nodal analysis, Find current in the 4Ω and 5Ω resistance of the circuit given below. Refer Fig. No. 2

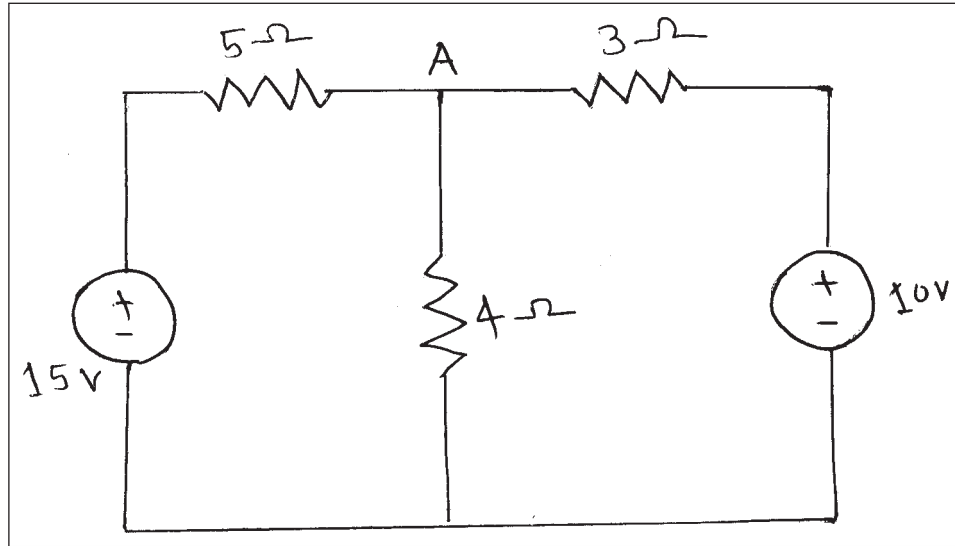


Fig. No. 2

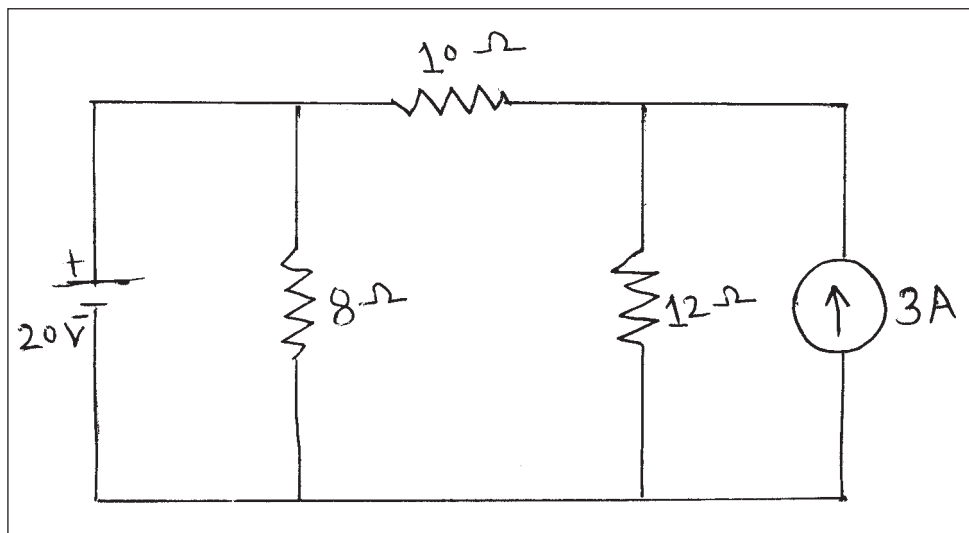
- e) Define duality of electric circuits and write duality of electrical elements.

4. Attempt any THREE of the following :

12

- a) A R-L-C series circuit with resistance of 20Ω , inductance of 0.25H and capacitance of $100\mu\text{F}$ is supplied with 240V A.C. supply Calculate -
 - i) Resonance frequency
 - ii) Current at this condition
 - iii) Power factor
 - iv) Quality factor
- b) Define the following terms -
 - i) Admittance
 - ii) Conductance
 - iii) Susceptance
 - iv) State the unit of conductance and susceptance.

- c) A 3 phase star connected load having phase impedance of $(6 + j10)\Omega$ and is supplied from 3ϕ , 400V, 50 Hz, AC supply. Determine –
- Phase voltage
 - Current drawn by the load
 - Active power
 - Reactive power
- d) Calculate the current flowing through 10Ω resistance using superposition theorem. Refer Fig. No. 3

Fig. No. 3

5. Attempt any TWO of the following :

12

- a) Two impedance $(12 + j16)\Omega$ and $(10 - j20)\Omega$ are connected in parallel across a supply of $200\angle 60^\circ$. Using admittance method calculate branch current, total current and power factor of the whole circuit.

- b) Write the node voltage equation and determine the currents I_1 and I_2 for the network given below. Refer Fig. No. 4

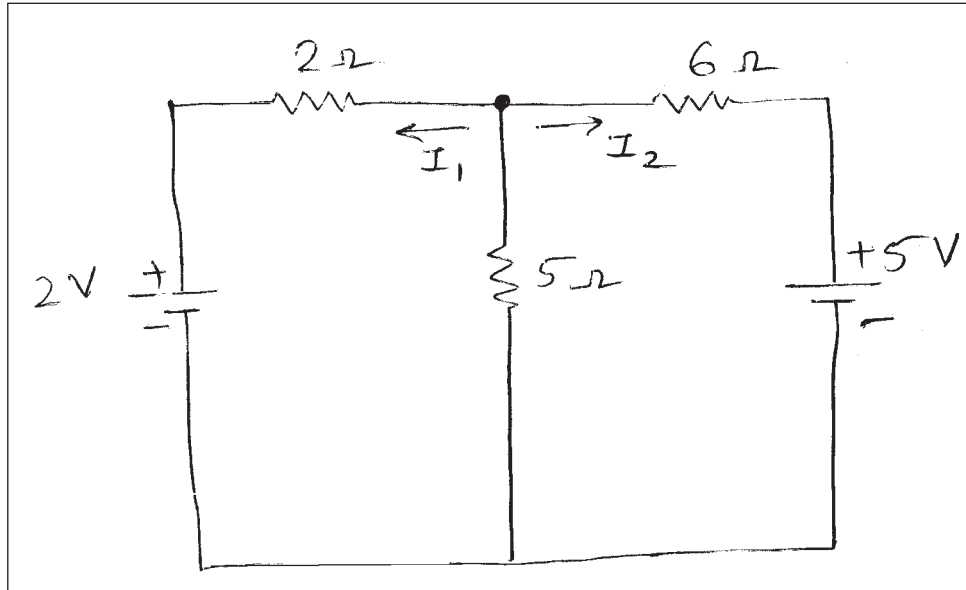


Fig. No. 4

- c) Determine the current through AB in the given circuit using Norton's theorem. Refer Fig. No. 5

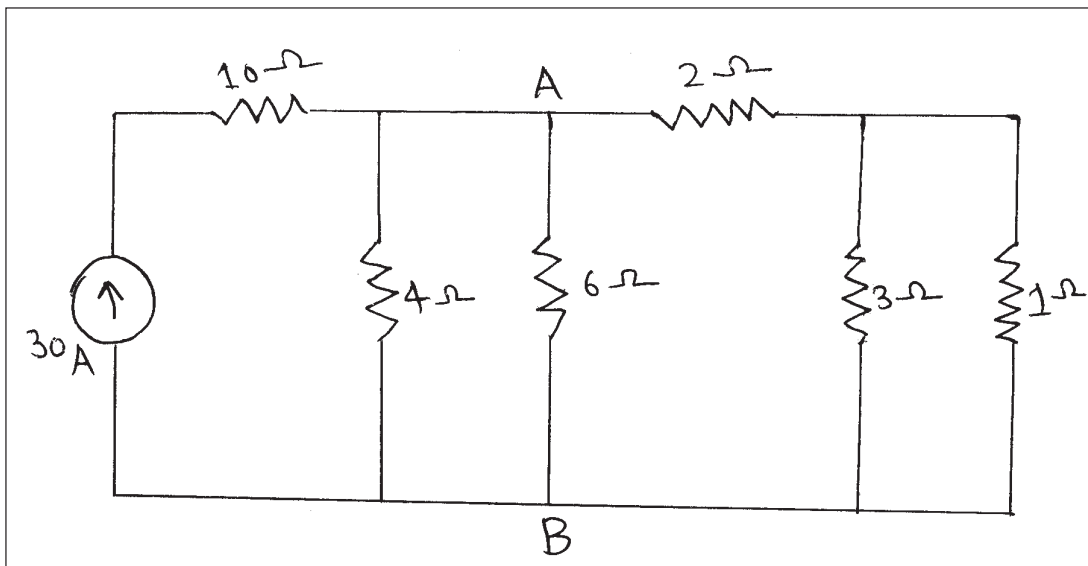
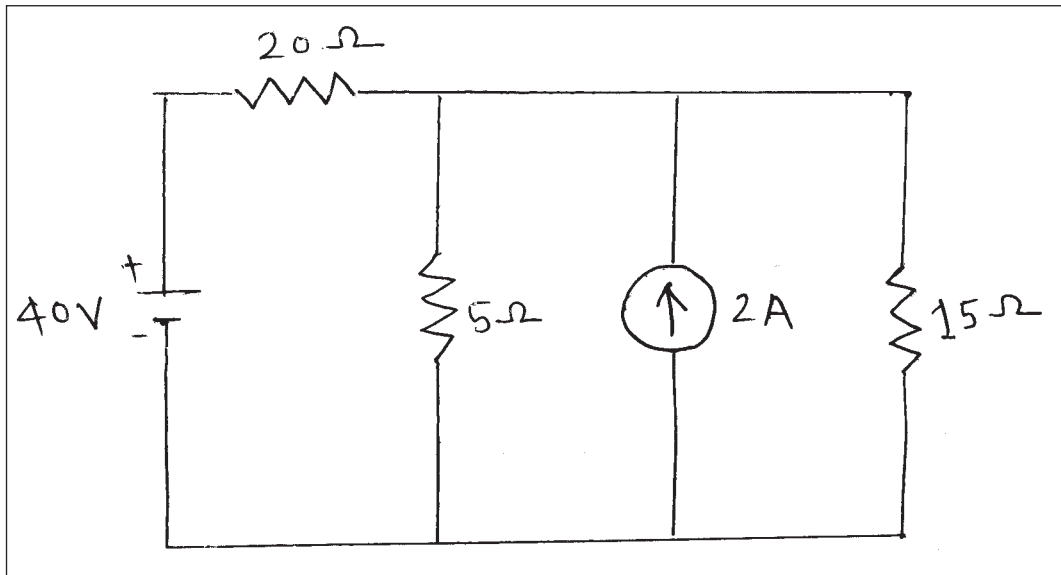


Fig. No. 5

6. Attempt any TWO of the following :**12**

- a) A coil of resistance 20 ohms is in series with a coil of 0.04 henry and is connected to ac mains at 200V and frequency 50 Hz then calculate –
- Current
 - Power factor
 - Voltage drop across resistance
 - Voltage drop across inductance.
- b) Three identical impedances are connected in delta to a 3 phase, 440 V. The line current is 40A and total power taken from the supply is 20 KW. Calculate resistance and reactance of each phase.
- c) Solve the given circuit to find the current through 15Ω resistance using Thevenin's theorem. Refer Fig. No. 6

**Fig. No. 6**